

# Microprocessor Final Design Document

Steven Bell

16 December 2010

CENG-3013

Oklahoma Christian University

# Contents

<b>1</b>	<b>Introduction</b>	<b>4</b>
1.1	Requirements . . . . .	4
<b>2</b>	<b>General Architecture Notes</b>	<b>5</b>
2.1	Chip-level IO . . . . .	5
2.2	Instruction set . . . . .	6
2.2.1	NOP . . . . .	6
2.2.2	ADD . . . . .	6
2.2.3	SUB . . . . .	6
2.2.4	MUL . . . . .	6
2.2.5	AND . . . . .	6
2.2.6	OR . . . . .	6
2.2.7	LSR . . . . .	6
2.2.8	LSL . . . . .	7
2.2.9	ASR . . . . .	7
2.2.10	ASL . . . . .	7
2.2.11	COMP . . . . .	7
2.2.12	NEG . . . . .	7
2.2.13	LOAD . . . . .	7
2.2.14	STORE . . . . .	7
2.2.15	MOVE . . . . .	7
2.2.16	Jump . . . . .	7
2.2.17	HALT . . . . .	8
<b>3</b>	<b>Module design</b>	<b>8</b>
3.1	Generic 16-bit register . . . . .	8
3.1.1	Design . . . . .	8
3.1.2	Testing . . . . .	8
3.2	Program counter . . . . .	9
3.2.1	Design . . . . .	9
3.2.2	Testing . . . . .	9
3.3	General-purpose register block . . . . .	9
3.3.1	Design . . . . .	9
3.3.2	Testing . . . . .	10
3.4	Arithmetic logic unit (ALU) . . . . .	10
3.4.1	Design . . . . .	11
3.4.2	Testing . . . . .	11
3.5	ALU Latch . . . . .	11
3.5.1	Design . . . . .	11
3.5.2	Testing . . . . .	12
3.6	Datapath . . . . .	12
3.6.1	Design . . . . .	12
3.6.2	Testing . . . . .	13
3.7	Control module . . . . .	14
3.7.1	State machine . . . . .	14
3.7.2	Control signal translation . . . . .	16
3.8	Address multiplexer . . . . .	18
3.9	Memory IO . . . . .	18
3.9.1	Design . . . . .	19
3.9.2	Testing . . . . .	19
3.10	Complete chip . . . . .	19
3.10.1	Design . . . . .	19

3.10.2 Testing . . . . .	20
<b>4 Hardware implementation</b>	<b>20</b>
4.1 Motivation and design criteria . . . . .	20
4.2 Part selection . . . . .	21
4.3 PCB Design . . . . .	21
4.4 Breadboard layout . . . . .	21
4.4.1 Pin mapping . . . . .	23
<b>5 Assembler</b>	<b>23</b>
<b>6 Conclusion</b>	<b>23</b>
6.1 Current status . . . . .	23
6.2 Future improvements . . . . .	24
<b>A Verilog module code</b>	<b>25</b>
A.1 Global constants . . . . .	25
A.2 Generic 16-bit register . . . . .	26
A.3 Program counter . . . . .	27
A.4 ALU . . . . .	27
A.5 ALU latch . . . . .	30
A.6 General-purpose register block . . . . .	31
A.7 Datapath . . . . .	32
A.8 Address Multiplexer . . . . .	33
A.9 Memory IO . . . . .	34
A.10 Control module state machine . . . . .	35
A.11 Control signals translator . . . . .	37
A.12 CPU . . . . .	40
<b>B Verilog testbench code</b>	<b>43</b>
B.1 Generic 16-bit register . . . . .	43
B.2 Program counter . . . . .	44
B.3 ALU . . . . .	46
B.4 ALU latch . . . . .	51
B.5 General-purpose register block . . . . .	52
B.6 Datapath . . . . .	55
B.7 Control module state machine . . . . .	61
B.8 Control signals translator . . . . .	65
B.9 CPU . . . . .	73
<b>C Output waveforms</b>	<b>76</b>
<b>D PCB diagrams</b>	<b>110</b>
D.1 Eagle schematic . . . . .	110
D.2 Eagle layout . . . . .	111
<b>E Assembler code</b>	<b>112</b>
<b>F Final test program</b>	<b>130</b>
<b>G Logic analyzer captures</b>	<b>135</b>

# 1 Introduction

The objective of this course (CENG-3013, Integrated Circuit Design) is to design an 8-bit microprocessor, model and simulate it using the Verilog hardware description language, and finally to implement it in hardware using a programmable logic device (PLD). This document describes my microprocessor design, the test code used to verify it, and the physical hardware implementation.

Three things make my work unique:

- Rather than using ABEL test vectors to test each Verilog module, I wrote all of my testbench code in Verilog. This had several advantages.
  - Using an all-Verilog approach enabled me to use tools other than Lattice ispLEVER Classic, most of which were far superior. I primarily used Icarus Verilog (<http://www.icarus.com/eda/verilog/>) combined with a Bash build script to automate the build and test process for all of the modules. Rather than having to build and test each module independently, I was able to run all of the tests at once and see the pass/fail results immediately. The build script also performed macro substitution, so a test failure message could refer to a specific line of code, rather than merely printing out a simulation timestep.
  - Verilog testbenches are vastly more flexible and efficient for testing large and complex modules. The CPU testbench simulates a block of ROM, which is loaded from a separate file. This makes it very easy to write additional test vectors and to copy the test code into the physical EEPROM. Likewise, the control module test consists of a short segment of Verilog code coupled with an easy-to-read text file containing the test process. This type of high-level testing made it extremely easy to add and edit tests.
  - Both Icarus Verilog and Aldec ActiveHDL perform functional simulation rather than gate-level simulation. This let me focus first on whether the code worked correctly, rather than puzzling over why the optimizer had removed my registers or combined all of my signals. Once the code worked, I could synthesize it with Synplicity and work out synthesis bugs.
- I constructed my own board using a Lattice MachXO PLD instead of using an LSI5512. The latter are no longer available, and have been replaced by the costly and already-outdated Mach4000 series. The MachXO parts are much less expensive, and (until the upcoming release of the MachXO2) are Lattice's flagship CPLD, with solid tool support and documentation.
- To circumvent the painstaking process of creating hexadecimal opcodes for the final test program, I wrote an assembler for my microprocessor which parses an input file and creates output files for Verilog simulation and EEPROM programming.

## 1.1 Requirements

The requirements in this section are taken from the project specification posted at the beginning of the semester:

- 8-bit data bus
- 16-bit address bus
- Eight 8-bit general purpose registers which can be used in pairs as four 16-bit registers.
- Instructions formatted as shown in Table 1.
- Instruction set as shown in Table 2.
- Jump condition codes as shown in Table 3.

Table 1: Instruction format

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Opcode					Source type		Destination type		Source register		Destination register			Condition	

Table 2: Required instruction set

Instruction	Opcode	Operands
NOP	0x00	-
Add	0x01	reg, reg/imm
Subtract	0x02	reg, reg/imm
Multiply	0x03	reg, reg/imm
Logical AND	0x04	reg, reg/imm
Logical OR	0x05	reg, reg/imm
Logical shift right	0x06	reg
Logical shift left	0x07	reg
Complement bits	0x08	reg
Load	0x10	reg, imm/address
Store	0x11	address, reg
Move	0x12	address, address
Jump	0x0F	address, condition
Halt	0x1F	-

Table 3: Jump condition codes

Condition	Bit designation
Always	00
Carry	01
Zero	10
Negative	11

## 2 General Architecture Notes

Where multi-byte values are used, they are stored in big-endian format, with the bits ordered from most significant to least significant. The processor has an 8-bit internal data bus which transfers data between the individual modules and connects to external RAM and ROM.

### 2.1 Chip-level IO

- Clock - Square wave input from function generator
- Reset - Active low input from switch
- Address bus - 16-bit output bus
- Data bus - 8-bit bidirectional bus
- ROM enable - Active low signal which enables the EEPROM
- RAM enable - Active low signal which enables the SRAM
- Memory write - Active high signal which switches the direction of the bidirectional buffer
- $\overline{\text{Write}}$  - Active low signal which enables writing to SRAM

## 2.2 Instruction set

This section briefly describes each of the instructions. Operations are considered to be 8-bit operations with 8-bit results, except for the multiply, which produces a 16-bit result. For each operation, the zero flag is set if the result contains all zeros.

The negative flag mirrors the most significant bit in the result. In the two's complement number system, this is equivalent to telling whether the value is positive or negative. Mathematical operations are performed exactly the same as for unsigned values, and the programmer can even choose to ignore the negative flag and work with the unsigned values (Wakerly, J. "Digital Design Principles and Practices, 4th Ed.", pp 37-43). In the event that a subtraction causes a borrow, the carry bit will be set, and this can be used to determine if a larger value was subtracted from a smaller value. This design is patterned after the operation of the negative flag in the Motorola M68HC11 ([www.freescale.com/files/microcontrollers/doc/ref\\_manual/M68HC11RM.pdf](http://www.freescale.com/files/microcontrollers/doc/ref_manual/M68HC11RM.pdf), page 204).

### 2.2.1 NOP

No operation. After reading this instruction, the processor continues immediately to the next instruction without any extra clock cycles.

### 2.2.2 ADD

Adds a value to a register. The source value can be another register, a memory location, or an 8-bit immediate. The carry flag is set if a one was carried out of the highest bit. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.3 SUB

Subtracts a value from a register. The source value can be another register, a memory location, or an 8-bit immediate. The carry flag is set if a one was borrowed. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero. Note that because the values are only 8 bits wide, 0x00 - 0x81 gives 0x80, which is not a negative number. Thus, the negative flag will not be set, but the carry bit will.

### 2.2.4 MUL

Multiplies an 8-bit register by an 8-bit value, producing a 16-bit result. The source value can be another register, a memory location, or an immediate. The result will be written to the destination register and its 16-bit pair, i.e, multiplying register a by register c will replace both a and b with the result. Best practice is to load both operands into a single register pair, so that no registers with other data are accidentally overwritten.

### 2.2.5 AND

Performs a bitwise AND between a register and a value. The source value can be another register, a memory location, or an 8-bit immediate. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.6 OR

Performs a bitwise OR between a register and a value. The source value can be another register, a memory location, or an 8-bit immediate. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.7 LSR

Performs a logical right-shift on a register and stores the result in the same register. All eight bits are shifted, and a zero is shifted into the top bit position. The carry flag is set if a 1 was shifted out. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.8 LSL

Performs a logical left-shift on a register and stores the result in the same register. All eight bits are shifted, and a zero is shifted into the lowest bit position. The carry flag is set if a 1 was shifted out. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.9 ASR

Performs an arithmetic right-shift on a register. Only the lower seven bytes are shifted; a copy of the sign bit is shifted into the bit position below the sign bit. The carry flag is set if a 1 was shifted out. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.10 ASL

Performs an arithmetic left-shift on a register. Only the lower seven bytes are shifted; a zero is shifted into the lowest bit position. The carry flag is set if a 1 was shifted out. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.11 COMP

Complements all of the bits in a register and stores the result in the same register. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.12 NEG

Performs a 2's complement (binary negation) on a register and stores the result in the same register. The negative flag is set if the highest bit is a 1, and the zero flag is set if the result is zero.

### 2.2.13 LOAD

Loads a value into a register. The source value can be a memory location or an immediate. The source can also be another register, which is also handled internally with the LOAD opcode. The assembler uses the mnemonic "COPY" to refer to loading one register into another.

### 2.2.14 STORE

Stores a register to RAM. A memory address is required.

### 2.2.15 MOVE

Copies the contents of one memory address to another. Two addresses are required; the register contents are not affected.

### 2.2.16 Jump

A jump relocates the current program counter to the memory location specified. After the jump completes, the processor immediately continues executing instructions at the new memory location.

The processor can jump:

- Always, regardless of ALU flags. This uses the assembler mnemonic "JMP"
- If the ALU carry bit was set in the last ALU operation. This uses the assembler mnemonic "JCAR"
- If the ALU zero bit was set in the last ALU operation. This uses the assembler mnemonic "JZERO"
- If the ALU negative bit was set in the last ALU operation. This uses the assembler mnemonic "JNEG"

### 2.2.17 HALT

Halts the processor's operation. No more instructions are read and the processor stays in the HALT state until it is reset.

## 3 Module design

### 3.1 Generic 16-bit register

A 16-bit register is used three times in the design: the jump register, the memory address register, and the instruction register. The same module is instantiated in all three of these cases.

#### 3.1.1 Design

The module has an 8-bit input, which in all three instantiations comes from the data bus. Two signals, `setHigh` and `setLow` determine whether this input is stored in the top half or bottom half of the register.

 


Figure 3.1: 16-bit register block diagram

The module code is shown in [Appendix A.2 on page 26](#).

#### 3.1.2 Testing

Since this was the first module coded, the test code was written in ABEL. It used the following procedure:

1. Reset the module, and ensure that the output is zero.
2. Load the high half of the register
3. Load the low half of the register
4. Load the high half while performing a reset. The reset should take precedence and the output should be zero.

The testbench code is shown in [Appendix B.1 on page 43](#).



## 3.2 Program counter

### 3.2.1 Design

The program counter holds the address of the next instruction byte and is used to index ROM when fetching instructions. It increases the output count by one on the rising edge of the clock when the `increment` signal is high. When the `set` signal is asserted, it loads the value from the jump register through the input `newCount`.

 


Figure 3.2: Program counter block diagram

The module code is shown in [Appendix A.3 on page 27](#).

### 3.2.2 Testing

The test uses the following procedure:

1. Perform a reset and check that the output is zero.
2. Leave the increment signal low and ensure that the counter does not increment and remains at zero.
3. Load the value 0xFFFF into the counter and check that the output equals 0xFFFF and was not incremented on this clock cycle.
4. Increment the counter and check that it equals 0x0000.
5. Increment the counter again and check that it rolls over to 0x0000.

The testbench code is shown in [Appendix B.2 on page 44](#).

## 3.3 General-purpose register block

The general-purpose register block contains 8 eight-bit registers which are used for data manipulation. They are grouped into pairs, creating 4 sixteen-bit registers which can receive the result of a multiply operation.

### 3.3.1 Design

Values are only stored on the rising edge of the clock, but the outputs are set via combinational logic. This means that the outputs are available immediately so register-to-register copies and ALU operations from the registers take place immediately without having to wait an additional clock cycle for the data to become available.

The register block has three 3-bit address inputs which are used to index the registers. The `input_select` input determines which register receives a value from the data bus if `read_data` is high; `output_select` determines which register is written when `write_data` is high. The `alu_output_value` bus goes directly to the ALU and is always active. The `alu_output_select` address determines which register is sent directly to the ALU on this bus.

The register pairing is not due to any hardware feature within the register block - the registers are implemented simply as an 8-element array of 8-bit registers. The pairing is performed by the control signals module, which

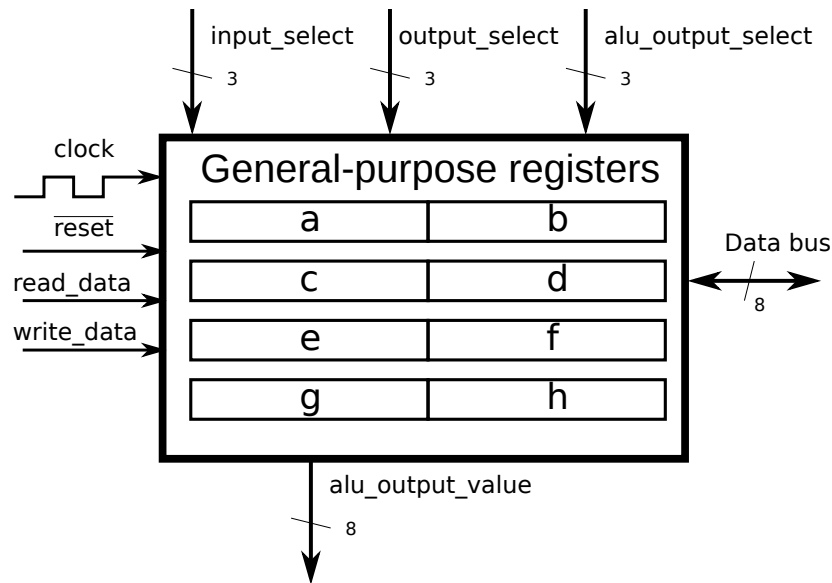


Figure 3.3: General-purpose registers block diagram

The module code is shown in [Appendix A.6 on page 31](#).

### 3.3.2 Testing

The test uses the following procedure:

1. Perform a reset.
2. Read all of the registers out and check that they read zero.
3. Sequentially load values into each of the registers.
4. Iterate back through the registers, read out their values, and check that they match what was stored.

The testbench code is shown in [Appendix B.5 on page 52](#)

## 3.4 Arithmetic logic unit (ALU)

The arithmetic logic unit implements all of the arithmetic operations specified: addition, subtraction, multiplication, logical AND and OR, left and right logical shifts, left and right arithmetic shifts, bitwise complement, and negation. It also contains a passthrough instruction so that the ALU latch can be used as a temporary register for the MOVE operation. Output flags are set based on the results of the operation.

### 3.4.1 Design

The ALU consists entirely of combinational logic and operations are performed whenever the inputs change. This wastes a tiny bit of power due to unnecessary gate switching, but simplifies the design. The output is only 8 bits, except for the multiply, which is 16 bits. The zero flag is defined for every operation: if the result is all zeros, the flag is set. Likewise, the negative flag is set whenever the highest bit of the result is a 1, which indicates a negative number in the two's complement system. The behavior and meaning of the carry flag is dependant on the operation. For add and subtract, it indicates a carry out or borrow in; for shifts, it indicates the bit that was shifted out.

 


Figure 3.4: ALU block diagram

The ALU module code is shown in [Appendix A.4 on page 27](#).

### 3.4.2 Testing

The ALU test consists of running a set of possible inputs and checking the result and the output flags. Each instruction is tested with several operations. The complete code is shown in [Appendix B.3 on page 46](#).

## 3.5 ALU Latch

The ALU latch grabs the result of the ALU operation, holds it, and then puts it on the databus when the store signals are asserted. It also latches the flags, so that a jump operates based on the last time the result was grabbed.

### 3.5.1 Design

The ALU latch uses a simple sequential design. The `alu_result` and `flags` are stored on the rising edge of the clock if `grab` is high. Combinational logic is used to determine which half of the stored value is put out to the data bus. If neither store signal is high, the output is high-z. The `flags_out` output is always enabled.

 


Figure 3.5: ALU latch block diagram

### 3.5.2 Testing

The test uses the following procedure:

1. Perform a reset.
2. Grab a value from the `alu_result` bus and hold it without putting the value on the data bus. The output should be high-z.
3. Put the high half of the value onto the data bus.
4. Put the low half of the value onto the data bus.
5. Grab a new value and put the result onto the data bus immediately.

Note that although the test passes as expected, the simulation ends as soon as the last test finishes so the final signal state is not shown on the waveform.

## 3.6 Datapath

### 3.6.1 Design

The datapath module combines the program counter, jump register, general-purpose registers, ALU, ALU latch, memory address register, and instruction register into a single unit connected by a data bus. The data bus is a bidirectional module port, so data can be brought in and out of the chip. A block diagram of the datapath is shown in Figure 3.6.

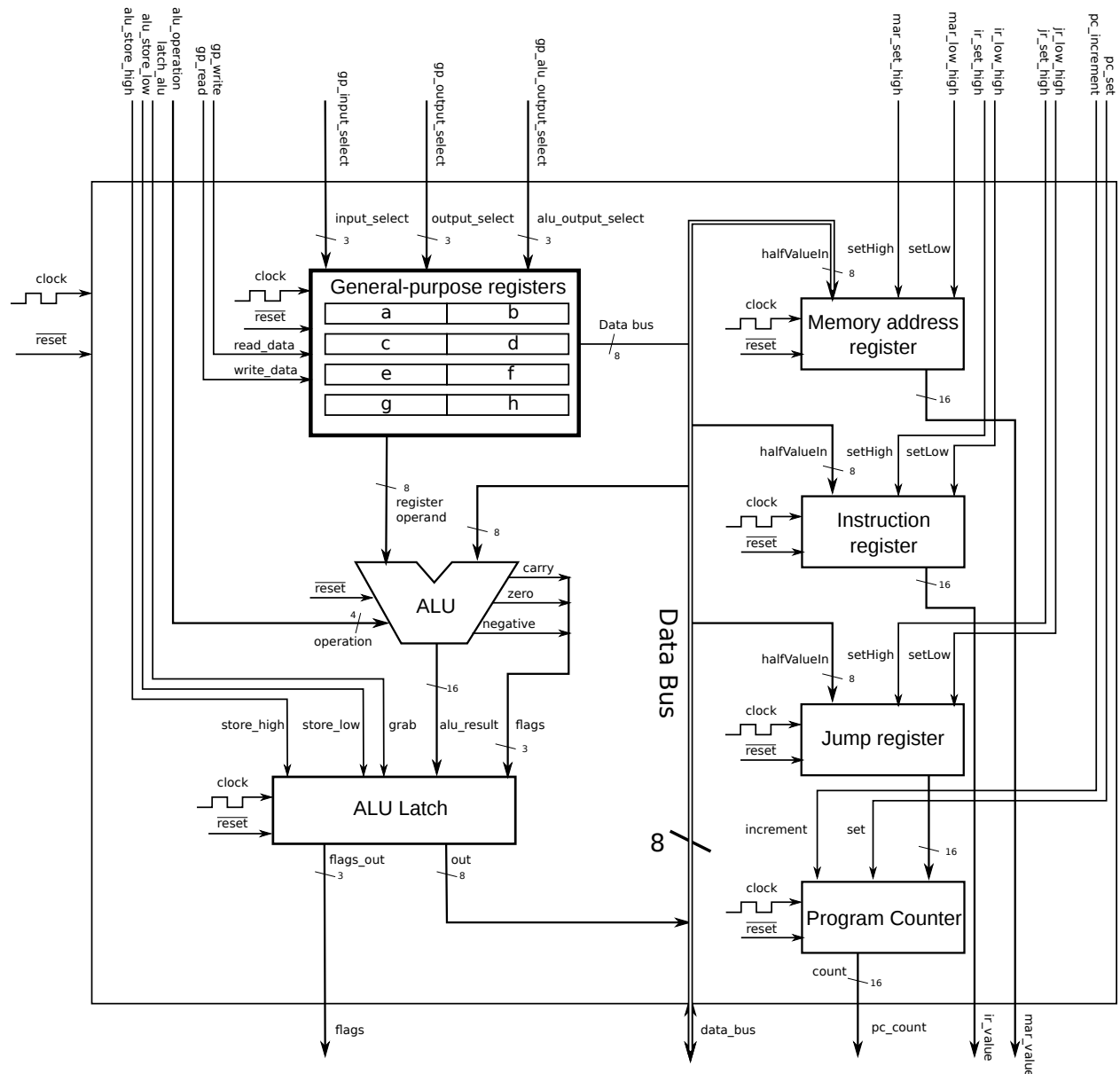


Figure 3.6: Datapath block diagram

### 3.6.2 Testing

The test uses the following procedure:

1. Perform a reset.
2. Load instruction register from the data bus (high and low).
3. Loading the jump register from the data bus (high and low).
4. Load program counter from jump register.
5. Iterate through each register and load a value from the data bus.
6. Iterate back through the registers and write it back to the data bus.

7. Load the memory address register from the data bus.
8. Load memory address register from the general-purpose registers.
9. Perform an ALU binary operation using two general-purpose registers.
10. Perform an ALU binary operation with an immediate.
11. Perform an ALU unary operation with a general-purpose register.
12. Perform an ALU passthrough and latch the ALU result.
13. Store the ALU result to data bus.

Reset for the general purpose registers is not tested.

### 3.7 Control module

The control module consists of two separate modules: a state machine which reads the output of the instruction register and determines what to do on the next clock cycle, and a signal translation module which maps the control state into controls signals for all of the other modules.

#### 3.7.1 State machine

**Design** The state diagram for the state machine is shown in Figure 3.8. The states are all defined as constants in a separate header file, shown in Appendix A.1 on page 25.

 


Figure 3.7: Block diagram of control module



**Testing** The testbench for the control state machine uses an external file which contains instruction bytes interleaved with the sequence of states which the module must go through. The testbench reads a line of the file and checks that the current state matches the expected state. If the state is either `FETCH_1` or `FETCH_2`, a hexadecimal byte is provided in the file and the testbench loads this into the simulated instruction register. Lines ending in a `#` symbol are comments and are ignored. A sample segment of the test file is shown below.

```

1  NOP#
2  FETCH_1
3  00
4  FETCH_2
5  00
6  Add#
7  FETCH_1
8  08
9  FETCH_2
10 20
11 ALU_OPERATION
12 STORE_RESULT_1
13 Multiply#
14 FETCH_1
15 18
16 FETCH_2
17 20
18 ALU_OPERATION
19 STORE_RESULT_1
20 STORE_RESULT_2

```

The test file checks every path of the state machine and ensures that each one works correctly.

### 3.7.2 Control signal translation

**Design** The state-to-control-vector matrix is shown in Table 4. Pure combinational logic with `assign` statements was used to produce the proper outputs. The general-purpose register addresses are taken directly from the opcode, except where the destination address is modified to produce a 16-bit store for the multiply operation. The ALU operation is taken directly from opcode bits [14:11].



Table 4: Mapping of states to control signals

	gp_read	gp_write	pc_set	pc_increment	mem_read	mem_write	latch_alu	alu_store_high	alu_store_low	ir_load_high	ir_load_low	jr_load_high	jr_load_low	mar_load_high	mar_load_low
RESET	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
FETCH_1	0	0	0	1	1	0	0	0	0	1	0	0	0	0	0
FETCH_2	0	0	0	1	1	0	0	0	0	0	1	0	0	0	0
FETCH_IMMEDIATE	?	0	0	1	1	0	0	0	0	0	0	0	0	0	0
ALU_OPERATION	0	1	0	0	0	0	1	0	0	0	0	0	0	0	0
ALU_IMMEDIATE	0	0	0	1	0	0	1	0	0	0	0	0	0	0	0
STORE_RESULT	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0
STORE_RESULT_2	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0
COPY_REGISTER_1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
COPY_REGISTER_2	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
FETCH_ADDRESS_1	0	0	0	1	1	0	0	0	0	0	0	0	0	1	0
FETCH_ADDRESS_2	0	0	0	1	1	0	0	0	0	0	0	0	0	0	1
FETCH_MEMORY	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0
STORE_MEMORY	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0
TEMP_FETCH	0	0	0	0	1	0	1	0	0	0	0	0	0	0	0
FETCH_ADDRESS_3	0	0	0	1	1	0	0	0	0	0	0	0	0	1	0
FETCH_ADDRESS_4	0	0	0	1	1	0	0	0	0	0	0	0	0	0	1
TEMP_STORE	0	0	0	0	0	1	0	0	1	0	0	0	0	0	0
LOAD_JUMP_1	0	0	0	1	1	0	0	0	0	0	0	1	0	0	0
LOAD_JUMP_2	0	0	0	1	1	0	0	0	0	0	0	0	1	0	0
EXECUTE_JUMP	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
HALT	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

The module also handles jump evaluation and execution. If the operation is a jump and the condition code is “always”, then the program counter `set` signal is asserted. If the operation is a jump, the condition code is `carry`, and the carry flag is set, then the signal is asserted. The same logic is used for the `carry` and `zero` jumps. No additional clock cycles are necessary for evaluating the jump.

 


Figure 3.9: Control signal translation module block diagram

The module code for the control signal translation module is shown in [Appendix A.11 on page 37](#).

**Testing** The testbench simply iterates through all of the states, setting the input state and then checking all of the outputs against those expected from the table. The testbench code is shown in [B.8 on page 65](#).

### 3.8 Address multiplexer

The address multiplexer switches the output address between the program counter and memory address register based on the state. If the processor is performing a load or store using a memory location, the MAR address is used; otherwise, the program counter is used. The module code is shown in [Appendix A.8 on page 33](#). The address multiplexer was tested as part of the CPU.

 


Figure 3.10: Address multiplexer block diagram

### 3.9 Memory IO

The memory IO module performs memory mapping to locate the ROM and RAM in address space, and translates the read and write signals into ROM and RAM chip enable signals.

### 3.9.1 Design

Because the program counter's reset is at 0x0000, it needs to find its first instruction at that memory location. This is done by memory-mapping the ROM to 0x0000 through 0x1FFF. The 8 by 8K RAM can occupy any portion of the address space; it was arbitrarily placed at 0x2000 through 0x3FFF. The module's operation is summarized in Table 5.

Table 5: Combinational operation of memory IO module

	Input address	
	0x0000 - 0x1FFFF	0x2000 - 0x3FFFF
readmemory = 1	rom_enable = 0, ram_enable = 1, write = 0	rom_enable = 1, ram_enable = 0, write = 0
writememory = 1	Invalid	rom_enable = 1, ram_enable = 0, write = 1
both low	rom_enable = 1, ram_enable = 1, write = 0	rom_enable = 1, ram_enable = 1, write = 0

 


Figure 3.11: Block diagram of memory IO module

### 3.9.2 Testing

The memory IO unit was tested as part of the CPU.

## 3.10 Complete chip

### 3.10.1 Design

The CPU module includes all of the other modules. It connects the control state machine to the datapath via the state translation module, connects the datapath to the outside using the address multiplexer and memory IO module. A block diagram of the CPU is shown in Figure 3.12. For clarity, the datapath control signals are collapsed into a single representative bus.

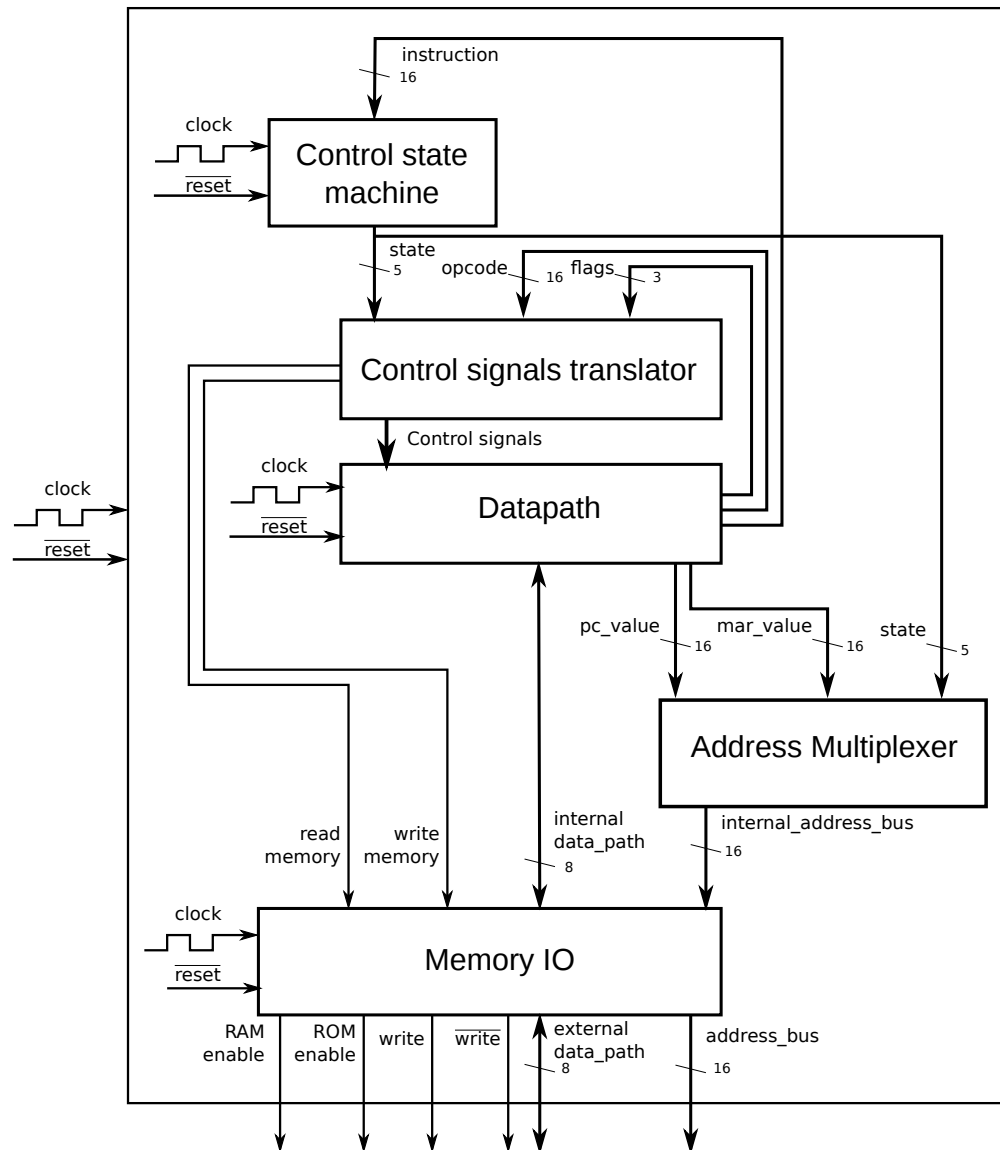


Figure 3.12: CPU block diagram

### 3.10.2 Testing

Rather than run a specific set of test vectors on the CPU, the testbench simulates RAM and ROM and effectively lets the chip run on its own. The initial ROM configuration is read in from a file produced by the assembler or by hand. The file contains a series of hexadecimal bytes, one per line. Lines beginning with the # symbol are comments and are ignored by the testbench.

After performing a reset, the testbench simply reads the address bus and memory enable lines and returns the appropriate value.

## 4 Hardware implementation

### 4.1 Motivation and design criteria

It was clear at the beginning of the class that many people would be competing for time on the implementation board, and its feature set and design are completely fixed. For these reasons, I decided early in the semester

to build my own board.

Two factors caused me to search for parts besides the LSI5512 provided in the class. There were relatively few chips and sockets available, and I assumed that other students would need them. Given that ours was the largest group of students to take this class at OC and that several graduate students would be building their own boards, a part shortage seemed imminent. More importantly, connecting wires to the 256-pin FPGBA socket is difficult and messy at best, and a debugging nightmare at worst. I desired some sort of breakout board which could interface easily with a breadboard.

## 4.2 Part selection

I researched several part families from Lattice, Xilinx, and Altera, comparing logic capacity, prices, IDE support, and other factors.

- The Lattice 4000V series (specifically the LC4512V) is the nominal successor to the discontinued LSI5000 series. It is compatible with the Lattice download cables in the Digital lab and is similar to the LSI5000 series. However, chips are surprisingly expensive (\$60), and is only supported by ispLEVER Classic, which compared to other tools is a very poor IDE.
- The Xilinx CoolRunner XC2C512 is moderately priced at \$40, and comes with a very powerful and polished IDE (Xilinx ISE WebPack), which Xilinx distributes for free. However, we do not have any download cables or programmers for the chip.
- In comparison to the CoolRunner CPLDs, Xilinx FPGAs are much cheaper and have an order of magnitude more gates. However, an FPGA is volatile, so it requires other hardware to be useful. Digilent makes several inexpensive (\$100-\$200) boards which contain a Xilinx Spartan FPGA and hardware to run them, including a USB-JTAG interface. This would be a simple and practical solution, but it is rather expensive and doesn't provide a simple interface to a breadboard.
- The Altera MAX II series is inexpensive (\$20), and has a free and powerful IDE. However, it requires a \$150 download cable.
- The Lattice MachXO series costs less than \$20 and works with programming cables in the Digital lab. It is fully supported by Lattice's newest IDE, known as Lattice Diamond. Although it does not seem as powerful as Xilinx ISE, Diamond is far superior to ispLEVER Classic.

My final selection was to use a MachXO series chip with a custom PCB.

The MachXO series uses a different architecture than traditional CPLDs which uses lookup tables rather than macrocells. The LCMXO-2280 has 2,280 lookup tables, which Lattice equates to 1140 macrocells. Early synthesis reports of my datapath showed approximately 200 macrocells used, and previous designs fit in the 512 macrocell LSI5512, so I was confident that my design would fit easily within the logic constraints of the LCMXO-2280.

## 4.3 PCB Design

I designed a 2-layer breakout PCB for the LCMXO-2280 using Eagle and had it fabricated by Advanced Circuits ([www.4pcb.com](http://www.4pcb.com)). The only other parts on the board were 16 eight-terminal female headers (Newark part #08N6773). One header is set up so that the ispDownload cable can be directly connected to the board (<http://www.latticesemi.com/lit/docs/devtools/dlcable.pdf>); a second header contains the  $V_{CC}$ ,  $V_{IO}$ , and ground connections for the device. The remaining headers are connected directly to the PLD's IO pins. The Eagle schematic and PCB layout are shown in Appendix D on page 110.

## 4.4 Breadboard layout

The breadboard was laid out as shown in Figure 4.1. A pair of 74HC245 buffers was used in series on the data bus to ensure that the 5 V external signals did not damage the chip. The data bus connects to a buffer running at 3.3 V, which connects to a buffer at 5 V, which connects to the RAM and ROM. Because each

buffer has a delay of approximately 100ns, the maximum clock speed of the processor is reduced to about 2 MHz. 74HC244 unidirectional buffers were used on the address bus.

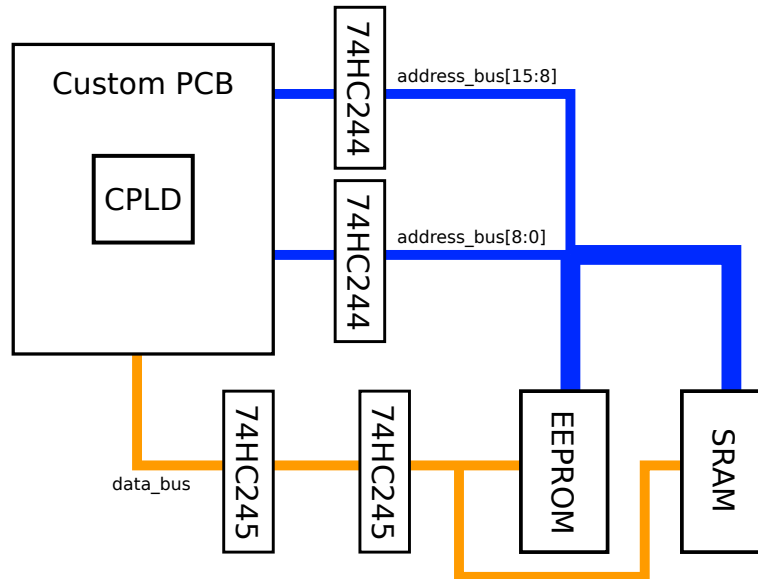


Figure 4.1: Block diagram of breadboard layout

Wires were color-coded using red for +3.3 V and +5 V, black for ground, blue for the address bus, orange for the data bus, green for other signals, and yellow for test points to the logic analyzer.

A photograph of the board is shown in Figure 4.2.

 


Figure 4.2: Photograph of the finished board

#### 4.4.1 Pin mapping

The MachXO pins are mapped as shown in the table below. The clock input is routed specifically as a clock pin by Lattice Diamond.

Port	Type	Pin	Port	Direction	Pin
clock	clock	1	address_bus_15	output	134
reset	input	76	address_bus_14	output	133
ram_enable	output	104	address_bus_13	output	132
rom_enable	output	105	address_bus_12	output	131
write	output	103	address_bus_11	output	130
write	output	102	address_bus_10	output	127
external_data_bus_7	bidirectional	95	address_bus_9	output	126
external_data_bus_6	bidirectional	94	address_bus_8	output	125
external_data_bus_5	bidirectional	92	address_bus_7	output	113
external_data_bus_4	bidirectional	91	address_bus_6	output	112
external_data_bus_3	bidirectional	90	address_bus_5	output	111
external_data_bus_2	bidirectional	89	address_bus_4	output	110
external_data_bus_1	bidirectional	87	address_bus_3	output	109
external_data_bus_0	bidirectional	86	address_bus_2	output	108
			address_bus_1	output	107
			address_bus_0	output	106

## 5 Assembler

The assembler is a command-line program written in C++ using the Qt framework. It takes an input file with assembly code based very loosely on Motorola 68HC11 assembly, and produces a Motorola SREC (.S19) file along with a hex dump which can be fed into the CPU simulation testbench. The assembler can handle labels as memory addresses, which is particularly useful for jump operations.

The assembler operates as follows:

1. The configuration is set up based on command-line parameters and the input file is opened.
2. One line of the file is read, broken up into individual tokens, and parsed.
3. If a label is encountered, the parser stores its memory address in a hash table for later reference.
4. If a label is referenced, the parser inserts the appropriate address.
5. If a label which has not yet been encountered is referenced, the parser adds the label to a table of unknown labels.
6. When the parser reaches the end of the file, it goes back through the unknown label list and fills in the remaining label references. If a label is still not defined, the assembler prints an error message.
7. The parser writes out the Motorola SREC file and, if requested, the simulation memory dump.

The complete assembler source code is given in Appendix E on page 112. Examples of the assembly source code which is parsed are given in Appendix F on page 130.

## 6 Conclusion

### 6.1 Current status

The required test program detailed in F on page 130 works correctly in simulation and in hardware. Captured waveforms from the logic analyzer are shown in Appendix G on page 135.

There is a bug in the ALU on certain multiplications: When a positive value is multiplied by a negative value to give a (e.g. -10 and 6, equivalent to 0xF5 and 0x06), the result is effectively treated as an 8-bit value but is put into the 16-bit register. Thus, rather than giving a 16-bit signed value, it returns an 8-bit signed value.

Arithmetic shifts are not working properly in the ALU, due to the way Verilog handles the arithmetic shift operator. The solution is to write a bit-level assignment to perform the arithmetic shift.

## 6.2 Future improvements

Several things could be improved on the current design. As my understanding of the Verilog language grew over the course of the semester, my coding style and practices evolved slightly. Were I to start again from scratch, I would:

- Be more careful in my differentiation of blocking and non-blocking assignments. Although my code works, it could probably be improved by using better logic design practices.
- Watch more closely for inferred latches and make sure to clock every module with storage. During the implementation phase, I had to fix several bugs related to inferred latches and unclocked operation.
- Run all of my testbenches based on the positive clock edges. Ultimately, my entire chip operates on the rising edge of the clock; nothing happens on the falling edge. However, I initially tested all of my modules assuming that inputs changed on the negative edges and that they did their work on the rising edge. This obscured my understanding of what was actually happening when I assembled the complete chip.
- Use port names to connect modules rather than argument order. This small syntactical feature was particularly useful at the CPU level, but would have been advantageous even for small modules.
- Define all constants in a single header file (with a .h extension) before writing my ALU and control state machine. I went through several iterations of merging and renaming files as I added new constants and switched build environments.



## A Verilog module code

### A.1 Global constants

```

1  /* constants.vh Definition file for chip-wide opcodes and other parameters
2  * Author: Steven Bell <steven.bell@student.oc.edu>
3  * Date: 4 November 2010
4  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
5  */
6
7  `ifndef _CONSTANTS_V_
8  `define _CONSTANTS_V_
9
10 `define ZEROFLAG 2
11 `define CARRYFLAG 1
12 `define NEGFLAG 0
13
14 // ALU Opcodes
15 // These are the four lower bits from the opcode (instruction bits 14-11)
16 `define ALU_PASSTHROUGH 4'b1100
17 `define ALU_ADD 4'b0001
18 `define ALU_SUBTRACT 4'b0010
19 `define ALU_MULTIPLY 4'b0011
20 `define ALU_AND 4'b0100
21 `define ALU_OR 4'b0101
22 `define ALU_LOGICAL_SHIFT_RIGHT 4'b0110
23 `define ALU_LOGICAL_SHIFT_LEFT 4'b0111
24 `define ALU_ARITH_SHIFT_RIGHT 4'b1001
25 `define ALU_ARITH_SHIFT_LEFT 4'b1010
26 `define ALU_TWOS_COMPLEMENT 4'b1011
27 `define ALU_COMPLEMENT 4'b1000
28 // Room for 2 more, 4'b1101 and 4'b1110
29 // 4'b0000 is taken for NOP 4'b1111 for JUMP - these will give a 0 result
30
31 // Control module opcodes
32 // These are the complete 5-bit opcodes used in the control module
33 `define NOP 5'b00000
34 `define ADD 5'b00001
35 `define SUBTRACT 5'b00010
36 `define MULTIPLY 5'b00011
37 `define AND 5'b00100
38 `define OR 5'b00101
39 `define LOGICAL_SHIFT_RIGHT 5'b00110
40 `define LOGICAL_SHIFT_LEFT 5'b00111
41 `define COMPLEMENT 5'b01000
42 `define ARITH_SHIFT_RIGHT 5'b01001
43 `define ARITH_SHIFT_LEFT 5'b01010
44 `define TWOS_COMPLEMENT 5'b01011
45 `define PASSTHROUGH 5'b01100
46 `define LOAD 5'b10000
47 `define STORE 5'b10001
48 `define MOVE 5'b10010
49 `define JUMP 5'b01111
50 `define HALT 5'b11111

```

```

51
52 `define SOURCE_REGISTER 2'b00
53 `define SOURCE_IMMEDIATE 2'b10
54 `define SOURCE_MEMORY 2'b01
55
56 // Control module states
57 // Used in the control module and the control_signals module
58 `define S_RESET 5'd0
59 `define S_FETCH_1 5'd1
60 `define S_FETCH_2 5'd2
61 `define S_ALU_OPERATION 5'd3
62 `define S_STORE_RESULT_1 5'd4
63 `define S_STORE_RESULT_2 5'd5
64 `define S_FETCH_IMMEDIATE 5'd6
65 `define S_COPY_REGISTER 5'd7
66 `define S_FETCH_ADDRESS_1 5'd8
67 `define S_FETCH_ADDRESS_2 5'd9
68 `define S_FETCH_MEMORY 5'd10
69 `define S_STORE_MEMORY 5'd11
70 `define S_TEMP_FETCH 5'd12
71 `define S_FETCH_ADDRESS_3 5'd13
72 `define S_FETCH_ADDRESS_4 5'd14
73 `define S_TEMP_STORE 5'd15
74 `define S_LOAD_JUMP_1 5'd16
75 `define S_LOAD_JUMP_2 5'd17
76 `define S_EXECUTE_JUMP 5'd18
77 `define S_HALT 5'd19
78 `define S_ALU_IMMEDIATE 5'd20
79
80 `endif

```

## A.2 Generic 16-bit register

```

1 /* register_16bit.v
2  * Implements a generic 16-bit register which is loaded in two
3  * sequential 8-byte actions.
4  * Author: Steven Bell <steven.bell@student.oc.edu>
5  * Date: 16 September 2010
6  * $LastChangedDate: 2010-09-23 08:44:58 -0500 (Thu, 23 Sep 2010) $
7  */
8
9 module register_16bit(clock, reset, setHigh, setLow, halfValueIn, valueOut);
10     input clock;
11     input reset; // Synchronous reset; active low
12     input setHigh; // When this signal is high, the top half of the value is
        loaded from the input line (data bus)
13     input setLow;
14     input [7:0] halfValueIn;
15     output reg [15:0] valueOut; // Output value containing both bytes
16
17     always @(posedge clock) begin
18         if(~reset) begin // If the reset line is low, then zero the register
19             valueOut = 0;
20         end

```

```

21     else if(setHigh) begin
22         valueOut[15:8] = halfValueIn; // Load the top half
23         // Leave the bottom half the same
24     end
25     else if(setLow) begin
26         // Leave the top half the same
27         valueOut[7:0] = halfValueIn; // Load the bottom half
28     end
29 end // END always
30
31 endmodule

```

### A.3 Program counter

```

1  /* program_counter.v
2  * Implements the 16-bit loadable program counter.
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 11 September 2010
5  * $LastChangedDate: 2010-11-23 09:34:58 -0600 (Tue, 23 Nov 2010) $
6  */
7
8  /* Program counter which is used to index memory to load instructions.
9  * It can be set to new values to implement a jump. We have to do the set
10 * in one shot, because otherwise we jump partway and can't get the next byte.
11 */
12 module program_counter(clock, reset, increment, set, new_count, count);
13     input clock;
14     input reset; // Synchronous reset; active low
15     input increment; // Only increment the counter when this signal is high
16     input set; // When this signal is high, the counter loads new_count into the
17         counter
18     input [15:0] new_count; // New value to set the counter to
19     output reg [15:0] count; // Output address of the program counter
20
21     // Clocked operation
22     always @(posedge clock) begin
23         if(~reset) begin // If the reset line is low, then zero the counter
24             count <= 0;
25         end
26         else if(set) begin // If set is high, then load a new value into the
27             counter
28             count <= new_count;
29         end
30         else if(increment) begin // Otherwise, if increment is high, add one to
31             the counter
32             count <= count + 1;
33         end
34     end // END always
35 endmodule

```

### A.4 ALU

```

1  /* alu.v
2  * Arithmetic logic unit.

```

```

3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 30 September 2010
5  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
6  */
7
8  `include "constants.v"
9
10 module alu(clock, reset, primaryOperand, secondaryOperand, operation, result,
    flags);
11     input clock; // TODO: remove the clock from the port list, since we're not
        using it anymore
12     input reset; // Asynchronous reset; active low
13     input[7:0] primaryOperand; // Used for all operations except passthrough
14     input[7:0] secondaryOperand; // Used for two-operand operations
15     input[3:0] operation; // Up to 16 operations
16     output[15:0] result;
17     reg[15:0] result;
18     output[2:0] flags;
19     reg[2:0] flags; // Zero, carry, negative
20
21     always @(*) begin
22         result[15:0] = 16'd0; // Reset all of the bits so we don't infer any
            latches
23                                     // But does the assignment (= rather than <=) cause
            extra logic?
24         // Do the requested operation
25         case(operation)
26             `ALU_PASSTHROUGH: begin
27                 result[7:0] = secondaryOperand; // Send the data bus input directly to
                    the result
28                 // It's pointless to pass the register operand through. If we need to
                    move it from
29                 // one register to another, we can just put it on the data bus.
30                 flags[`CARRYFLAG] = 1'b0; // There is never a carry on a passthrough
31                 flags[`NEGFLAG] = result[7];
32             end
33             `ALU_ADD: begin
34                 result[8:0] = primaryOperand + secondaryOperand;
35                 flags[`CARRYFLAG] = result[8]; // See if a bit was carried
36                 flags[`NEGFLAG] = result[7];
37             end
38             `ALU_SUBTRACT: begin
39                 result[8:0] = primaryOperand - secondaryOperand;
40                 flags[`CARRYFLAG] = result[8]; // If the bit is a 1, then we had to
                    borrow
41                 flags[`NEGFLAG] = result[7];
42             end
43             `ALU_MULTIPLY: begin
44                 result[15:0] = primaryOperand * secondaryOperand;
45                 flags[`CARRYFLAG] = 1'b0;
46                 flags[`NEGFLAG] = result[15];
47             end
48             `ALU_AND: begin
49                 result[7:0] = primaryOperand & secondaryOperand;

```

```

50     flags['CARRYFLAG'] = 1'b0;
51     flags['NEGFLAG'] = result[7];
52 end
53 'ALU_OR: begin
54     result[7:0] = primaryOperand | secondaryOperand;
55     flags['CARRYFLAG'] = 1'b0;
56     flags['NEGFLAG'] = result[7];
57 end
58 'ALU_LOGICAL_SHIFT_RIGHT: begin
59     result[7:0] = primaryOperand >> 1;
60     flags['CARRYFLAG'] = primaryOperand[0]; // Set the carry to be the bit
        that got shifted out
61     flags['NEGFLAG'] = result[7]; // This will always be 0; perhaps we
        should set it explicitly?
62 end
63 'ALU_LOGICAL_SHIFT_LEFT: begin
64     result[7:0] = primaryOperand << 1;
65     flags['CARRYFLAG'] = primaryOperand[7]; // Set the carry to be the bit
        that got shifted out
66     flags['NEGFLAG'] = result[7];
67 end
68 'ALU_ARITH_SHIFT_RIGHT: begin
69     result[7:0] = primaryOperand >>> 1;
70     flags['CARRYFLAG'] = primaryOperand[0]; // Set the carry to be the bit
        that got shifted out
71     flags['NEGFLAG'] = result[7];
72 end
73 'ALU_ARITH_SHIFT_LEFT: begin
74     result[7:0] = primaryOperand <<< 1;
75     flags['CARRYFLAG'] = primaryOperand[7]; // Set the carry to be the bit
        that got shifted out
76     flags['NEGFLAG'] = result[7];
77 end
78 'ALU_TWOS_COMPLEMENT: begin
79     result = ~primaryOperand; // Complement
80     result = result + 8'd1; // and add one
81     flags['CARRYFLAG'] = 1'b0;
82     flags['NEGFLAG'] = result[7];
83 end
84 'ALU_COMPLEMENT: begin
85     result = ~primaryOperand;
86     flags['CARRYFLAG'] = 1'b0;
87     flags['NEGFLAG'] = result[7];
88 end
89 default: begin
90     result[15:0] = 15'd0;
91     flags['CARRYFLAG'] = 1'b0;
92     flags['NEGFLAG'] = 1'b0;
93 end
94 endcase
95
96 if(operation == 'ALU_MULTIPLY) begin
97     flags['ZEROFLAG'] = (result[15:0] == 16'h0000) ? 1'b1 : 1'b0;
98 end

```

```

99     else begin
100         flags['ZEROFLAG] = (result[7:0] == 8'h00) ? 1'b1 : 1'b0;
101     end // if(operation == 'MULTIPLY)
102 end //always @(posedge clock)
103
104 endmodule

```

## A.5 ALU latch

```

1  /* alu_latch.v
2  * Grabs the result from the ALU and puts it on the data bus
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 11 October 2010
5  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
6  */
7
8  module alu_latch(
9      input clock,
10     input reset,
11     input[15:0] alu_result, // Result from the ALU
12     input[2:0] flags, // ALU flags which must also be latched
13     input grab, // Active-high signal telling us whether or not to latch the
        value
14     input store_high, // Put the top 8 bytes on the data bus (only used for
        multiply)
15     input store_low, // Put the low 8 bytes on the data bus
16     output reg[7:0] out,
17     output reg[2:0] flags_out
18 );
19
20     reg[15:0] value; // Stores the full-length output value
21
22     always @(posedge clock) begin
23         if(reset == 1'b0) begin
24             value <= 16'b0;
25         end
26         if(grab == 1'b1) begin // Latch the ALU value when the grab signal is high
27             value <= alu_result;
28             flags_out <= flags;
29         end
30     end // always
31
32     /* This part will synthesize into combinational logic which puts
33     * the appropriate set of signals onto the data bus. */
34     always @(*) begin
35         if(store_low == 1'b1) begin
36             out <= value[7:0];
37         end
38         else if(store_high == 1'b1) begin
39             out <= value[15:8];
40         end
41         else begin
42             out <= 8'hzz;
43         end

```

```

44     end
45
46 endmodule

```

## A.6 General-purpose register block

```

1  /* gp_registers.v
2  * 8x8 bit general purpose register set.
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 23 September 2010
5  * $LastChangedDate: 2010-12-14 09:01:55 -0600 (Tue, 14 Dec 2010) $
6  */
7
8  module gp_registers
9  (
10     input  clock,
11     input  reset, // Active-low synchronous reset
12     input  read_data, // Flag telling us whether or not to load a register value
13                   // from the data bus (active high)
14     input  write_data, // Flag telling us whether or not to write a register to
15                   // the data bus (active high)
16     // We'll just leave the ALU output always enabled, since it can't mess
17     // things up and we
18     // don't care about the slight increase in power consumption due to flipping
19     // unnecessary gates.
20
21     input[2:0] input_select, // Register to put the input value into
22     input[2:0] output_select, // Index of the register we want to put on the
23                   // data bus output
24     input[2:0] alu_output_select, // Index of the register we want to put on the
25                   // ALU output
26
27     inout[7:0] data_bus, // Contains the input value to store, or the output we
28                   // write
29     output[7:0] alu_output_value // Output bus to the ALU
30 );
31
32 reg[7:0] register_data[7:0]; // Data array, 8 bits x 8 registers
33 wire[7:0] output_value; // Temporary latch, because the data_bus is a wire
34                   // and not a reg
35
36 integer i; // Used for iterating through the registers when resetting them
37
38 always@(posedge clock) begin
39     if(reset == 1'b0) begin
40         // Remember that this code produces hardware, and all of the registers
41         // will be reset simultaneously
42         for(i = 0; i < 8; i = i+1) begin
43             register_data[i] <= 8'd0;
44         end
45     end
46
47     if(read_data == 1'b1) begin
48         register_data[input_select] <= data_bus;
49     end
50 end

```

```

40     end
41 end // always
42
43 // Combinational logic to interface with the data bus
44
45 assign output_value = register_data[output_select];
46 assign data_bus = write_data ? output_value : 8'hzz;
47 assign alu_output_value = register_data[alu_output_select];
48
49 endmodule

```

## A.7 Datapath

```

1  /* datapath.v
2   * Datapath which includes the general purpose registers, special purpose
3   * registers, ALU, and the connections between them.
4   * Author: Steven Bell <steven.bell@student.oc.edu>
5   * Date: 6 October 2010
6   * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
7   */
8
9  module datapath(
10     input  clock,
11     input  reset,
12     input  pc_increment,
13     input  pc_set,
14     input  gp_read,
15     input  gp_write,
16     input [2:0] gp_input_select,
17     input [2:0] gp_output_select,
18     input [2:0] gp_alu_output_select,
19     input [3:0] alu_operation,
20     input  latch_alu,
21     input  alu_store_high,
22     input  alu_store_low,
23     input  mar_set_high,
24     input  mar_set_low,
25     input  ir_set_high,
26     input  ir_set_low,
27     input  jr_set_high,
28     input  jr_set_low,
29
30     output wire [15:0] pc_count, // Program counter output
31     output wire [15:0] mar_value, // Memory address register output
32     output wire [15:0] ir_value, // Instruction register output
33     output wire [2:0] flags, // ALU flags
34
35     inout [7:0] data_bus
36 );
37
38 // Shared connections
39 wire [7:0] register_operand; // Bus from the general-purpose registers to the
    ALU

```



```

40  wire[15:0] pc_jump_count; // Bus from the jump register to the program
    counter (value to jump to)
41  wire[15:0] alu_result;
42  wire[2:0] flags_temp;
43
44  // Program counter (only reads from jump register, not data bus)
45  program_counter m_program_counter(clock, reset, pc_increment, pc_set,
    pc_jump_count, pc_count);
46
47  // Jump register which holds the value for the program counter to jump to
48  register_16bit m_jump_register(clock, reset, jr_set_high, jr_set_low,
    data_bus, pc_jump_count);
49
50  // General-purpose registers
51  gp_registers m_gp_registers(clock, reset, gp_read, gp_write, gp_input_select
    , gp_output_select, gp_alu_output_select, data_bus, register_operand);
52
53  // ALU and ALU latch
54  alu m_alu(clock, reset, register_operand, data_bus, alu_operation,
    alu_result, flags_temp);
55  alu_latch m_alu_latch(clock, reset, alu_result, flags_temp, latch_alu,
    alu_store_high, alu_store_low, data_bus, flags);
56
57  // Memory address register
58  register_16bit m_address_register(clock, reset, mar_set_high, mar_set_low,
    data_bus, mar_value);
59
60  // Instruction register
61  register_16bit m_instruction_register(clock, reset, ir_set_high, ir_set_low,
    data_bus, ir_value);
62
63
64
65  endmodule

```

## A.8 Address Multiplexer

```

1  /* address_mux.v Multiplexer that picks the output address bus value from
    either the MAR or
2  *           the program counter based the control module state.
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 6 December 2010
5  * $LastChangedDate: 2010-12-16 17:48:32 -0600 (Thu, 16 Dec 2010) $
6  */
7
8  `include "constants.v"
9
10 module address_mux(
11     input [15:0] pc_value,
12     input [15:0] mar_value,
13     input [4:0] state,
14     output [15:0] address_bus
15 );
16

```

```

17     assign address_bus = (state === `S_FETCH_MEMORY || state === `S_STORE_MEMORY
18         ||
19         state === `S_TEMP_FETCH || state === `S_TEMP_STORE) ?
20         mar_value : pc_value;
21 endmodule

```

## A.9 Memory IO

```

1  /* memio.v Memory IO module which performs memory mapping and holds the
2  * digital IO banks.
3  *
4  * Author: Steven Bell <steven.bell@student.oc.edu>
5  * Date: 5 December 2010
6  * $LastChangedDate$
7  */
8
9  module memio(
10     input read_memory,
11     input write_memory,
12     inout[7:0] internal_data_path,
13     inout[7:0] external_data_path,
14
15     input[15:0] address_in, // Full 16-bit address input
16     output[15:0] address_out, // Output address; not all 16 bits may be used
17     // TODO: digital inputs/outputs
18     output ram_enable, // Active low signal which turns the RAM on
19     output rom_enable, // Active low signal which turns the ROM on
20     output write, // Active high signal which tells the bidirectional buffers we
21         're writing
22     output write_bar // Opposite of write; active low signal which tells the RAM
23         we're writing
24 );
25 // TODO: use this to make sure we don't crash and burn if both read and
26 // write are asserted
27 wire enabled;
28 assign enabled = read_memory ^ write_memory;
29
30
31 assign internal_data_path = read_memory ? external_data_path : 8'hzz;
32 assign external_data_path = write_memory ? internal_data_path : 8'hzz;
33
34
35 // Map the ROM to 0000 - 1FFF
36 // Output is active low
37 assign rom_enable = !(address_in[15:13] === 3'b000);
38
39 // Map the RAM to 2000 - 3FFF
40 // Output is active low
41 assign ram_enable = !(address_in[15:13] === 3'b001);
42
43 assign address_out = address_in; // Passthrough for now
44 assign write = write_memory;
45 assign write_bar = !write_memory;
46
47 endmodule

```

## A.10 Control module state machine

```

1  /* control.v
2  * Control module which fetches instructions and drives all of the other
3  * modules.
4  * Author: Steven Bell <steven.bell@student.oc.edu>
5  * Date: 28 October 2010
6  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
7  */
8
9  `include "constants.v"
10
11 module control
12 (
13     input clock,
14     input reset,
15     input [15:0] instruction, // Value from the instruction register
16     output reg [4:0] state // Current control state
17 );
18
19 always @(posedge clock) begin
20
21     // Moving into reset is handled by an if statement at the end
22     case(state)
23         `S_RESET:
24             // Everything is zero
25             if(reset != 1'b0) begin // If reset is no longer asserted, it's time
26                 // to start!
27                 state <= `S_FETCH_1;
28             end
29         `S_FETCH_1:
30             // Always to go to fetch 2, since every opcode is two bytes
31             state <= `S_FETCH_2;
32         `S_FETCH_2:
33             // Figure out what to do next based on the first half of the opcode
34             // We won't have the second half until the end of the clock
35             if(instruction[15:11] == `NOP) begin
36                 state <= `S_FETCH_1;
37             end
38             else if(instruction[15:11] == `JUMP) begin
39                 state <= `S_LOAD_JUMP_1;
40             end
41             // If the opcode begins with a zero, then it's an ALU operation,
42             // except if it's
43             // 01101 or 01110, which are not used (JUMP and NOP are already
44             // handled)
45             else if(instruction[15] == 1'b0 && instruction[15:11] != 5'b01101 &&
46                 instruction != 5'b01110) begin
47                 if(instruction[10:9] == `SOURCE_REGISTER) begin
48                     state <= `S_ALU_OPERATION;
49                 end
50                 else begin // TODO: Crash gracefully if it's invalid
51                     state <= `S_ALU_IMMEDIATE;
52                 end
53             end
54         endcase
55     end
56 end

```

```

49     end
50     else if(instruction[15:11] == `LOAD) begin
51         if(instruction[10:9] == `SOURCE_REGISTER) begin
52             state <= `S_COPY_REGISTER;
53         end
54         else if(instruction[10:9] == `SOURCE_IMMEDIATE) begin
55             state <= `S_FETCH_IMMEDIATE;
56         end
57         else if(instruction[10:9] == `SOURCE_MEMORY) begin
58             state <= `S_FETCH_ADDRESS_1;
59         end
60     end
61     else if(instruction[15:11] == `STORE ||
62             instruction[15:11] == `MOVE) begin
63         state <= `S_FETCH_ADDRESS_1;
64     end
65     else if(instruction[15:11] == `S_HALT) begin
66         state <= `S_HALT;
67     end
68     else begin
69         state <= `S_HALT;
70     end
71
72     `S_ALU_OPERATION:
73         state <= `S_STORE_RESULT_1;
74
75     `S_ALU_IMMEDIATE:
76         state <= `S_STORE_RESULT_1;
77
78     `S_STORE_RESULT_1:
79         // If the operation was a multiply, we have to do 2 stores
80         if(instruction[15:11] == `MULTIPLY) begin
81             state <= `S_STORE_RESULT_2;
82         end
83         // Otherwise, we're ready for the next operation
84         else begin
85             state <= `S_FETCH_1;
86         end
87     `S_STORE_RESULT_2:
88         state <= `S_FETCH_1;
89     `S_FETCH_IMMEDIATE:
90         // Because this state is used both for storing immediates into the
91         // registers
92         // and for grabbing immediate values for the ALU, this state loads the
93         // immediate
94         // value into the register. It will be overwritten by the ALU result
95         // if there is one.
96         // This could be fixed by creating a separate state for loading
97         // immediates.
98         if(instruction[15:11] == `LOAD) begin
99             state <= `S_FETCH_1;
100         end
101         else begin
102             state <= `S_ALU_OPERATION;

```

```

99     end
100     `S_COPY_REGISTER:
101         state <= `S_FETCH_1;
102     `S_FETCH_ADDRESS_1:
103         state <= `S_FETCH_ADDRESS_2;
104     `S_FETCH_ADDRESS_2:
105         if(instruction[15:11] == `LOAD) begin
106             state <= `S_FETCH_MEMORY;
107         end
108         else if(instruction[15:11] == `STORE) begin
109             state <= `S_STORE_MEMORY;
110         end
111         else if(instruction[15:11] == `MOVE) begin
112             state <= `S_TEMP_FETCH;
113         end
114     `S_FETCH_MEMORY:
115         state <= `S_FETCH_1;
116     `S_STORE_MEMORY:
117         state <= `S_FETCH_1;
118     `S_TEMP_FETCH:
119         state <= `S_FETCH_ADDRESS_3;
120     `S_FETCH_ADDRESS_3:
121         state <= `S_FETCH_ADDRESS_4;
122     `S_FETCH_ADDRESS_4:
123         state <= `S_TEMP_STORE;
124     `S_TEMP_STORE:
125         state <= `S_FETCH_1;
126     `S_LOAD_JUMP_1:
127         state <= `S_LOAD_JUMP_2;
128     `S_LOAD_JUMP_2:
129         state <= `S_EXECUTE_JUMP;
130     `S_EXECUTE_JUMP:
131         state <= `S_FETCH_1;
132     `S_HALT:
133         state <= `S_HALT; // Just stay put!
134 endcase
135
136 if(reset == 0) begin
137     state <= `S_RESET;
138 end
139
140 end
141
142
143 endmodule

```

## A.11 Control signals translator

```

1  /* control_signals.v
2  * Module which translates the control module state into the set of control
   signals
3  * for the rest of the chip.
4  * Author: Steven Bell <steven.bell@student.oc.edu>
5  * Date: 24 November 2010

```

```

6  * $LastChangedDate$
7  */
8
9  `include "constants.v"
10
11 module control_signals(
12     input [4:0] state, // State from the control state machine
13     input [15:0] opcode, // Full 16-bit opcode from the instruction register
14     input [2:0] alu_flags, // Carry/Zero/Negative flags from ALU
15
16     output ir_load_high, // Load the high 8 bits of the instruction from the
        data bus
17     output ir_load_low, // Load the low 8 bits of the instruction
18     output gp_read, // Read a value from the data bus into a register
19     output gp_write, // Write a value from the register onto the data bus
20     output pc_set, // Set the program counter from the jump register
21     output pc_increment, // Increment the program counter
22     output mem_read, // Read a value from memory onto the data bus
23     output mem_write, // Write a value from the data bus out to memory (RAM)
24     output latch_alu,
25     output alu_store_high, // Write the high 8 bits of the ALU result to the
        data bus
26     output alu_store_low, // Write the low 8 bits of the ALU result to the data
        bus
27     output jr_load_high, // Load the high 8 bits of the jump destination into
        the jump register
28     output jr_load_low, // Load the low 8 bits of the jump destination
29     output mar_load_high, // Load the high 8 bits of the memory address into the
        MAR
30     output mar_load_low, // Load the low 8 bits of the memory address
31
32     output [3:0] alu_operation,
33     output [2:0] gp_input_select,
34     output [2:0] gp_output_select, // Register select for GP registers to data
        bus
35     output [2:0] gp_alu_output_select // Register select for GP registers
        directly to ALU
36 );
37
38 // Signals directly from the opcode
39 assign alu_operation = (opcode[15:11] === `MOVE) ? `ALU_PASSTHROUGH : opcode
    [14:11];
40 // The assignments below assume that the ALU operand directly from the GP
    registers
41 // is the "primary operand" used for unary operations.
42 assign gp_input_select[2:1] = opcode[4:3]; // GP registers from data bus
43
44 wire gp_address_force; // Bit used to force a particular address when using
    a multiply
45 assign gp_address_force = (state === `S_STORE_RESULT_2) ? 1'b1 : 1'b0;
46 assign gp_input_select[0] = (opcode[15:11] === `MULTIPLY) ? gp_address_force
    : opcode[2];
47 assign gp_output_select = opcode[7:5]; // GP registers to the data bus
48 assign gp_alu_output_select = opcode[4:2]; // GP registers to the ALU

```

```

49
50 // Signals from the state machine
51 assign ir_load_high = (state === 'S_FETCH_1);
52 assign ir_load_low = (state === 'S_FETCH_2);
53 // Read into the registers if we have a store, a copy, or are loading an
    immediate into a register
54 assign gp_read = (state === 'S_STORE_RESULT_1 || state === 'S_STORE_RESULT_2
    ||
55                 state === 'S_COPY_REGISTER || state === 'S_FETCH_MEMORY ||
56                 (state === 'S_FETCH_IMMEDIATE && opcode[15:11] === 'LOAD))
    ;
57 // Write from the registers if we have a register ALU operation or a store
58 assign gp_write = ((state === 'S_ALU_OPERATION && opcode[10:9] === 2'b00) ||
59                  state === 'S_STORE_MEMORY || state === 'S_COPY_REGISTER);
60 // Jump only if the code from the ALU tells us to
61 assign pc_set = (state === 'S_EXECUTE_JUMP &&
62                (opcode[1:0] === 2'b00 ||
63                 opcode[1:0] === 2'b01 && alu_flags['CARRYFLAG] == 1'b1) ||
64                 opcode[1:0] === 2'b10 && alu_flags['ZEROFLAG] == 1'b1) ||
65                 opcode[1:0] === 2'b11 && alu_flags['NEGFLAG] == 1'b1));
66
67 assign pc_increment = (state === 'S_FETCH_1 || state === 'S_FETCH_2 ||
68                       state === 'S_FETCH_IMMEDIATE || state ===
69                           'S_ALU_IMMEDIATE ||
70                           state === 'S_FETCH_ADDRESS_1 || state ===
71                           'S_FETCH_ADDRESS_2 ||
72                           state === 'S_FETCH_ADDRESS_3 || state ===
73                           'S_FETCH_ADDRESS_4 ||
74                           state === 'S_LOAD_JUMP_1 || state === 'S_LOAD_JUMP_2)
    ;
75 assign mem_read = (state === 'S_FETCH_1 || state === 'S_FETCH_2 ||
76                   state === 'S_FETCH_IMMEDIATE || state ===
77                       'S_ALU_IMMEDIATE ||
78                       state === 'S_FETCH_ADDRESS_1 || state ===
79                       'S_FETCH_ADDRESS_2 ||
80                       state === 'S_FETCH_MEMORY || state === 'S_TEMP_FETCH ||
81                       state === 'S_FETCH_ADDRESS_3 || state ===
82                       'S_FETCH_ADDRESS_4 ||
83                       state === 'S_LOAD_JUMP_1 || state === 'S_LOAD_JUMP_2);
84
85 assign mem_write = (state === 'S_STORE_MEMORY || state === 'S_TEMP_STORE);
86 assign latch_alu = (state === 'S_ALU_OPERATION || state === 'S_ALU_IMMEDIATE
87                     ||
88                     state === 'S_TEMP_FETCH);
89 // On store 1, store the lower half, unless there is a multiply.
90 assign alu_store_high = (state === 'S_STORE_RESULT_1 && opcode[15:11] ===
    'MULTIPLY);
91 assign alu_store_low = ((state === 'S_STORE_RESULT_1 && opcode[15:11] !==
    'MULTIPLY) ||
92                        state === 'S_STORE_RESULT_2 || state ===
93                            'S_TEMP_STORE);
94 assign jr_load_high = (state === 'S_LOAD_JUMP_1);
95 assign jr_load_low = (state === 'S_LOAD_JUMP_2);

```

```

88     assign mar_load_high = (state === `S_FETCH_ADDRESS_1 || state ===
      `S_FETCH_ADDRESS_3);
89     assign mar_load_low = (state === `S_FETCH_ADDRESS_2 || state ===
      `S_FETCH_ADDRESS_4);
90
91
92 endmodule

```

## A.12 CPU

```

1  /* cpu.v Top level module for IC design project
2  * Author: Steven Bell <steven.bell@student.oc.edu>
3  * Date: 5 December 2010
4  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
5  */
6
7  module cpu(
8      input clock,
9      input reset,
10     inout[7:0] external_data_bus,
11     output[15:0] address_bus,
12     output ram_enable,
13     output rom_enable,
14     output write,
15     output write_bar,
16     output[4:0] state
17 );
18
19     // Signals from control module to datapath
20     wire pc_increment;
21     wire pc_set;
22     wire gp_read;
23     wire gp_write;
24     wire[2:0] gp_input_select;
25     wire[2:0] gp_output_select;
26     wire[2:0] gp_alu_output_select;
27     wire[3:0] alu_operation;
28     wire latch_alu;
29     wire alu_store_high;
30     wire alu_store_low;
31     wire mar_set_high;
32     wire mar_set_low;
33     wire ir_set_high;
34     wire ir_set_low;
35     wire jr_set_high;
36     wire jr_set_low;
37
38     // Signals from datapath to control module
39     wire[15:0] ir_value; // Instruction register
40     wire[2:0] alu_flags;
41
42     // Other signals from datapath
43     wire[15:0] pc_count;
44     wire[15:0] mar_value;

```



```

45  wire[7:0] data_bus; // Internal data bus
46
47  //wire[4:0] state;
48  wire[15:0] address_mux_out;
49
50  datapath dp(.clock(clock),
51             .reset(reset),
52             .pc_increment(pc_increment),
53             .pc_set(pc_set),
54             .gp_read(gp_read),
55             .gp_write(gp_write),
56             .gp_input_select(gp_input_select),
57             .gp_output_select(gp_output_select),
58             .gp_alu_output_select(gp_alu_output_select),
59             .alu_operation(alu_operation),
60             .latch_alu(latch_alu),
61             .alu_store_high(alu_store_high),
62             .alu_store_low(alu_store_low),
63             .mar_set_high(mar_set_high),
64             .mar_set_low(mar_set_low),
65             .ir_set_high(ir_set_high),
66             .ir_set_low(ir_set_low),
67             .jr_set_high(jr_set_high),
68             .jr_set_low(jr_set_low),
69             .pc_count(pc_count),
70             .mar_value(mar_value),
71             .ir_value(ir_value),
72             .flags(alu_flags),
73             .data_bus(data_bus));
74
75  control cm(.clock(clock),
76            .reset(reset),
77            .instruction(ir_value),
78            .state(state));
79
80  control_signals cs(.state(state),
81                    .opcode(ir_value),
82                    .alu_flags(alu_flags),
83                    .ir_load_high(ir_set_high),
84                    .ir_load_low(ir_set_low),
85                    .gp_read(gp_read),
86                    .gp_write(gp_write),
87                    .pc_set(pc_set),
88                    .pc_increment(pc_increment),
89                    .mem_read(mem_read),
90                    .mem_write(mem_write),
91                    .latch_alu(latch_alu),
92                    .alu_store_high(alu_store_high),
93                    .alu_store_low(alu_store_low),
94                    .jr_load_high(jr_set_high),
95                    .jr_load_low(jr_set_low),
96                    .mar_load_high(mar_set_high),
97                    .mar_load_low(mar_set_low),
98                    .alu_operation(alu_operation),

```

```
99         .gp_input_select(gp_input_select),
100         .gp_output_select(gp_output_select),
101         .gp_alu_output_select(gp_alu_output_select));
102
103     address_mux am(.pc_value(pc_count),
104                   .mar_value(mar_value),
105                   .state(state),
106                   .address_bus(address_mux_out));
107
108
109     memio mem(.read_memory(mem_read),
110              .write_memory(mem_write),
111              .internal_data_path(data_bus),
112              .external_data_path(external_data_bus),
113              .address_in(address_mux_out),
114              .address_out(address_bus),
115              .ram_enable(ram_enable),
116              .rom_enable(rom_enable),
117              .write(write),
118              .write_bar(write_bar));
119
120 endmodule
```

## B Verilog testbench code

### B.1 Generic 16-bit register

```

1  // register_16bit_test.abv
2  // ABEL test vector file for register_16_bit.v
3  // Author: Steven Bell <steven.bell@student.oc.edu>
4  // Date: 16 September 2010
5  // $LastChangedDate: 2010-09-23 08:44:58 -0500 (Thu, 23 Sep 2010) $
6
7  MODULE register_16bit
8
9  // Inputs
10     clock pin;
11     reset pin;
12     setHigh pin;
13     setLow pin;
14     instructionByteIn_7_ pin;
15     instructionByteIn_6_ pin;
16     instructionByteIn_5_ pin;
17     instructionByteIn_4_ pin;
18     instructionByteIn_3_ pin;
19     instructionByteIn_2_ pin;
20     instructionByteIn_1_ pin;
21     instructionByteIn_0_ pin;
22
23
24  // Outputs
25     instructionOut_15_ pin;
26     instructionOut_14_ pin;
27     instructionOut_13_ pin;
28     instructionOut_12_ pin;
29     instructionOut_11_ pin;
30     instructionOut_10_ pin;
31     instructionOut_9_ pin;
32     instructionOut_8_ pin;
33     instructionOut_7_ pin;
34     instructionOut_6_ pin;
35     instructionOut_5_ pin;
36     instructionOut_4_ pin;
37     instructionOut_3_ pin;
38     instructionOut_2_ pin;
39     instructionOut_1_ pin;
40     instructionOut_0_ pin;
41
42  // Buses
43     instructionByteIn = [instructionByteIn_7_,instructionByteIn_6_,
44                           instructionByteIn_5_,instructionByteIn_4_,instructionByteIn_3_,
45                           instructionByteIn_2_,instructionByteIn_1_,instructionByteIn_0_];
46     instructionOut = [instructionOut_15_,instructionOut_14_,instructionOut_13_,
47                       instructionOut_12_,instructionOut_11_,instructionOut_10_,
48                       instructionOut_9_,instructionOut_8_,instructionOut_7_,
49                       instructionOut_6_,instructionOut_5_,instructionOut_4_,
50                       instructionOut_3_,instructionOut_2_,instructionOut_1_,

```

```

        instructionOut_0_];
45
46     u = .u.; // Rising edge
47     d = .d.; // Falling edge
48     x = .x.; // Don't care
49
50 Test_vectors
51 ([clock,reset,setHigh,setLow,instructionByteIn] -> [instructionOut])
52 [u, 0, 0, 0, ^hde] -> [^h0000]; // Reset
53 [u, 1, 1, 0, ^hde] -> [^hde00]; // Set high
54 [u, 1, 0, 1, ^had] -> [^hdead]; // Set low
55 [u, 0, 1, 0, ^hfa] -> [^h0000]; // Reset while setting high; reset should
    take precedence
56 [u, 1, 1, 1, ^hfa] -> [^hfa00]; // Set both high and low; high should should
    take precedence, low will not be set
57 [u, 1, 0, 1, ^hce] -> [^hface]; // Set low
58 END

```

## B.2 Program counter

```

1  /* program_counter_test.v
2  * Verilog testbench for program_counter.v
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 11 September 2010
5  * $LastChangedDate: 2010-11-23 09:34:58 -0600 (Tue, 23 Nov 2010) $
6  */
7
8  // Expected clock frequency is ~10 MHz = 100ns
9  // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
10 `timescale 1 ns / 10 ps
11
12 module program_counter_test();
13
14     reg reset = 1'b1; // Active low reset for the part
15     reg increment = 1'b0;
16     reg set = 1'b0; // Set the count from the external source
17     reg[15:0] counterIn = 16'hfffe; // Input value to the counter
18     wire[15:0] counterOut; // Counter output for accessing memory
19
20     // Clock
21     reg clock = 1'b0;
22     always #50 clock = !clock; // 100 time ticks per cycle = 10 MHz clock
23
24     program_counter pc_dut(clock, reset, increment, set, counterIn, counterOut);
25
26     // Test
27     initial begin
28         // Reset
29         @(negedge clock) begin
30             reset = 1'b0;
31         end
32         checkCount(16'b0, __LINE__);
33
34         // Check that counter doesn't increment without the signal being asserted

```

```

35     @(negedge clock) begin
36         reset = 1'b1;
37     end
38     checkCount(16'b0, __LINE__);
39
40     // Load a value
41     @(negedge clock) begin
42         set = 1'b1;
43     end
44     checkCount(16'hfffe, __LINE__);
45
46     // Load a value while incrementing, the new value should take precedence
47     @(negedge clock) begin
48         set = 1'b1;
49         increment = 1'b1;
50     end
51     checkCount(16'hfffe, __LINE__);
52
53     // Increment
54     @(negedge clock) begin
55         set = 1'b0;
56         increment = 1'b1;
57     end
58     checkCount(16'hffff, __LINE__);
59
60     // Test rollover
61     @(negedge clock) begin
62         increment = 1'b1;
63     end
64     checkCount(16'h0000, __LINE__);
65
66     $finish;
67 end
68
69
70 // Waveform log file and monitoring
71 initial begin
72     $dumpfile("program_counter.vcd");
73     $dumpvars();
74     //$monitor("time: %d, value: %h", $time, counterOut);
75 end
76
77 task checkCount(input[15:0] expected, input integer lineNum);
78 begin
79     @(posedge clock) #5 begin
80         if(counterOut == expected) begin
81             $display("%3d_-_Test_passed", lineNum);
82         end
83         else begin
84             $display("%3d_-_Test_failed,_expected_%h,_got_%h", lineNum, expected,
85                 counterOut);
86         end
87     end
88 end

```

```

88     endtask
89
90 endmodule

```

### B.3 ALU

```

1  /* alu_test.v
2  * Testbench for the arithmetic logic unit
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 30 September 2010
5  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
6  */
7
8  // Expected clock frequency is ~10 MHz = 100ns
9  // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
10 `timescale 1 ns / 10 ps
11
12 module alu_test();
13
14     reg reset = 1;
15     reg[7:0] registerParam; // Parameter from the general purpose registers (
        primary)
16     reg[7:0] databusParam; // Parameter from the data bus (secondary)
17     reg[3:0] operation; // Operation to perform
18     wire[15:0] result; // ALU result
19     wire[2:0] flags;
20
21     // Clock
22     reg clock = 0;
23     always #50 clock = !clock; //100 time ticks per cycle = 10 MHz clock
24
25     // DUT
26     alu aluDUT(clock, reset, registerParam, databusParam, operation, result,
        flags);
27
28     // Waveform file and monitoring
29     initial begin
30         $dumpfile("alu.vcd");
31         $dumpvars; // Dump everything
32         //$monitor("%d + %d = %d ", registerParam, databusParam, result);
33     end
34
35
36     initial begin
37         perform_reset();
38         // Test PASSTHROUGH
39         // Passthrough uses the secondary input (data bus) rather than the primary
        (GP registers)
40         test_operation(8'd0, 8'd2, `ALU_PASSTHROUGH, 8'd2, 3'b000, __LINE__); // "
        Normal" passthrough
41         test_operation(8'd1, 8'd0, `ALU_PASSTHROUGH, 8'd0, 3'b100, __LINE__); //
        Test zero
42         test_operation(8'd0, -8'd1, `ALU_PASSTHROUGH, -8'd1, 3'b001, __LINE__); //
        Test negative

```

```

43
44 // Test ADD
45 test_operation(8'd1, 8'd2, 'ALU_ADD, 8'd3, 3'b000, __LINE__); // Normal
    add
46 test_operation(8'd255, 8'd2, 'ALU_ADD, 8'd1, 3'b010, __LINE__); // Test
    carry
47 test_operation(8'd125, 8'd10, 'ALU_ADD, 8'd135, 3'b001, __LINE__); // Test
    negative
48 test_operation(-8'd15, 8'd10, 'ALU_ADD, -8'd5, 3'b001, __LINE__); // Test
    negative another way
49 test_operation(8'd250, 8'd6, 'ALU_ADD, 8'd0, 3'b110, __LINE__); // Test
    carry and zero
50
51 // Test SUBTRACT
52 // Note that the subtraction of a negative number causes a borrow because
    of the sign bit. This
53 // is not exactly the desired behavior, but it is the simplest logically
    consistent behavior.
54 test_operation(8'd10, 8'd6, 'ALU_SUBTRACT, 8'd4, 3'b000, __LINE__); //
    Normal subtract
55 test_operation(8'd10, 8'd10, 'ALU_SUBTRACT, 8'd0, 3'b100, __LINE__); //
    Test zero
56 test_operation(8'd10, 8'd15, 'ALU_SUBTRACT, -8'd5, 3'b011, __LINE__); //
    Test borrow and negative
57 test_operation(8'd2, -8'd6, 'ALU_SUBTRACT, 8'd8, 3'b010, __LINE__); //
    Subtraction of negative number
58 test_operation(-8'd128, 8'd1, 'ALU_SUBTRACT, 8'd127, 3'b000, __LINE__); //
    Test underflow (no borrow)
59
60 // Test MULTIPLY
61 test_operation16(8'd10, 8'd6, 'ALU_MULTIPLY, 16'd60, 3'b000, __LINE__); //
    Small multiply
62 test_operation16(8'd100, 8'd60, 'ALU_MULTIPLY, 16'd6000, 3'b000, __LINE__)
    ; // Large multiply
63 test_operation16(-8'd1, -8'd1, 'ALU_MULTIPLY, 16'd1, 3'b000, __LINE__); //
    Huge multiply
64 test_operation16(-8'd10, 8'd6, 'ALU_MULTIPLY, -16'd60, 3'b000, __LINE__);
    // Normal multiply
65 // BUG: Signed multiplication doesn't work exactly as I expect, due to the
    input values having only
66 // 8 bits but producing a 16-bit result.
67
68 // Test AND
69 test_operation(8'b10101010, 8'b01100110, 'ALU_AND, 8'b00100010, 3'b000,
    __LINE__); // Normal AND
70 test_operation(8'b10101010, 8'b01010101, 'ALU_AND, 8'b00000000, 3'b100,
    __LINE__); // Test zero
71 test_operation(8'b10101010, 8'b11100110, 'ALU_AND, 8'b10100010, 3'b001,
    __LINE__); // Test negative
72
73 // Test OR
74 test_operation(8'b00101010, 8'b01100110, 'ALU_OR, 8'b01101110, 3'b000,
    __LINE__); // Normal OR

```

```

75     test_operation(8'b10101010, 8'b01100110, 'ALU_OR, 8'b11101110, 3'b001,
       __LINE__); // Test negative
76     test_operation(8'b00000000, 8'b00000000, 'ALU_OR, 8'b00000000, 3'b100,
       __LINE__); // Test zero
77
78     // Test LOGICAL_SHIFT_RIGHT
79     test_operation(8'b10101010, 8'b11111111, 'ALU_LOGICAL_SHIFT_RIGHT, 8'
       b01010101, 3'b000, __LINE__); // Shift out a 0
80     test_operation(8'b10101011, 8'b11111111, 'ALU_LOGICAL_SHIFT_RIGHT, 8'
       b01010101, 3'b010, __LINE__); // Shift out a 1
81     test_operation(8'b00000000, 8'b11111111, 'ALU_LOGICAL_SHIFT_RIGHT, 8'
       b00000000, 3'b100, __LINE__); // Test zero
82
83     // Test LOGICAL_SHIFT_LEFT
84     test_operation(8'b00101010, 8'b11111111, 'ALU_LOGICAL_SHIFT_LEFT, 8'
       b01010100, 3'b000, __LINE__); // Shift out a 0
85     test_operation(8'b10101010, 8'b11111111, 'ALU_LOGICAL_SHIFT_LEFT, 8'
       b01010100, 3'b010, __LINE__); // Shift out a 1
86     test_operation(8'b00000000, 8'b11111111, 'ALU_LOGICAL_SHIFT_LEFT, 8'
       b00000000, 3'b100, __LINE__); // Test zero
87     test_operation(8'b11000000, 8'b11111111, 'ALU_LOGICAL_SHIFT_LEFT, 8'
       b10000000, 3'b011, __LINE__); // Test carry and negative
88
89     // Test ARITH_SHIFT_RIGHT
90     test_operation(8'b00101010, 8'b11111111, 'ALU_ARITH_SHIFT_RIGHT, 8'
       b00010101, 3'b000, __LINE__); // Shift out a 0
91     test_operation(8'b00101011, 8'b11111111, 'ALU_ARITH_SHIFT_RIGHT, 8'
       b00010101, 3'b010, __LINE__); // Shift out a 1
92     test_operation(8'b00000000, 8'b11111111, 'ALU_ARITH_SHIFT_RIGHT, 8'
       b00000000, 3'b100, __LINE__); // Test zero
93     test_operation(8'b10101010, 8'b11111111, 'ALU_ARITH_SHIFT_RIGHT, 8'
       b11010101, 3'b001, __LINE__); // Test sign bit shift
94     // BUG: The test above fails - apparently Verilog only does an arithmetic
       shift if the value is signed
95     // so it seems to just be doing a logical shift. I could hack an
       arithmetic shift, or maybe there is
96     // a way to treat the input as a signed value?
97
98     // Test ARITH_SHIFT_LEFT
99     test_operation(8'b00101010, 8'b11111111, 'ALU_ARITH_SHIFT_LEFT, 8'
       b01010100, 3'b000, __LINE__); // Shift out a 0
100    test_operation(8'b10101010, 8'b11111111, 'ALU_ARITH_SHIFT_LEFT, 8'
       b01010100, 3'b010, __LINE__); // Shift out a 1
101    test_operation(8'b01101010, 8'b11111111, 'ALU_ARITH_SHIFT_LEFT, 8'
       b11010100, 3'b001, __LINE__); // Test overflow
102    test_operation(8'b00000000, 8'b11111111, 'ALU_ARITH_SHIFT_LEFT, 8'
       b00000000, 3'b100, __LINE__); // Test zero
103
104    // Test TWOS_COMPLEMENT
105    test_operation(8'b00000001, 8'b11111111, 'ALU_TWOS_COMPLEMENT, 8'b11111111
       , 3'b001, __LINE__); // 1 -> -1
106    test_operation(8'b10000000, 8'b11111111, 'ALU_TWOS_COMPLEMENT, 8'b10000000
       , 3'b001, __LINE__); // 128 -> -128

```



```

107     test_operation(8'd50, 8'b11111111, 'ALU_TWOS_COMPLEMENT, -8'd50, 3'b001,
108         __LINE__); // 50 -> -50
109     test_operation(-8'd50, 8'b11111111, 'ALU_TWOS_COMPLEMENT, 8'd50, 3'b000,
110         __LINE__); // -50 -> 50
111     test_operation(8'd0, 8'b11111111, 'ALU_TWOS_COMPLEMENT, 8'd0, 3'b100,
112         __LINE__); // 50 -> -50
113
114     // Test COMPLEMENT
115     test_operation(8'b10000001, 8'b11111111, 'ALU_COMPLEMENT, 8'b01111110, 3'
116         b000, __LINE__); // Test positive
117     test_operation(8'b00000001, 8'b11111111, 'ALU_COMPLEMENT, 8'b11111110, 3'
118         b001, __LINE__); // Test negative
119     test_operation(8'b11111111, 8'b11111111, 'ALU_COMPLEMENT, 8'b00000000, 3'
120         b100, __LINE__); // Test zero
121
122     @(negedge clock) begin
123         $finish;
124     end
125 end
126
127 /* Cycles the reset input to the ALU to put it into a known state.
128  * Takes no parameters. */
129 task perform_reset();
130     begin
131         @(negedge clock) begin
132             reset = 0;
133         end
134         @(negedge clock) begin
135             reset = 1;
136         end
137     end
138 endtask
139
140 /* Performs an ALU operation giving an 8 bit result and determines whether the
141  * result and flags match the expected results and flags.
142  *
143  * tParam1 - First operand for the ALU; typically from the general purpose
144  *           registers
145  * tParam2 - Second operand for the ALU; typically from the data bus
146  * tOperation - Operation to perform on the two operands
147  * tExpectedValue - Expected result of the operation
148  * tExpectedFlags - Expected zero, carry, and negative flags from the
149  *                 operation
150  * lineNum - Line number the test is on. This should generally be a
151  *           preprocessor macro.
152  */
153 task test_operation(input[7:0] tParam1, input[7:0] tParam2, input[3:0]
154     tOperation,
155     input[7:0] tExpectedValue, input[2:0] tExpectedFlags,
156     input integer lineNum);
157     begin
158         @(negedge clock) begin // Wait for falling edge

```

```

150     registerParam = tParam1; // Set the inputs
151     databusParam = tParam2;
152     operation = tOperation; // Select the operation
153 end
154 @(posedge clock) begin // Wait for rising edge, and delay so the values
    are stable
155     #5;
156     if(result[7:0] != tExpectedValue) begin // Check the outputs
157         $display("%3d_-_Test_failed!_Expected_result_%d,_got_%d", lineNum,
            tExpectedValue, result[7:0]);
158     end
159     else if(flags != tExpectedFlags) begin
160         $display("%3d_-_Test_failed!_Expected_flags_%b,_got_%b", lineNum,
            tExpectedFlags, flags);
161     end
162     else begin
163         $display("%3d_-_Test_passed", lineNum);
164     end
165 end // @(posedge clock)
166 end // task
167 endtask
168
169
170 /* Performs an ALU operation giving a 16-bit result and determines whether the
171 * result and flags match the expected results and flags.
172 *
173 * tParam1 - First operand for the ALU; typically from the general purpose
    registers
174 * tParam2 - Second operand for the ALU; typically from the data bus
175 * tOperation - Operation to perform on the two operands
176 * tExpectedValue - Expected result of the operation
177 * tExpectedFlags - Expected zero, carry, and negative flags from the
    operation
178 * lineNum - Line number the test is on. This should generally be a
    preprocessor macro.
179 */
180 task test_operation16(input[7:0] tParam1, input[7:0] tParam2, input[3:0]
    tOperation,
181                     input[15:0] tExpectedValue, input[2:0] tExpectedFlags,
    input integer lineNum);
182 begin
183     @(negedge clock) begin // Wait for falling edge
184         registerParam = tParam1; // Set the inputs
185         databusParam = tParam2;
186         operation = tOperation; // Select the operation
187     end
188     @(posedge clock) begin // Wait for rising edge, and delay so the values
        are stable
189         #5;
190         if(result[15:0] != tExpectedValue) begin // Check the outputs
191             $display("%3d_-_Test_failed!_Expected_result_%d,_got_%d", lineNum,
                tExpectedValue, result[7:0]);
192         end
193         else if(flags != tExpectedFlags) begin

```

```

194     $display("%3d_-_Test_failed!_Expected_flags_%b,_got_%b", lineNum,
        tExpectedFlags, flags);
195     end
196     else begin
197         $display("%3d_-_Test_passed", lineNum);
198     end
199     end
200     // Print the result
201     end
202 endtask
203
204
205 endmodule

```

## B.4 ALU latch

```

1  /* alu_latch_test.v
2  * Testbench for the ALU latch
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 14 October 2010
5  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
6  */
7
8  // Expected clock frequency is ~10 MHz = 100ns
9  // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
10 `timescale 1 ns / 10 ps
11
12 module alu_latch_test();
13     reg reset = 1;
14     reg[15:0] alu_result;
15     reg grab;
16     reg store_high;
17     reg store_low;
18     wire[7:0] databus; // Output of ALU latch goes to data bus (for now)
19
20     // Clock
21     reg clock = 0;
22     always #50 clock = ~clock; // 100 time ticks per cycle = 10 MHz clock
23
24     // DUT
25     alu_latch latchDUT(.clock(clock),
26                        .reset(reset),
27                        .alu_result(alu_result),
28                        .grab(grab),
29                        .store_high(store_high),
30                        .store_low(store_low),
31                        .out(databus));
32
33     // Monitoring and dumpfile
34     initial begin
35         $dumpfile("alu_latch.vcd");
36         $dumpvars; // Dump everything
37     end
38

```

```

39 // Beginning of test
40 initial begin
41     @(negedge clock) begin
42         reset = 0;
43     end
44     @(negedge clock) begin
45         reset = 1;
46     end
47
48     //      input      grab  high  low  expected
49     do_test(16'hbeef, 1'b1, 1'b0, 1'b0, 8'hzz, __LINE__); // Latch a value,
50         but don't put it out
51     do_test(16'hdead, 1'b0, 1'b1, 1'b0, 8'hbe, __LINE__); // Hold the value
52         and put the high half out
53     do_test(16'hdead, 1'b0, 1'b0, 1'b1, 8'hbf, __LINE__); // Hold the value
54         and put the low half out
55     do_test(16'hface, 1'b1, 1'b0, 1'b1, 8'hce, __LINE__); // Load a new value
56         and put it's low half out
57
58     $finish; // End the simulation
59 end
60
61 task do_test(input [15:0] r, input g, input h, input l, input [7:0] expected,
62     input integer line);
63 begin
64     @(negedge clock) begin
65         alu_result = r;
66         grab = g;
67         store_high = h;
68         store_low = l;
69     end
70     @(posedge clock) begin
71         #5; // Wait for the bits to flip, then check them
72         if(databus === expected) begin
73             $display("%3d_ _Test_passed", line);
74         end
75         else begin
76             $display("%3d_ _Test_failed!_Expected_%h,_got_%h", line, expected,
77                 databus);
78         end
79     end
80 end
81 endtask
82 endmodule

```

## B.5 General-purpose register block

```

1 /* gp_registers_test.v
2  * Testbench for the general purpose register set.
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 23 September 2010
5  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $

```

```

6  */
7
8  // Expected clock frequency is ~10 MHz = 100ns
9  // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
10 `timescale 1 ns / 10 ps
11
12 module gp_registers_test;
13
14     reg reset;
15     reg read_data; // save data to register
16     reg write_data; // write data from register
17     reg[2:0] input_select; // Register to put the input value into
18     reg[2:0] output_select; // Index of the register we want to put on the data
        bus output
19     reg[2:0] alu_output_select; // Index of the register we want to put on the
        ALU output
20
21     wire[7:0] data_bus; // Contains the input value to store, or the output we
        write
22     wire[7:0] alu_output_value; // Output bus to the ALU
23
24     // Data bus
25     reg[7:0] data_bus_driver; // Simulation of another device driving the data
        bus
26     reg data_bus_driven; // Whether or not something else is driving the data
        bus
27     assign data_bus = data_bus_driven ? data_bus_driver : 8'hzz;
28
29     // Test variables
30     parameter NUM_REGISTERS = 8; // Number of registers we have
31     integer regidx; // Used to cycle through the registers
32
33     // Clock
34     reg clock = 0;
35     always #50 clock = !clock; //100 time ticks per cycle = 10 MHz clock
36
37     // DUT
38     gp_registers registers(clock, reset, read_data, write_data,
39                           input_select, output_select, alu_output_select,
40                           data_bus, alu_output_value);
41
42     // Waveform log file
43     initial begin
44         $dumpfile("gp_registers.vcd");
45         $dumpvars; // Dump everything
46         //$monitor("time: %5d, clock: %d, reset: %d ", $time, clock, reset);
47     end
48
49     // Test code
50     initial begin
51         // Reset the registers
52         @(negedge clock)
53             reset = 0;
54         @(negedge clock)

```

```

55     reset = 1;
56
57
58     // Iterate through the registers and check that they were reset
59     for(regidx = 0; regidx < NUM_REGISTERS; regidx = regidx + 1) begin
60         // On the negative edge of the clock, request the value out both ports
61         @(negedge clock) begin
62             write_data = 1'b1; // The registers will be writing data out to the
63                 bus
64             read_data = 1'b0;
65             output_select = regidx;
66             alu_output_select = regidx;
67         end
68         // On the positive edge, read the output and check it
69         @(posedge clock) begin
70             #30; // Wait for the value to change - is there a better way?
71             if(data_bus != 8'h00 || alu_output_value != 8'h00) begin
72                 $display("Register_%d_not_reset!_Value_is_%d/%d", regidx, data_bus,
73                     alu_output_value);
74             end // if
75         end // posedge clock
76     end // checking reset
77
78     // Iterate through the registers and assign values that we will read
79     later
80     for(regidx = 0; regidx < NUM_REGISTERS; regidx = regidx + 1) begin
81         // On the negative edge of the clock, set up the inputs
82         @(negedge clock) begin
83             write_data = 1'b0;
84             read_data = 1'b1; // The registers will now be reading data in
85             data_bus_driven = 1'b1; // And we will be driving the data bus
86             data_bus_driver = regidx + 10; // Store a unique nonzero value for
87                 each register
88             input_select = regidx;
89             output_select = (regidx + 1) % NUM_REGISTERS; // Read out a different
90                 register than
91             alu_output_select = (regidx + 1) % NUM_REGISTERS; // the one we are
92                 writing to
93         end
94         // On the positive edge, read the output and check it
95         @(posedge clock) begin
96             #30; // Wait for the value to change - is there a better way?
97             // BUG: This will fail on the last loop
98             //if(data_bus != 8'hzz || alu_output_value != 8'h00) begin
99             //    $display("Register %d not writing properly! Output is %d/%d",
100                 regidx, data_bus, alu_output_value);
101             //end // if
102         end // posedge clock
103     end // assigning test values
104
105     // Iterate through the registers and check that we can read the test
106     values out again

```

```

101   for(regidx = 0; regidx < NUM_REGISTERS; regidx = regidx + 1) begin
102       // On the negative edge of the clock, request the value out both ports
103       @(negedge clock) begin
104           write_data = 1'b1; // The registers will be writing data out to the
105                               bus
106           read_data = 1'b0;
107           data_bus_driven = 1'b0; // The registers will be driving the bus
108           output_select = regidx;
109           alu_output_select = regidx;
110       end
111       // On the positive edge, read the output and check it
112       @(posedge clock) begin
113           #30; // Wait for the value to change - is there a better way?
114           if(data_bus != regidx + 10 || alu_output_value != regidx + 10) begin
115               $display("Register_%d_failed!_Expected_%d,_got_%d_and_%d", regidx,
116                       regidx + 10, data_bus, alu_output_value);
117           end // if
118       end // posedge clock
119   end // checking reset
120
121   @(negedge clock)
122   $finish;
123
124 end
125 endmodule

```

## B.6 Datapath

```

1  /* datapath_test.v
2  * Testbench for the arithmetic logic unit
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 6 October 2010
5  * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
6  */
7
8  // Expected clock frequency is ~10 MHz = 100ns
9  // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
10 `timescale 1 ns / 10 ps
11
12 `include "constants.v"
13
14 module datapath_test();
15
16     parameter NAME_LEN = 239; // Length of the string in bytes, minus one (30 *
17                                 8 - 1)
18
19     reg reset;
20     reg gp_read;
21     reg gp_write;
22     reg pc_increment;
23     reg pc_set;
24     reg[2:0] gp_input_select;
25     reg[2:0] gp_output_select;

```

```

25  reg[2:0] gp_alu_output_select;
26  reg[3:0] alu_operation;
27  reg latch_alu;
28  reg alu_store_high;
29  reg alu_store_low;
30  reg mar_set_high;
31  reg mar_set_low;
32  reg ir_set_high;
33  reg ir_set_low;
34  reg jr_set_high;
35  reg jr_set_low;
36
37  wire[15:0] pc_count; // Program counter output
38  wire[15:0] mar_value; // Memory address register output
39  wire[15:0] ir_value; // Instruction register output
40  wire[2:0] alu_flags; // ALU flags
41
42  /* Data bus
43   * Because the data bus is a bidirectional port, we can't treat it as a wire
44   * (which must have continuous assignment) or a reg (which can't be
45   * continuously
46   * assigned). We have to create a reg which holds the value, and then use
47   * an
48   * assign statement to pick what we want. */
49  reg[7:0] data_bus_driver; // Holds the value we want to put onto the bus
50  reg data_bus_input; // When true, the data bus reads from data_bus_driver,
51  // when false, it's an output
52  wire[7:0] data_bus; // Wire connected to the DUT
53
54  assign data_bus = data_bus_input ? data_bus_driver : 8'hzz;
55
56  // Testbench variables
57  integer regIdx; // Index variable for the general purpose registers
58  reg[NAME_LEN:0] testName; // Holds the printed name for some tests
59
60  // Clock
61  reg clock = 0;
62  always #50 clock = !clock; // 100 time ticks per cycle = 10 MHz clock
63
64  // DUT
65  datapath dp(
66      .clock(clock),
67      .reset(reset),
68      .pc_increment(pc_increment),
69      .pc_set(pc_set),
70      .gp_read(gp_read),
71      .gp_write(gp_write),
72      .gp_input_select(gp_input_select),
73      .gp_output_select(gp_output_select),
74      .gp_alu_output_select(gp_alu_output_select),
75      .alu_operation(alu_operation),
76      .latch_alu(latch_alu),
77      .alu_store_high(alu_store_high),
78      .alu_store_low(alu_store_low),

```



```

76         .mar_set_high(mar_set_high),
77         .mar_set_low(mar_set_low),
78         .ir_set_high(ir_set_high),
79         .ir_set_low(ir_set_low),
80         .jr_set_high(jr_set_high),
81         .jr_set_low(jr_set_low),
82         .pc_count(pc_count),
83         .mar_value(mar_value),
84         .ir_value(ir_value),
85         .flags(alu_flags),
86         .data_bus(data_bus));
87
88 // Waveform log file and monitoring
89 initial begin
90     $dumpfile("datapath.vcd");
91     $dumpvars;
92     $monitor();
93 end
94
95 // Beginning of the test
96 initial begin
97     // Reset
98     @(negedge clock)
99     resetSignals();
100    reset = 1'b0;
101    @(posedge clock) #5
102    check16("Program_counter_reset", pc_count, 16'b0, __LINE__);
103    check16("MAR_reset", mar_value, 16'b0, __LINE__);
104    check16("Instruction_register_reset", ir_value, 16'b0, __LINE__);
105
106    // Load instruction register from the data bus
107    @(negedge clock)
108    resetSignals();
109    data_bus_driver = 8'h0ef;
110    data_bus_input = 1'b1;
111    ir_set_low = 1'b1;
112    @(posedge clock) #5
113    check16("Instruction_register_load_low", ir_value, 16'h00ef, __LINE__);
114    @(negedge clock)
115    resetSignals();
116    data_bus_driver = 8'hbe;
117    data_bus_input = 1'b1;
118    ir_set_high = 1'b1;
119    @(posedge clock) #5
120    check16("Instruction_register_load_high", ir_value, 16'hbeef, __LINE__);
121
122    // Load the jump register from the data bus
123    // The jump register doesn't have an output except to the program counter
124    @(negedge clock)
125    resetSignals();
126    data_bus_driver = 8'hce;
127    data_bus_input = 1'b1;
128    jr_set_low = 1'b1;
129    @(negedge clock)

```

```

130     resetSignals();
131     data_bus_driver = 8'hfa;
132     data_bus_input = 1'b1;
133     jr_set_high = 1'b1;
134     // Put the jump register value into the program counter and check it
135     @(negedge clock)
136         resetSignals();
137         pc_set = 1'b1;
138     @(posedge clock) #5
139         check16("Jump_register", pc_count, 16'hface, __LINE__);
140
141     // Increment the program counter
142     @(negedge clock)
143         resetSignals();
144         pc_increment = 1'b1;
145     @(posedge clock) #5
146         check16("Program_counter_increment", pc_count, 16'hfacf, __LINE__);
147
148     // Load each general purpose register from the data bus
149     resetSignals();
150     for(regIdx = 0; regIdx < 8; regIdx = regIdx + 1) begin
151         @(negedge clock)
152             data_bus_driver = regIdx; // Load each register with its index
153             data_bus_input = 1'b1; // We are driving the data bus
154             gp_input_select = regIdx; // regIdx will never be more than 7, so this
                is safe
155             gp_read = 1'b1; // Read from the data bus into the register
156     end
157
158     // Put each general purpose register back on the data bus and check it
159     for(regIdx = 0; regIdx < 8; regIdx = regIdx + 1) begin
160         @(negedge clock)
161             resetSignals();
162             gp_output_select = regIdx;
163             gp_write = 1'b1;
164         @(posedge clock) #5
165             $sformat(testName, "General-purpose_reg_#%1d", regIdx);
166             checkDatabus(testName, regIdx, __LINE__);
167     end
168
169     // Load memory address register from the data bus
170     @(negedge clock)
171         resetSignals();
172         data_bus_driver = 8'had;
173         data_bus_input = 1'b1;
174         mar_set_low = 1'b1;
175     @(posedge clock) #5
176         check16("MAR_load_low", mar_value, 16'h00ad, __LINE__);
177     @(negedge clock)
178         resetSignals();
179         data_bus_driver = 8'hde;
180         data_bus_input = 1'b1;
181         mar_set_high = 1'b1;
182     @(posedge clock) #5

```

```

183     check16("MAR_load_high", mar_value, 16'hdead, __LINE__);
184
185     // Load memory address register from the GP registers
186     // This loads the high byte and then the low byte, to ensure that that
187     // works just
188     // as well as loading low and then high.
189     // This code assumes that the register values are equal to their addresses
190     @(negedge clock)
191     resetSignals();
192     gp_output_select = 3'h4;
193     gp_write = 1'b1;
194     mar_set_high = 1'b1;
195     @(negedge clock)
196     resetSignals();
197     gp_output_select = 3'h5;
198     gp_write = 1'b1;
199     mar_set_low = 1'b1;
200     @(posedge clock) #5
201     check16("MAR_load_from_GPR", mar_value, 16'h0405, __LINE__);
202
203     // Perform 2-operand ALU operation using GP registers
204     // Add registers 5 and 6, and check that the result is 11
205     @(negedge clock)
206     resetSignals();
207     gp_alu_output_select = 3'h6; // Register 6 directly to ALU
208     gp_output_select = 3'h5; // Register 5 on data bus
209     gp_write = 1'b1;
210     alu_operation = 'ALU_ADD;
211     latch_alu = 1'b1; // Latch this result so we can put it on the data bus
212     // There's no way to see the ALU output except to put it on the data bus,
213     // so that's what we do next.
214     @(negedge clock)
215     resetSignals();
216     alu_store_low = 1'b1;
217     @(posedge clock)
218     checkDatabus("ALU_binary_from_GP", 8'd11, __LINE__);
219
220     // Perform 2-operand ALU operation using an immediate
221     // Multiply 6 by 100 and check that the result is 0x0258 (600)
222     @(negedge clock)
223     resetSignals();
224     gp_alu_output_select = 3'h6; // Register 6 directly to ALU
225     data_bus_driver = 8'd100; // Immediate value of 100
226     data_bus_input = 1'b1;
227     alu_operation = 'ALU_MULTIPLY;
228     latch_alu = 1'b1; // Latch this result so we can put it on the data bus
229     @(negedge clock)
230     resetSignals();
231     alu_store_high = 1'b1;
232     @(negedge clock)
233     checkDatabus("ALU_binary_with_immediate_high", 8'h02, __LINE__);
234     @(negedge clock)
235     resetSignals();
236     alu_store_low = 1'b1;

```

```

236   @(posedge clock)
237   checkDatabus("ALU_binary_with_immediate_low", 8'h58, __LINE__);
238
239
240   // Perform 1-operand ALU operation using GP register
241   // Invert register 1 to get 0b11111110 (0xFE)
242   @(negedge clock)
243   resetSignals();
244   gp_alu_output_select = 3'h1; // Register 6 directly to ALU
245   alu_operation = 'ALU_COMPLEMENT;
246   latch_alu = 1'b1; // Latch this result so we can put it on the data bus
247   @(negedge clock)
248   resetSignals();
249   alu_store_low = 1'b1;
250   @(posedge clock)
251   checkDatabus("ALU_unary_from_GP", 8'hfe, __LINE__);
252
253   // Perform ALU passthrough
254   // Copy the value 125 into the ALU latch and write it back out to the
      databus
255   @(negedge clock)
256   resetSignals();
257   data_bus_driver = 8'd125;
258   data_bus_input = 1'b1;
259   alu_operation = 'ALU_PASSTHROUGH;
260   latch_alu = 1'b1; // Latch this result so we can put it on the data bus
261   @(negedge clock)
262   resetSignals();
263   alu_store_low = 1'b1;
264   @(negedge clock)
265   checkDatabus("ALU_passthrough", 8'd125, __LINE__);
266
267
268
269   @(negedge clock)
270   $finish;
271 end // End of the test
272
273 // Sets all of the signals to their inactive state.
274 task resetSignals();
275 begin
276     reset = 1;
277     data_bus_input = 1'b0;
278     pc_increment = 1'b0;
279     pc_set = 1'b0;
280     gp_read = 0;
281     gp_write = 0;
282     gp_input_select = 0;
283     gp_output_select = 0;
284     gp_alu_output_select = 0;
285     alu_operation = 0;
286     latch_alu = 1'b0;
287     alu_store_high = 1'b0;
288     alu_store_low = 1'b0;

```

```

289     mar_set_high = 0;
290     mar_set_low = 0;
291     ir_set_high = 0;
292     ir_set_low = 0;
293     jr_set_high = 0;
294     jr_set_low = 0;
295 end
296 endtask
297
298 task check16(input [NAME_LEN:0] name, input [15:0] value, input [15:0] expected
    , input integer lineNum);
299 begin
300     if(value === expected) begin
301         $display("%3d_ Test_passed: %s", lineNum, name);
302     end
303     else begin
304         $display("%3d_ Test_failed, expected %h, got %h: %s", lineNum,
            expected, value, name);
305     end
306 end
307 endtask
308
309 task checkDatabus(input [NAME_LEN:0] name, input [7:0] expected, input
    integer lineNum);
310 begin
311     if(data_bus === expected) begin
312         $display("%3d_ Test_passed: %s", lineNum, name);
313     end
314     else begin
315         $display("%3d_ Test_failed, expected %h, got %h: %s", lineNum,
            expected, data_bus, name);
316     end
317 end
318 endtask
319
320 endmodule

```

## B.7 Control module state machine

```

1  /* control_test.v
2  * Testbench for the control module. This code uses an external text file,
3  * control_vectors, which contains a series of control module states and
    opcodes
4  * where necessary. After performing a reset, the code reads a line from the
5  * file, executes a clock cycle, and checks that the control module entered
    the
6  * specified state.
7  * This code does not check that the state vectors are outputted properly. It
    only
8  * checks that the state sequence is correct.
9  * Author: Steven Bell <steven.bell@student.oc.edu>
10 * Date: 23 November 2010
11 * $LastChangedDate: 2010-12-13 18:04:13 -0600 (Mon, 13 Dec 2010) $
12 */

```

```

13
14 // Expected clock frequency is ~10 MHz = 100ns
15 // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
16 `timescale 1 ns / 10 ps
17
18 module control_test();
19     parameter STRING_LEN = 239; // Maximum length of the strings we read in bits
        (minus one)
20     reg reset = 1; // Reset signal for the part
21     reg[15:0] instruction_register; // Dummy instruction register which we load
        from the file
22
23     wire[4:0] control_state; // Current state of the control module
24
25     // Clock
26     reg clock = 0;
27     always #50 clock = ~clock;
28
29     // DUT
30     control controlDUT(.clock(clock),
31                        .reset(reset),
32                        .instruction(instruction_register),
33                        .state(control_state));
34
35     // Logging
36     initial begin
37         $dumpfile("control.vcd");
38         $dumpvars(); // Dump everything
39     end
40
41     // Variables for reading the file
42     integer file;
43     integer r; // Result from scanf; required by verilog spec, but not used
44     reg[STRING_LEN:0] stateString;
45     reg[7:0] opcodeByte;
46
47
48     // Beginning of test
49     initial begin
50         // Perform reset
51         @(negedge clock)
52         reset = 1'b0;
53         @(negedge clock)
54         reset = 1'b1;
55
56         // Start reading the file
57         file = $fopen("control_vectors", "r");
58
59         // Loop until we get to the end of the file
60         while(!$feof(file)) begin
61             // Read a line with a desired state
62             r = $fscanf(file, "%s", stateString);
63             while(isComment(stateString)) begin // Keep reading and printing
                comments until we get an instruction

```

```

64     $display("%s", stateString);
65     r = $fscanf(file, "%s", stateString);
66     end
67
68     // On the rising edge of the clock, the module should be in that state
69     @(posedge clock) #5
70     testOpcode(stateString, control_state);
71
72     // If the state is a fetch, then read the opcode byte from the file and
73     // set the instruction register appropriately
74     if(stateString == "FETCH_1") begin
75         r = $fscanf(file, "%2h", opcodeByte);
76         instruction_register[15:8] = opcodeByte;
77     end
78     else if(stateString == "FETCH_2") begin
79         r = $fscanf(file, "%2h", opcodeByte);
80         instruction_register[7:0] = opcodeByte;
81     end
82
83     end
84
85
86     // How do we test jumps??
87
88     // End of the test
89     $display("Test_completed_successfully!");
90     $finish;
91 end
92
93 /* Compares a state string (e.g, "FETCH_2") to a state number (e.g, 2) to
94  * see if they match.  If so, it prints the state string.  If not, it prints
95  * an error message and quits the simulation */
96 task testOpcode(input [20*8-1:0] string, input [4:0] state);
97     reg [4:0] desiredState; // State value determined from the string
98     begin
99
100         case(string)
101             "RESET":
102                 desiredState = `S_RESET;
103             "FETCH_1":
104                 desiredState = `S_FETCH_1;
105             "FETCH_2":
106                 desiredState = `S_FETCH_2;
107             "ALU_OPERATION":
108                 desiredState = `S_ALU_OPERATION;
109             "ALU_IMMEDIATE":
110                 desiredState = `S_ALU_IMMEDIATE;
111             "STORE_RESULT_1":
112                 desiredState = `S_STORE_RESULT_1;
113             "STORE_RESULT_2":
114                 desiredState = `S_STORE_RESULT_2;
115             "FETCH_IMMEDIATE":
116                 desiredState = `S_FETCH_IMMEDIATE;
117             "COPY_REGISTER":

```

```

118     desiredState = `S_COPY_REGISTER;
119     "FETCH_ADDRESS_1":
120     desiredState = `S_FETCH_ADDRESS_1;
121     "FETCH_ADDRESS_2":
122     desiredState = `S_FETCH_ADDRESS_2;
123     "FETCH_MEMORY":
124     desiredState = `S_FETCH_MEMORY;
125     "STORE_MEMORY":
126     desiredState = `S_STORE_MEMORY;
127     "TEMP_FETCH":
128     desiredState = `S_TEMP_FETCH;
129     "FETCH_ADDRESS_3":
130     desiredState = `S_FETCH_ADDRESS_3;
131     "FETCH_ADDRESS_4":
132     desiredState = `S_FETCH_ADDRESS_4;
133     "TEMP_STORE":
134     desiredState = `S_TEMP_STORE;
135     "LOAD_JUMP_1":
136     desiredState = `S_LOAD_JUMP_1;
137     "LOAD_JUMP_2":
138     desiredState = `S_LOAD_JUMP_2;
139     "EXECUTE_JUMP":
140     desiredState = `S_EXECUTE_JUMP;
141     "HALT":
142     desiredState = `S_HALT;
143     default:
144     desiredState = 5'b00000;
145 endcase
146
147 if(state == desiredState) begin
148     $display("%h,%s", instruction_register, string);
149 end
150 else begin
151     $display("Test_failed!_Expected_state_%s,_but_got_%d", string, state);
152     $display("Instruction_register_contained_%h_at_failure",
153         instruction_register);
154     $finish; // quit the simulation
155 end
156 endtask
157
158 function isComment(input[STRING_LEN:0] str);
159 begin
160     if(str[7:0] == "#") begin
161         isComment = 1'b1;
162     end
163     else begin
164         isComment = 1'b0;
165     end
166 end
167 endfunction
168
169
170 endmodule

```



## B.8 Control signals translator

```

1  /* control_signals_test.v Testbench for control signals module, which
2  * translates the control module state into the vector of control signals.
3  * Author: Steven Bell <steven.bell@student.oc.edu>
4  * Date: 2 December 2010
5  * $LastChangedDate$
6  */
7
8  // Expected clock frequency is ~10 MHz = 100ns
9  // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
10 `timescale 1 ns / 10 ps
11
12 // Need to see if there's something like C's #ifndef for headers
13 //`include "constants.vh"
14
15 module control_signals_test();
16     // Inputs to the DUT
17     reg[4:0] state;
18     reg[15:0] opcode;
19     reg[2:0] alu_flags;
20
21     // Outputs from the DUT
22     wire ir_load_high;
23     wire ir_load_low;
24     wire gp_read;
25     wire gp_write;
26     wire pc_set;
27     wire pc_increment;
28     wire mem_read;
29     wire mem_write;
30     wire latch_alu;
31     wire alu_store_high;
32     wire alu_store_low;
33     wire jr_load_high;
34     wire jr_load_low;
35     wire mar_load_high;
36     wire mar_load_low;
37     wire[3:0] alu_operation;
38     wire[2:0] gp_input_select;
39     wire[2:0] gp_output_select;
40     wire[2:0] gp_alu_output_select;
41
42     // Variables representing the desired values for the outputs
43     reg d_ir_load_high;
44     reg d_ir_load_low;
45     reg d_gp_primary_addr;
46     reg d_gp_alu_addr;
47     reg d_gp_read;
48     reg d_gp_write;
49     reg d_pc_set;
50     reg d_pc_increment;
51     reg d_mem_read;
52     reg d_mem_write;

```

```

53  reg d_latch_alu;
54  reg d_alu_store_high;
55  reg d_alu_store_low;
56  reg d_jr_load_high;
57  reg d_jr_load_low;
58  reg d_mar_load_high;
59  reg d_mar_load_low;
60  reg[3:0] d_alu_operation;
61  reg[2:0] d_gp_input_select;
62  reg[2:0] d_gp_output_select;
63  reg[2:0] d_gp_alu_output_select;
64
65  // Variables for module tasks
66  reg passed = 1'b1;
67
68  // DUT
69  control_signals csDUT(.state(state),
70                      .opcode(opcode),
71                      .alu_flags(alu_flags),
72                      .ir_load_high(ir_load_high),
73                      .ir_load_low(ir_load_low),
74                      .gp_read(gp_read),
75                      .gp_write(gp_write),
76                      .pc_set(pc_set),
77                      .pc_increment(pc_increment),
78                      .mem_read(mem_read),
79                      .mem_write(mem_write),
80                      .latch_alu(latch_alu),
81                      .alu_store_high(alu_store_high),
82                      .alu_store_low(alu_store_low),
83                      .jr_load_high(jr_load_high),
84                      .jr_load_low(jr_load_low),
85                      .mar_load_high(mar_load_high),
86                      .mar_load_low(mar_load_low),
87                      .alu_operation(alu_operation),
88                      .gp_input_select(gp_input_select),
89                      .gp_output_select(gp_output_select),
90                      .gp_alu_output_select(gp_alu_output_select));
91
92  // Monitoring and dumpfile
93  initial begin
94      $dumpfile("control_signals.vcd");
95      $dumpvars; // Dump everything
96  end
97
98  // Beginning of test
99  initial begin
100     // Reset
101     state = `S_RESET;
102     opcode = 16'hbeef;
103     zeroDesired();
104
105     checkSignals(__LINE__);
106

```

```
107
108 // Fetch 1
109 state = `S_FETCH_1;
110 opcode = 16'hface;
111 zeroDesired();
112 d_ir_load_high = 1;
113 d_mem_read = 1;
114 d_pc_increment = 1;
115
116 checkSignals(__LINE__);
117
118
119 // Fetch 2
120 state = `S_FETCH_2;
121 opcode = 16'hface;
122 zeroDesired();
123 d_ir_load_low = 1;
124 d_mem_read = 1;
125 d_pc_increment = 1;
126
127 checkSignals(__LINE__);
128
129
130 // ALU operation with immediate, no write from register
131 state = `S_ALU_OPERATION;
132 opcode = 16'h0c00;
133 zeroDesired();
134 d_latch_alu = 1;
135
136 checkSignals(__LINE__);
137
138
139 // ALU operation with two registers
140 state = `S_ALU_OPERATION;
141 opcode = 16'h0800;
142 zeroDesired();
143 d_gp_write = 1;
144 d_latch_alu = 1;
145
146 checkSignals(__LINE__);
147
148
149 // Store result
150 state = `S_STORE_RESULT_1;
151 opcode = 16'h0c00;
152 zeroDesired();
153 d_gp_read = 1;
154 d_alu_store_low = 1;
155
156 checkSignals(__LINE__);
157
158
159 // Store a multiply
160 state = `S_STORE_RESULT_1;
```

```
161 opcode = 16'h1820;
162 zeroDesired();
163 d_gp_read = 1;
164 d_alu_store_high = 1;
165 checkSignals(__LINE__);
166
167 // Store the second half of the multiply
168 state = `S_STORE_RESULT_2;
169 opcode = 16'h1820;
170 zeroDesired();
171 d_gp_read = 1;
172 d_alu_store_low = 1;
173 checkSignals(__LINE__);
174
175 // Do a copy
176 state = `S_COPY_REGISTER;
177 opcode = 16'h0000;
178 zeroDesired();
179 d_gp_read = 1;
180 d_gp_write = 1;
181 checkSignals(__LINE__);
182
183 // Do an address fetch
184 state = `S_FETCH_ADDRESS_1;
185 opcode = 16'h0000;
186 zeroDesired();
187 d_pc_increment = 1;
188 d_mem_read = 1;
189 d_mar_load_high = 1;
190 checkSignals(__LINE__);
191
192 state = `S_FETCH_ADDRESS_2;
193 opcode = 16'h0000;
194 zeroDesired();
195 d_pc_increment = 1;
196 d_mem_read = 1;
197 d_mar_load_low = 1;
198 checkSignals(__LINE__);
199
200 // Memory fetch
201 state = `S_FETCH_MEMORY;
202 opcode = 16'h0000;
203 zeroDesired();
204 d_gp_read = 1;
205 d_mem_read = 1;
206 checkSignals(__LINE__);
207
208 // Memory store
209 state = `S_STORE_MEMORY;
210 opcode = 16'h0000;
211 zeroDesired();
212 d_gp_write = 1;
213 d_mem_write = 1;
214 checkSignals(__LINE__);
```

```
215
216 // Do a move starting with the temp fetch
217 state = `S_TEMP_FETCH;
218 opcode = 16'h9000;
219 zeroDesired();
220 d_latch_alu = 1;
221 d_mem_read = 1;
222 checkSignals(__LINE__);
223
224 // Continue move; get the destination address
225 state = `S_FETCH_ADDRESS_3;
226 opcode = 16'h9000;
227 zeroDesired();
228 d_pc_increment = 1;
229 d_mem_read = 1;
230 d_mar_load_high = 1;
231 checkSignals(__LINE__);
232
233 state = `S_FETCH_ADDRESS_4;
234 opcode = 16'h9000;
235 zeroDesired();
236 d_pc_increment = 1;
237 d_mem_read = 1;
238 d_mar_load_low = 1;
239 checkSignals(__LINE__);
240
241 // Do the temp store
242 state = `S_TEMP_STORE;
243 opcode = 16'h9000;
244 zeroDesired();
245 d_alu_store_low = 1;
246 d_mem_write = 1;
247 checkSignals(__LINE__);
248
249 // Load the jump register
250 state = `S_LOAD_JUMP_1;
251 opcode = 16'h7800;
252 zeroDesired();
253 d_pc_increment = 1;
254 d_mem_read = 1;
255 d_jr_load_high = 1;
256 checkSignals(__LINE__);
257
258 state = `S_LOAD_JUMP_2;
259 opcode = 16'h7800;
260 zeroDesired();
261 d_pc_increment = 1;
262 d_mem_read = 1;
263 d_jr_load_low = 1;
264 checkSignals(__LINE__);
265
266 // Test jump always
267 state = `S_EXECUTE_JUMP;
268 opcode = 16'h7800;
```

```
269     zeroDesired();
270     d_pc_set = 1;
271     checkSignals(__LINE__);
272
273     // Test jump if carry - don't jump
274     state = `S_EXECUTE_JUMP;
275     opcode = 16'h7801;
276     alu_flags = 3'b000;
277     zeroDesired();
278     d_pc_set = 0;
279     checkSignals(__LINE__);
280
281     // Jump if carry - do jump
282     state = `S_EXECUTE_JUMP;
283     opcode = 16'h7801;
284     alu_flags = 3'b010;
285     zeroDesired();
286     d_pc_set = 1;
287     checkSignals(__LINE__);
288
289     // Test jump if zero - don't jump
290     state = `S_EXECUTE_JUMP;
291     opcode = 16'h7802;
292     alu_flags = 3'b000;
293     zeroDesired();
294     d_pc_set = 0;
295     checkSignals(__LINE__);
296
297     // Jump if zero - do jump
298     state = `S_EXECUTE_JUMP;
299     opcode = 16'h7802;
300     alu_flags = 3'b100;
301     zeroDesired();
302     d_pc_set = 1;
303     checkSignals(__LINE__);
304
305     // Test jump if negative - don't jump
306     state = `S_EXECUTE_JUMP;
307     opcode = 16'h7803;
308     alu_flags = 3'b000;
309     zeroDesired();
310     d_pc_set = 0;
311     checkSignals(__LINE__);
312
313     // Jump if negative - do jump
314     state = `S_EXECUTE_JUMP;
315     opcode = 16'h7803;
316     alu_flags = 3'b001;
317     zeroDesired();
318     d_pc_set = 1;
319     checkSignals(__LINE__);
320
321
322     // Check halt
```

```

323     state = `HALT;
324     opcode = 16'hff00;
325     zeroDesired();
326     checkSignals(__LINE__);
327
328
329
330
331
332
333     $finish;
334 end
335
336 task checkSignals(input integer lineNum);
337 begin
338     #100
339     if(ir_load_high != d_ir_load_high) begin
340         $display("%4d:_IR_high_test_failed;_expected_%h_but_got_%h", lineNum,
341             d_ir_load_high, ir_load_high);
342         passed = 1'b0;
343     end
344     if(ir_load_low != d_ir_load_low) begin
345         $display("%4d:_IR_low_test_failed;_expected_%h_but_got_%h", lineNum,
346             d_ir_load_low, ir_load_low);
347         passed = 1'b0;
348     end
349     if(gp_read != d_gp_read) begin
350         $display("%4d:_GP_read_test_failed;_expected_%h_but_got_%h", lineNum,
351             d_gp_read, gp_read);
352         passed = 1'b0;
353     end
354     if(gp_write != d_gp_write) begin
355         $display("%4d:_GP_write_test_failed;_expected_%h_but_got_%h", lineNum,
356             d_gp_write, gp_write);
357         passed = 1'b0;
358     end
359     if(pc_set != d_pc_set) begin
360         $display("%4d:_PC_set_test_failed;_expected_%h_but_got_%h", lineNum,
361             d_pc_set, pc_set);
362         passed = 1'b0;
363     end
364     if(pc_increment != d_pc_increment) begin
365         $display("%4d:_PC_increment_test_failed;_expected_%h_but_got_%h",
366             lineNum, d_pc_increment, pc_increment);
367         passed = 1'b0;
368     end
369     if(mem_read != d_mem_read) begin
370         $display("%4d:_Memory_read_test_failed;_expected_%h_but_got_%h",
371             lineNum, d_mem_read, mem_read);
372         passed = 1'b0;
373     end
374     if(mem_write != d_mem_write) begin
375         $display("%4d:_Memory_write_test_failed;_expected_%h_but_got_%h",
376             lineNum, d_mem_write, mem_write);

```

```

369     passed = 1'b0;
370 end
371 if(latch_alu != d_latch_alu) begin
372     $display("%4d:_ALU_latch_test_failed;_expected_%h_but_got_%h", lineNum,
373             d_latch_alu, latch_alu);
374     passed = 1'b0;
375 end
376 if(alu_store_high != d_alu_store_high) begin
377     $display("%4d:_ALU_store_high_test_failed;_expected_%h_but_got_%h",
378             lineNum, d_alu_store_high, alu_store_high);
379     passed = 1'b0;
380 end
381 if(alu_store_low != d_alu_store_low) begin
382     $display("%4d:_ALU_store_low_test_failed;_expected_%h_but_got_%h",
383             lineNum, d_alu_store_low, alu_store_low);
384     passed = 1'b0;
385 end
386 if(jr_load_high != d_jr_load_high) begin
387     $display("%4d:_JR_high_test_failed;_expected_%h_but_got_%h", lineNum,
388             d_jr_load_high, jr_load_high);
389     passed = 1'b0;
390 end
391 if(ir_load_low != d_ir_load_low) begin
392     $display("%4d:_JR_low_test_failed;_expected_%h_but_got_%h", lineNum,
393             d_jr_load_low, jr_load_low);
394     passed = 1'b0;
395 end
396 if(mar_load_high != d_mar_load_high) begin
397     $display("%4d:_MAR_high_test_failed;_expected_%h_but_got_%h", lineNum,
398             d_mar_load_high, mar_load_high);
399     passed = 1'b0;
400 end
401 if(mar_load_low != d_mar_load_low) begin
402     $display("%4d:_MAR_low_test_failed;_expected_%h_but_got_%h", lineNum,
403             d_mar_load_low, mar_load_low);
404     passed = 1'b0;
405 end
406 if(passed == 1'b1) begin
407     $display("%4d:_Test_passed", lineNum);
408 end
409 end
410 endtask
411
412 task zeroDesired();
413 begin
414     d_ir_load_high = 1'b0;
415     d_ir_load_low = 1'b0;
416     d_gp_primary_addr = 1'b0;
417     d_gp_alu_addr = 1'b0;
418     d_gp_read = 1'b0;
419     d_gp_write = 1'b0;
420     d_pc_set = 1'b0;

```



```

416     d_pc_increment = 1'b0;
417     d_mem_read = 1'b0;
418     d_mem_write = 1'b0;
419     d_latch_alu = 1'b0;
420     d_alu_store_high = 1'b0;
421     d_alu_store_low = 1'b0;
422     d_jr_load_high = 1'b0;
423     d_jr_load_low = 1'b0;
424     d_mar_load_high = 1'b0;
425     d_mar_load_low = 1'b0;
426     d_alu_operation = 4'd0;
427     d_gp_input_select = 3'd0;
428     d_gp_output_select = 3'd0;
429     d_gp_alu_output_select = 3'd0;
430 end
431 endtask
432
433
434 endmodule

```

## B.9 CPU

```

1  /* cpu_test.v Testbench for full CPU
2  * Author: Steven Bell <steven.bell@student.oc.edu>
3  * Date: 6 December 2010
4  * $LastChangedDate: 2010-12-16 17:48:32 -0600 (Thu, 16 Dec 2010) $
5  */
6
7  // Expected clock frequency is ~10 MHz = 100ns
8  // Tick freq is 1 GHz => 100 ticks is one clock cycle; resolution is 10 ps
9  `timescale 1 ns / 10 ps
10
11 module cpu_test();
12     parameter RAM_SIZE = 16; // Size of the RAM in bytes
13     parameter RAM_ADDRESS_BITS = 4; // How many address bits the RAM needs
14     parameter ROM_SIZE = 1024; // Size of the ROM in bytes
15     parameter ROM_ADDRESS_BITS = 10; // How many address bits the ROM needs
16     parameter MAX_LINE_LENGTH = 200; // Maximum length of line in input file
17
18     // Signals for DUT
19     reg reset;
20     reg[7:0] data_bus_driver; // Value from the memory to drive the bus
21     reg memory_drives_bus; // True if the memory is driving the data bus
22     wire[7:0] data_bus; // Bidirectional data bus
23     wire[15:0] address_bus; // Address bus coming out of the chip
24     wire ram_enable;
25     wire rom_enable;
26     wire write;
27
28     // Variables for file processing and simulation
29     integer clock_cycles; // Number of clock cycles we've stepped through
30     reg[7:0] rom[0:ROM_SIZE-1]; // Simulated EEPROM
31     reg[7:0] ram[0:RAM_SIZE-1]; // Simulated RAM
32     integer i; // Index for ROM

```

```

33 integer file; // File handle
34 integer c; // Test character for seeing if the a line begins with a comment
35 integer r; // Unused placeholder for return values from file parsing
36 reg[8*MAX_LINE_LENGTH:0] line; // Unused placeholder for string comments
    that get read
37
38 // Clock
39 reg clock = 0;
40 always #50 clock = ~clock;
41
42 // DUT
43 cpu cpuDUT(.clock(clock),
44             .reset(reset),
45             .external_data_bus(data_bus),
46             .address_bus(address_bus),
47             .ram_enable(ram_enable),
48             .rom_enable(rom_enable),
49             .write(write));
50
51 // Waveform log file
52 initial begin
53     $dumpfile("cpu.vcd");
54     $dumpvars;
55 end
56
57 // Bidirectional driver code for data bus
58 assign data_bus = memory_drives_bus ? data_bus_driver : 16'hzz;
59
60 // Beginning of test
61 initial begin
62     // Initialize ROM to all zeros
63     for(i = 0; i < ROM_SIZE; i = i + 1) begin
64         rom[i] = 8'd0;
65     end
66
67     $display("Loading_instructions_into_simulated_ROM_from_\\"cpu_code\\"");
68     // Start reading the file
69     file = $fopen("cpu_code", "r");
70
71     // Loop until we get to the end of the file and initialize ROM with the
        contents
72     i = 0; // Start back at the beginning of ROM
73     while(! $feof(file)) begin
74         // Check if the first character is a '#', signifying a comment
75         c = $fgetc(file);
76         if(c == "#") begin
77             // If we've got a comment, skip to the next line
78             r = $fgets(line, file);
79         end
80         else begin
81             // Otherwise, assume that it's a hex value and try to read it
82             r = $ungetc(c, file);
83             r = $fscanf(file, "%h\n", rom[i]);
84             i = i + 1;

```

```


85     end
86 end
87
88 // Test: print out the contents of ROM
89 for(i = 0; i < 20; i = i + 1) begin
90     $write("%h_", rom[i]);
91     if(i % 8 == 7) begin
92         $write("\n");
93     end
94 end
95
96 // Perform a reset
97 @(negedge clock)
98     reset = 1'b0;
99 @(negedge clock)
100    reset = 1'b1;
101
102 // And off we go!
103 for(clock_cycles = 0; clock_cycles < 500; clock_cycles = clock_cycles + 1)
104     begin
105         @(posedge clock)
106         memory_drives_bus = 1'b0; // Relinquish control of the data bus until we
107             're told to keep using it
108         #10 // Wait for the memory address to be set before we try to give back
109             data!
110         if(rom_enable == 1'b0) begin // ROM output-enable is active low
111             data_bus_driver = rom[address_bus];
112         end
113         else if(ram_enable == 1'b0) begin // RAM output-enable is also active
114             low
115             if(write == 1'b1) begin // CPU is writing to RAM
116                 ram[address_bus[RAM_ADDRESS_BITS-1:0]] = data_bus;
117             end
118             else begin // CPU is reading from RAM
119                 data_bus_driver = ram[address_bus[RAM_ADDRESS_BITS-1:0]];
120             end
121         end // if(rom/ram enable)
122         memory_drives_bus = !write;
123
124         // $display("%h %h", address_bus, data_bus);
125     end // for(clock_cycles)
126 $finish;
127 end // initial
128 endmodule

```

 
## C Output waveforms

Waveforms were created by dumping the signals to a VCD file directly from Verilog, converting them to Aldec's .abf file format using the Aldec command-line utilities `vcd2asdb` and `awfconv`, and viewing them in ActiveHDL's waveform viewer.



1. Generic 16-bit register .....	77
2. Program counter .....	78
3. ALU .....	79
4. ALU latch .....	81
5. General-purpose register block .....	82
6. Datapath .....	83
7. Control module state machine .....	86
8. Control signals translator .....	87
9. CPU final test, part A .....	89
10. CPU final test, part B .....	102



 



Program Counter









# ALU

Name	0	100	200	300	400	500	600	700	800	900	1000	1100	1200	1300	1400	ns
clock																
reset																
primaryOperand	XX00010001FF7DF1FA0A02															
secondaryOperand	XX0200FF020A060A0FFA															
operation	XC12															
result	XXXX0002000000FF00030101008700FB01000004000001FB0108															
flags	XXX000100001000010001110000100011010															

Name	1490	1590	1690	1790	1890	1990	2090	2190	2290	2390	2490	2590	2690	2790	2890	ns
clock																
reset																
primaryOperand	800A64FFF6AA2AA00AAAB002A															
secondaryOperand	01063CFF066655E66600FF															
operation	34567															
result	007F003C1770FE0105C40022000000A2006E00EE0000005500000054															
flags	000001000100001000000011000000101000															

Name	2980	3080	3180	3280	3380	3480	3580	3680	3780	3880	3980	4080	4180	4280	4380	ns
clock																
reset																
primaryOperand	AA00C02A2B00AA2AA6A00018032CE															
secondaryOperand																
operation	9AB															
result	00000080001500000055005400D40000FFFFFF80FFCEFF32															
flags	0101000110000101000001000110000000															

ALU

Name	4470	4570	4670	4770	4870	4970	5070	5170	5270	5370	5470	5570	5670	5770	5870	ns
clock																
reset																
primaryOperand																
secondaryOperand																
operation																
result																
flags																





# ALU Latch

Name	0	100	200	300	400	500	600	700	800	900	1000	1100	1200	1300	1400	ns
clock																
reset																
grab																
alu_result	XXXX BEEF DEAD FACE															
store_high																
store_low																
databus	XX ZZ BE EF															


Name	1490	1590	1690	1790	1890	1990	2090	2190	2290	2390	2490	2590	2690	2790	2890	ns
clock																
reset																
grab																
alu_result																
store_high																
store_low																
databus																

Name	2980	3080	3180	3280	3380	3480	3580	3680	3780	3880	3980	4080	4180	4280	4380	ns
clock																
reset																
grab																
alu_result																
store_high																
store_low																
databus																


# General purpose registers

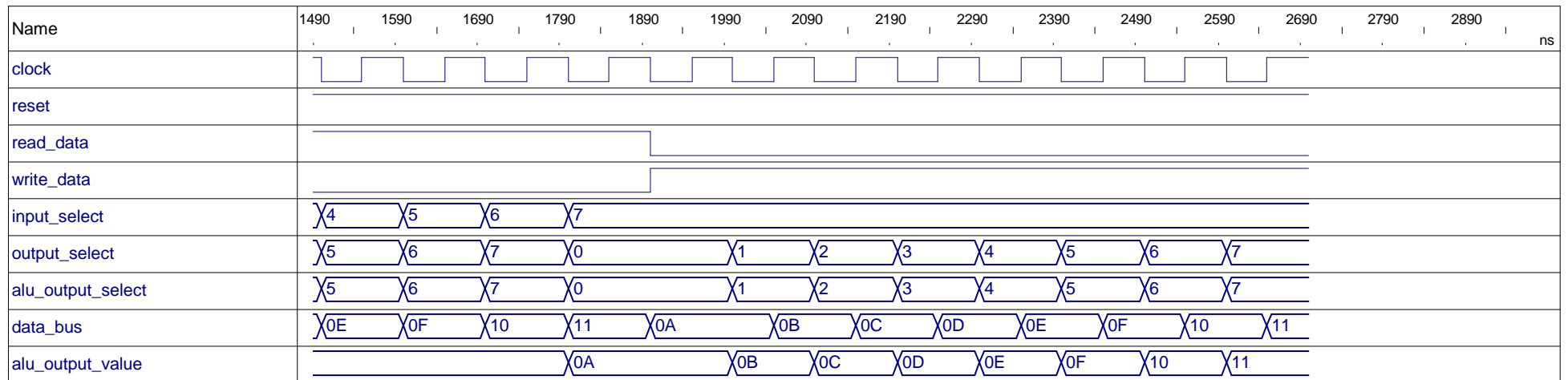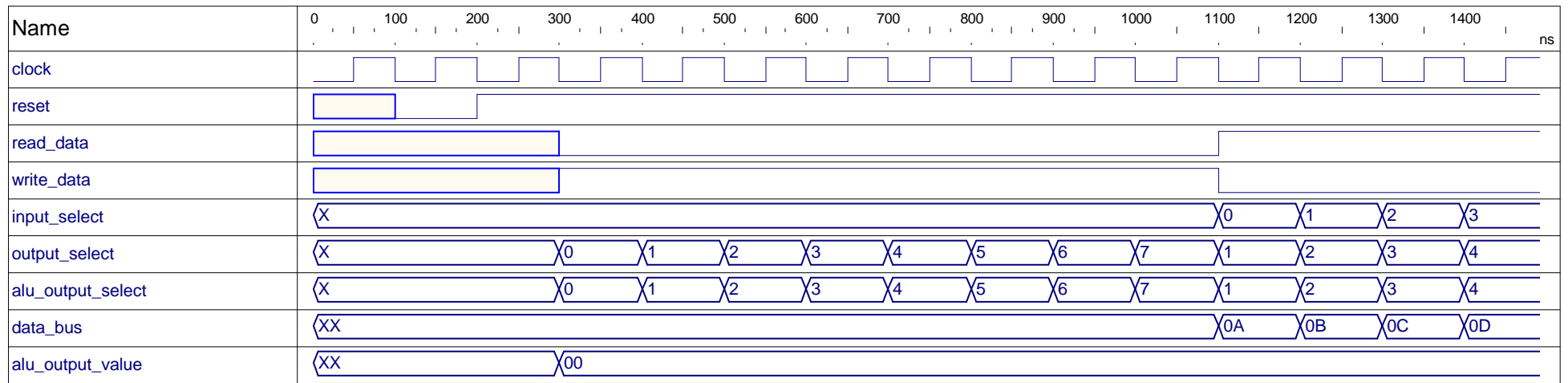


## Datapath

 





## Datapath

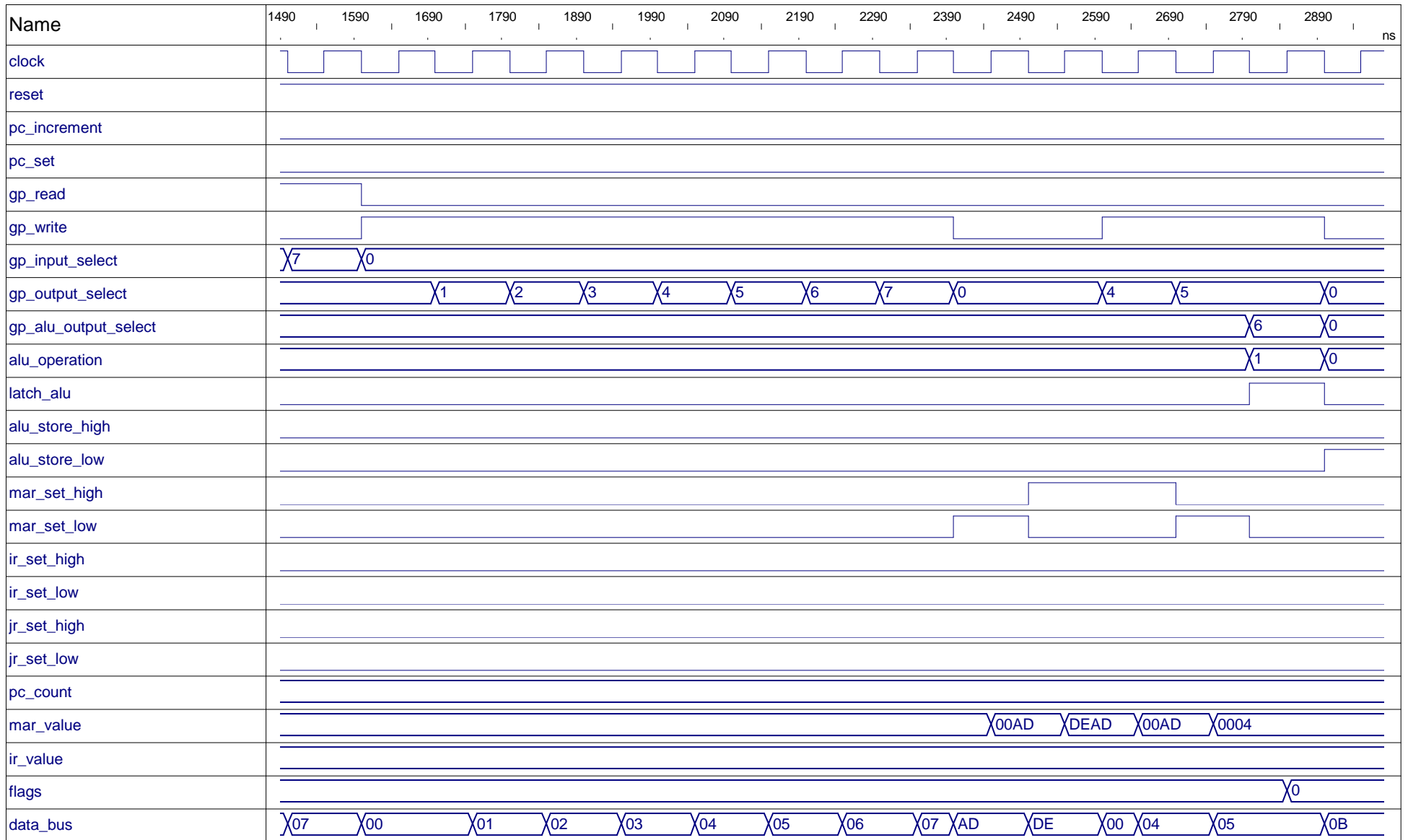


## Datapath

 

# Control state machine

    

# Control signal translator


 


# Control signal translator



Name	1490	1590	1690	1790	1890	1990	2090	2190	2290	2390	2490	2590	2690	2790	2890	ns
state	X0F	X10	X11	X12	X13	X14									X1F	
opcode						7800		7801		7802		7803		FF00		
alu_flags							0	2	0	4	0	1				
ir_load_high																
ir_load_low																
gp_read																
gp_write																
pc_set																
pc_increment																
mem_read																
mem_write																
latch_alu																
alu_store_high																
alu_store_low																
jr_load_high																
jr_load_low																
mar_load_high																
mar_load_low																
alu_operation																
gp_input_select																
gp_output_select																
gp_alu_output_select																





# CPU test program, part A

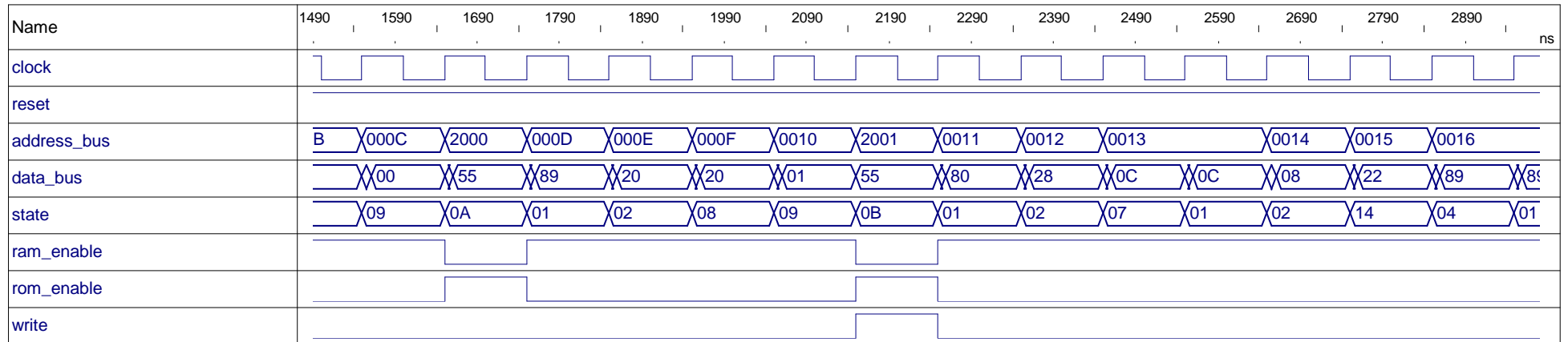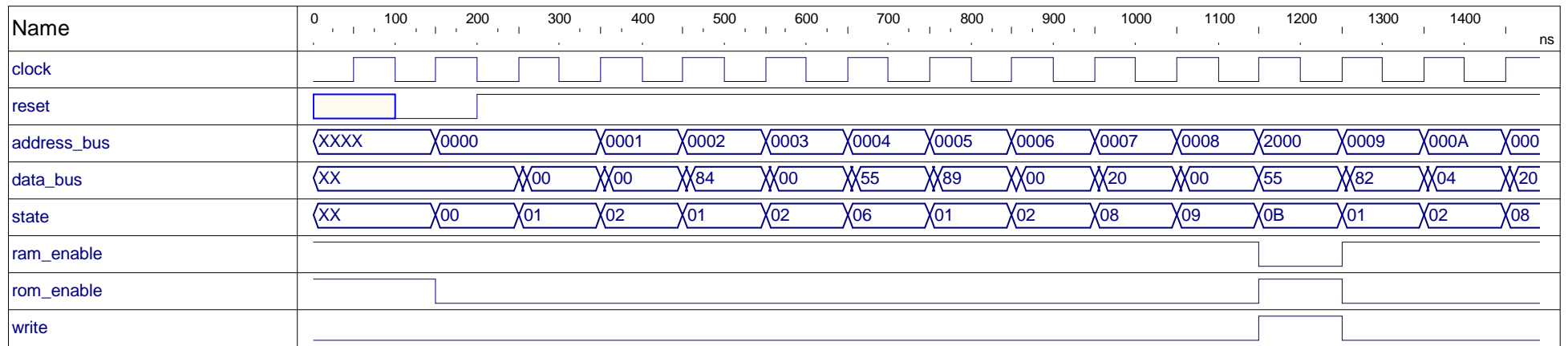



# CPU test program, part A

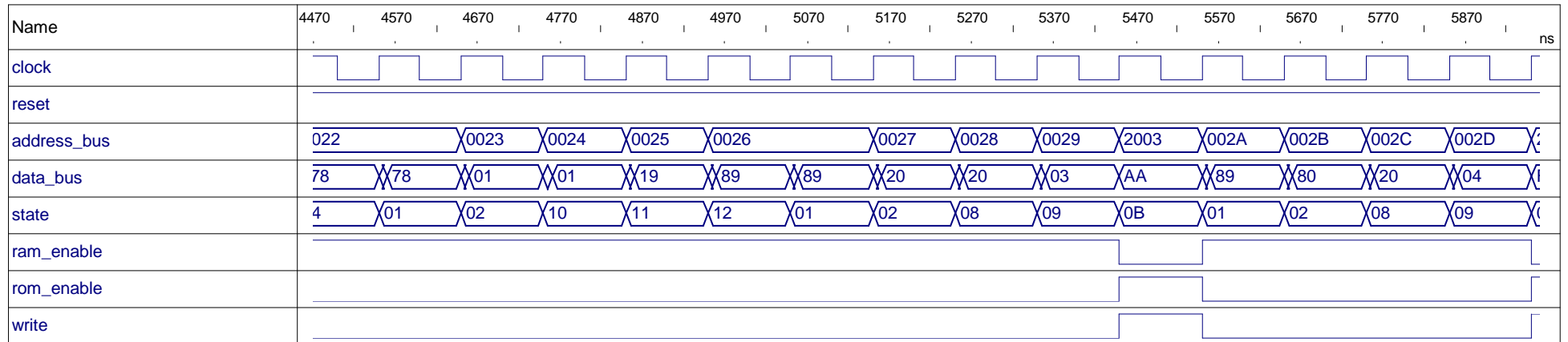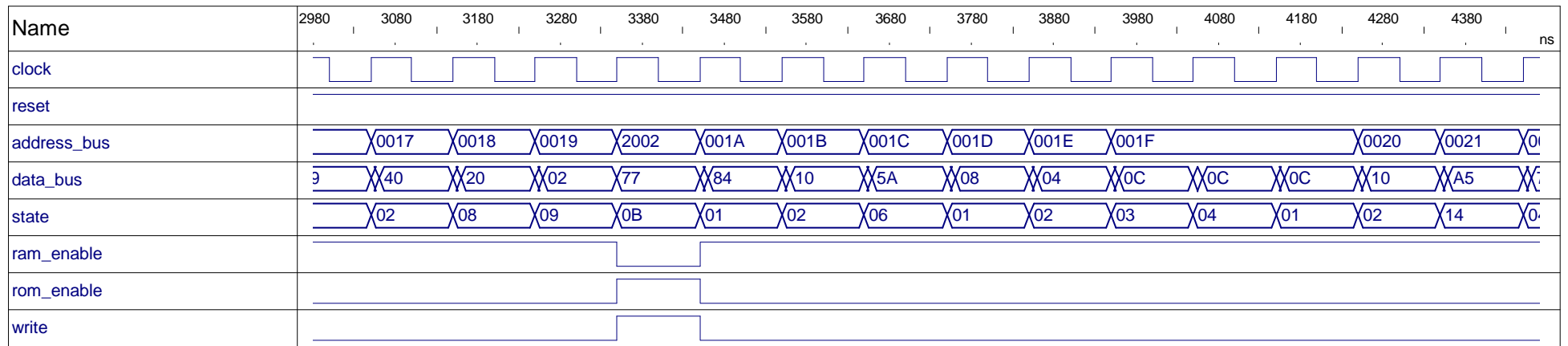



# CPU test program, part A

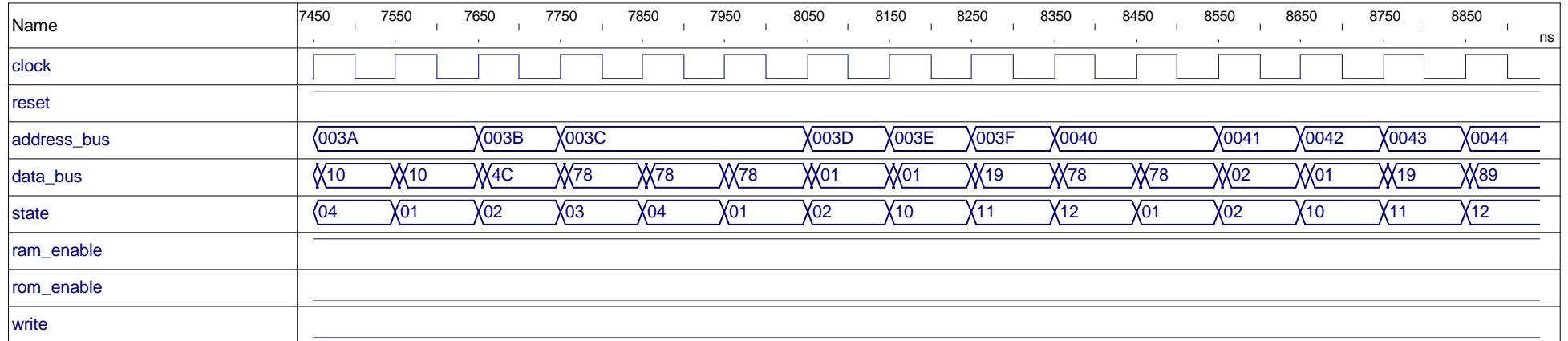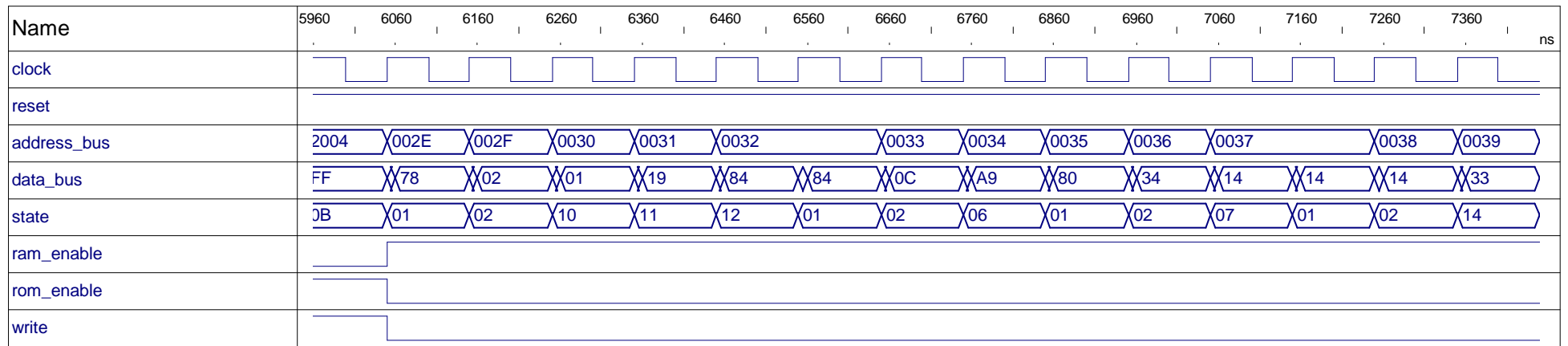



# CPU test program, part A

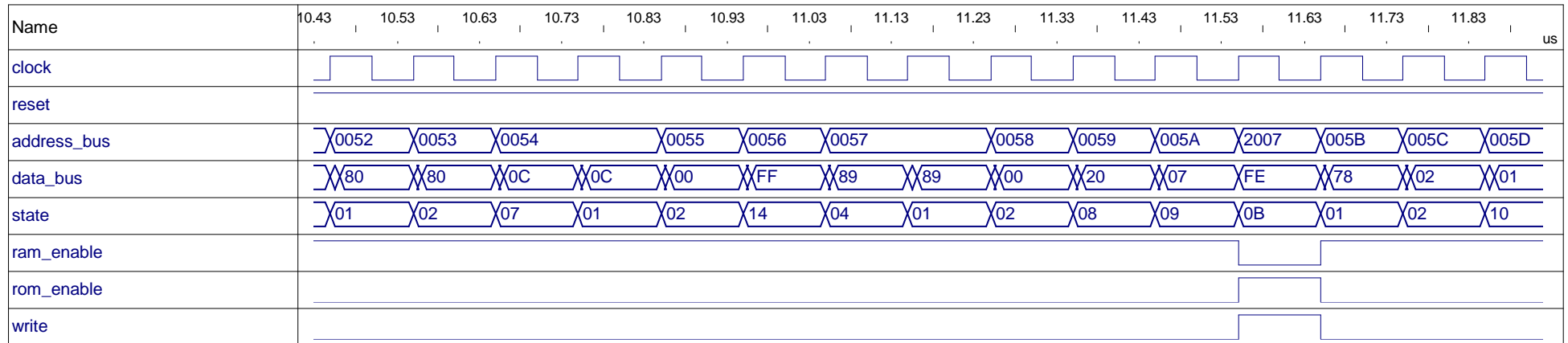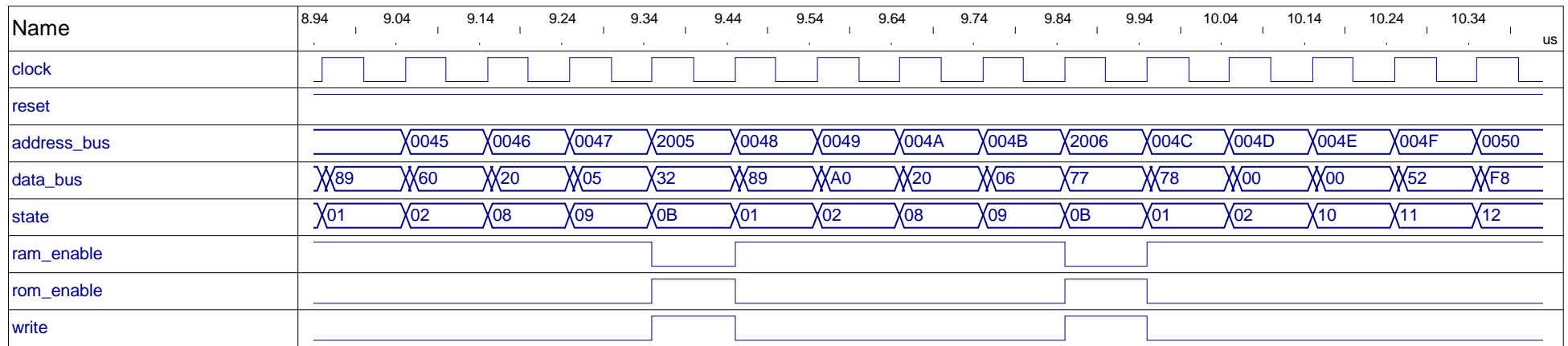



# CPU test program, part A

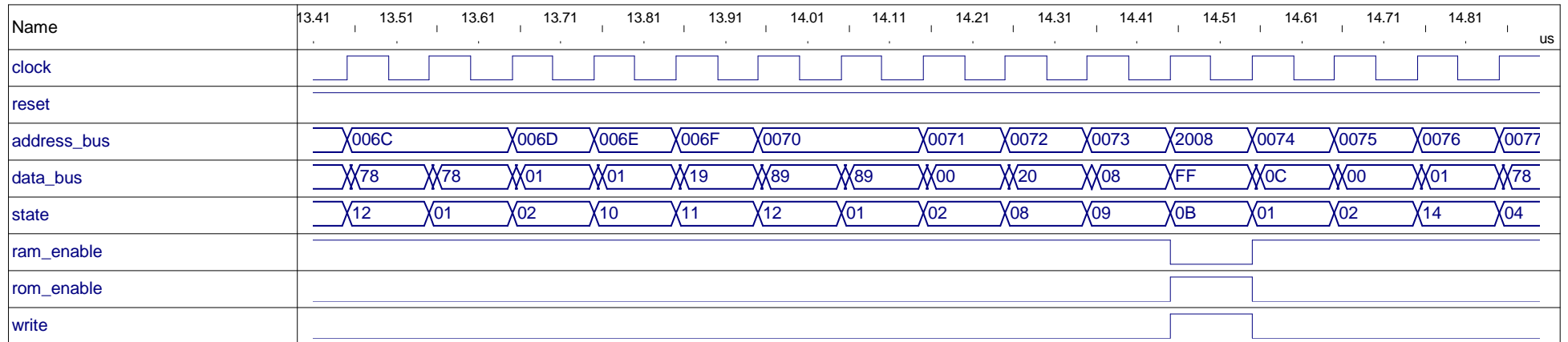 



# CPU test program, part A

 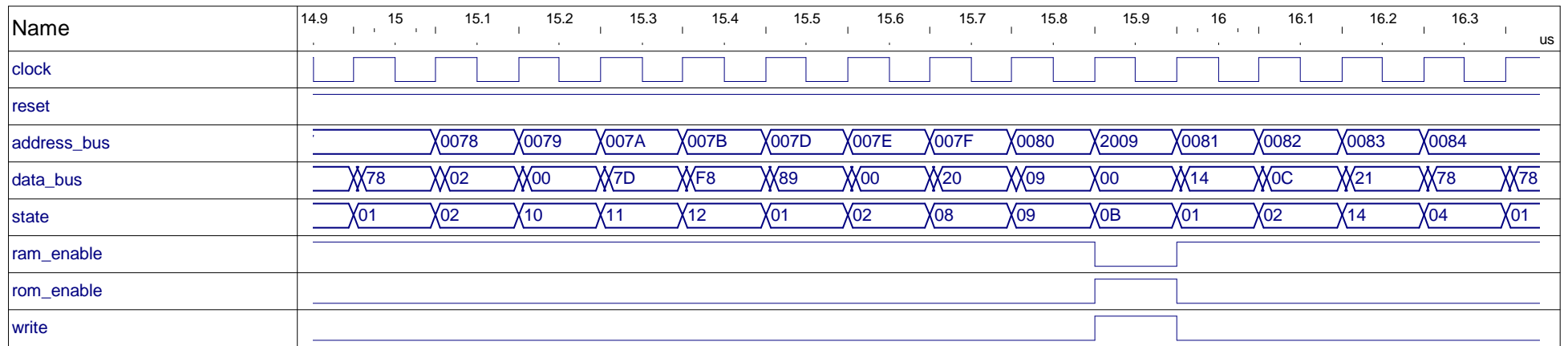

# CPU test program, part A

 
 


# CPU test program, part A

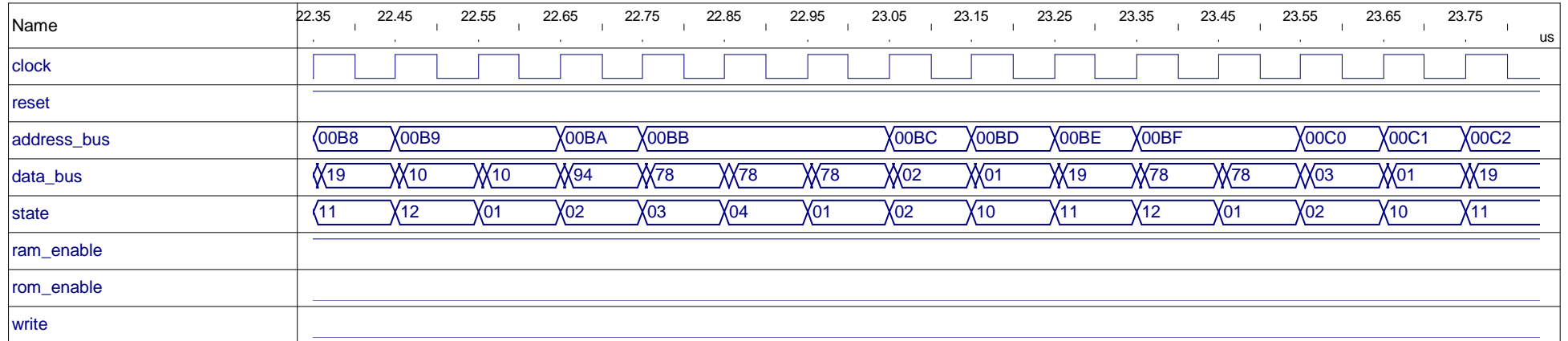
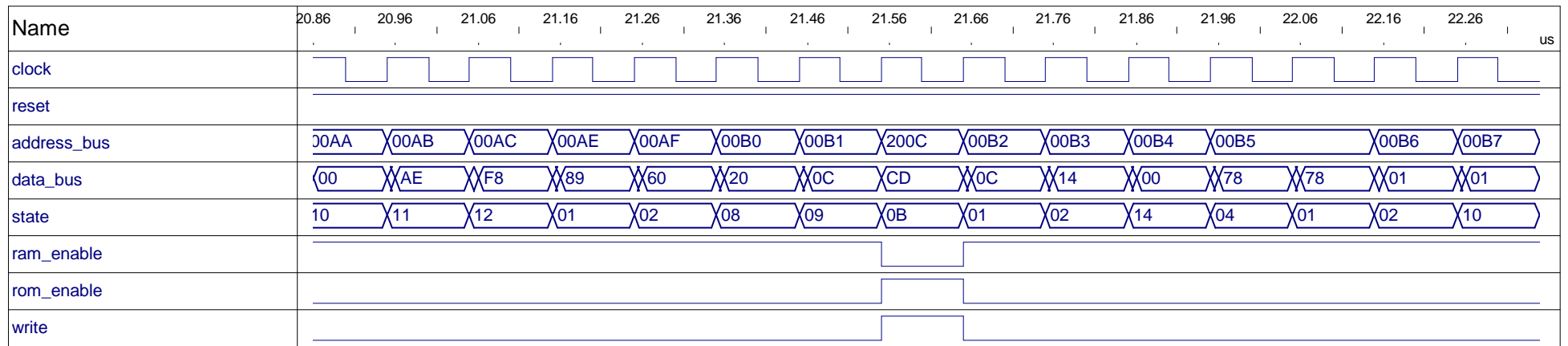






# CPU test program, part A

 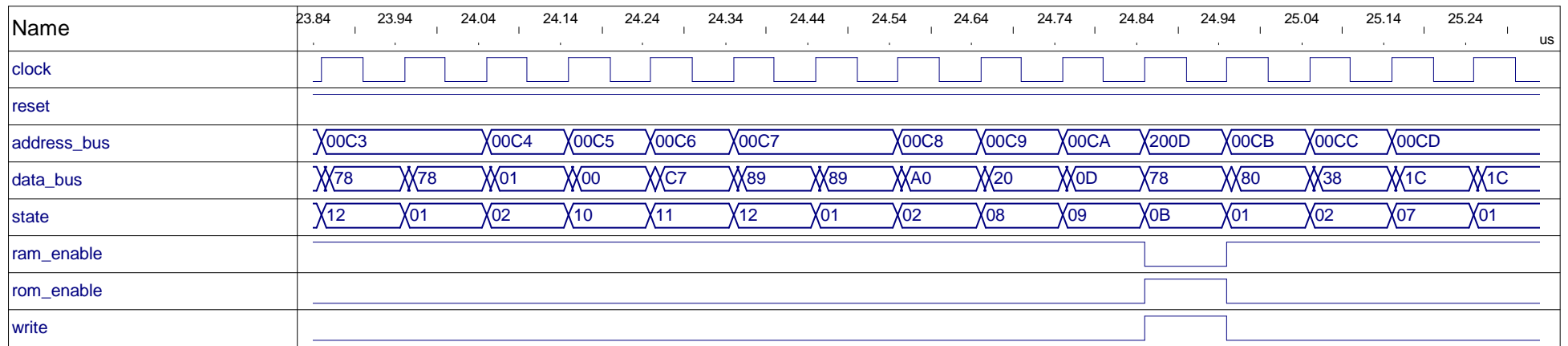



# CPU test program, part A

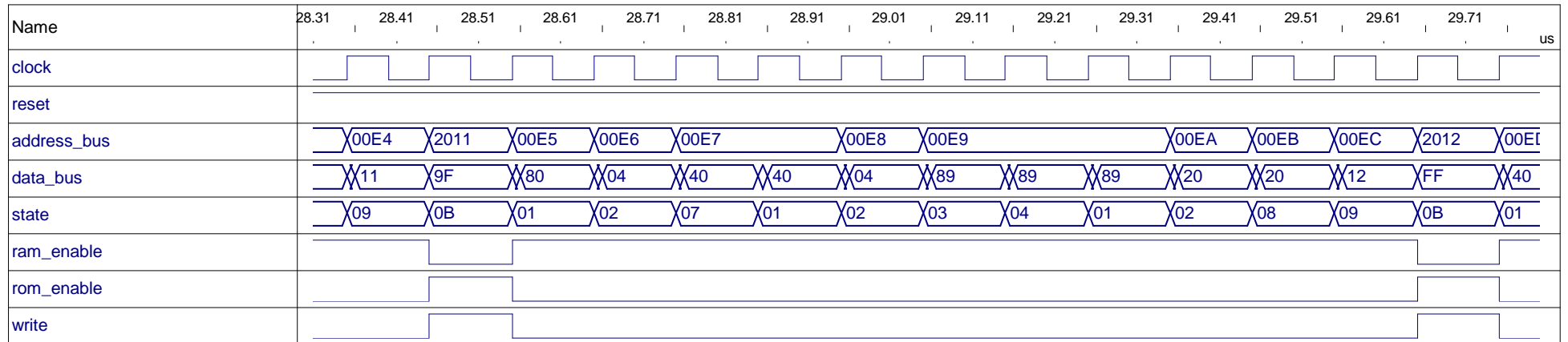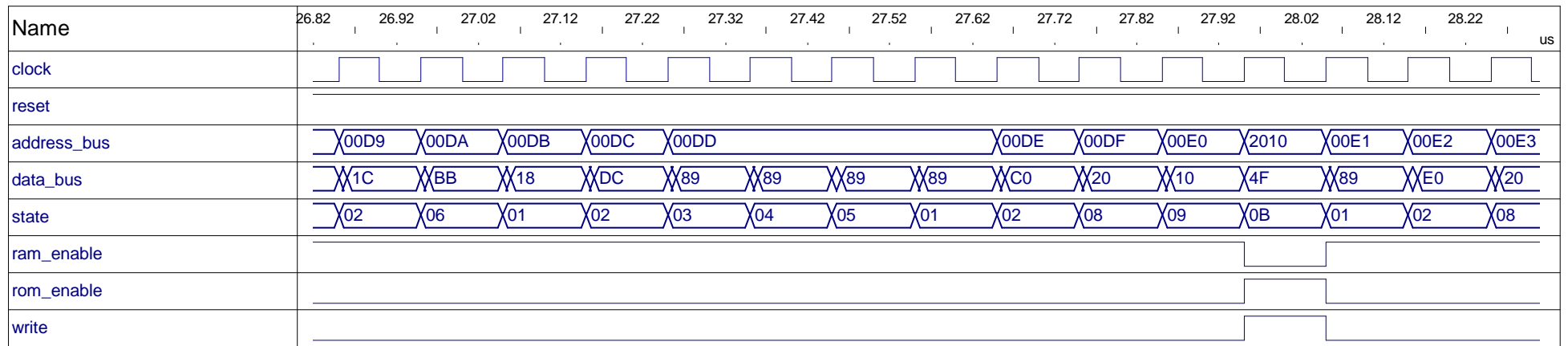


# CPU test program, part A

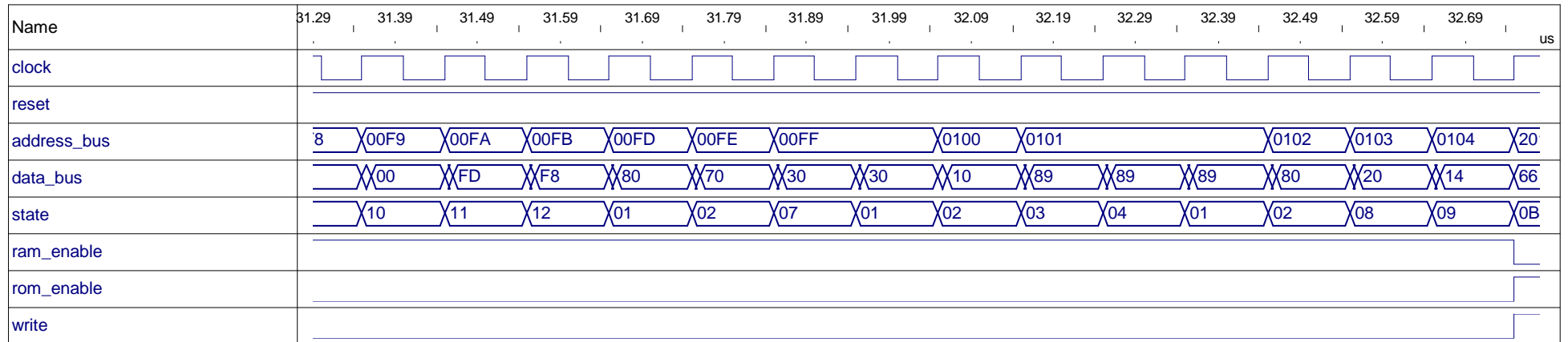 



# CPU test program, part A

  



CPU test program, part A

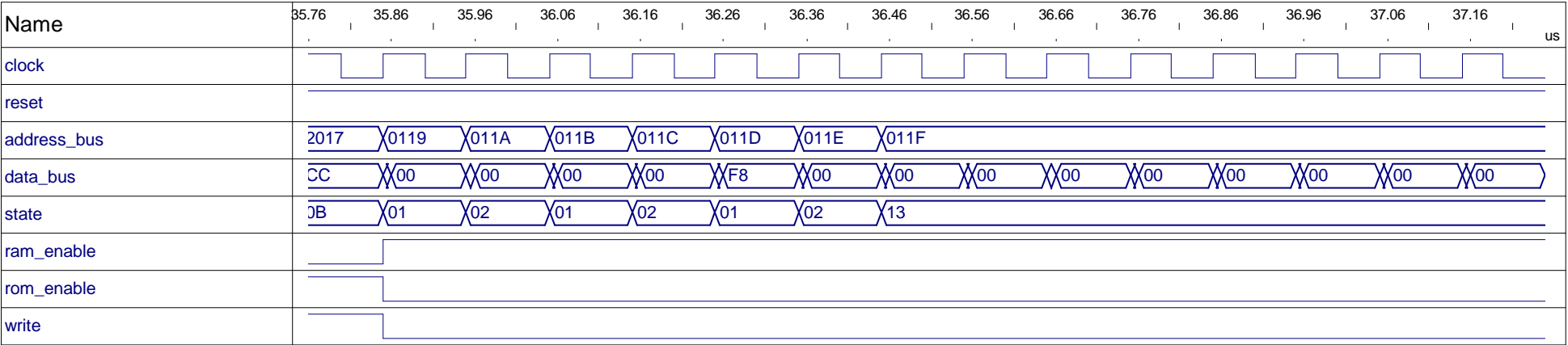



# CPU test program B

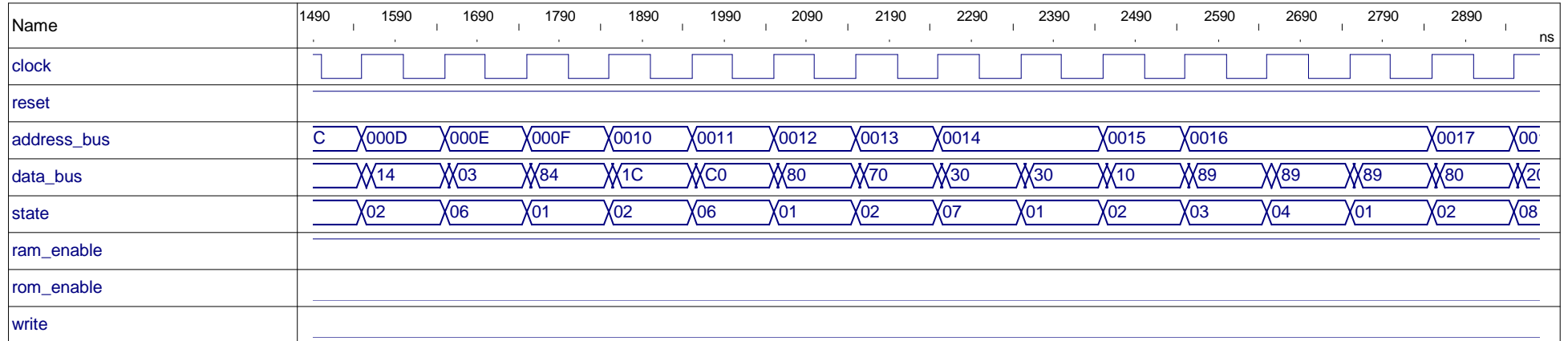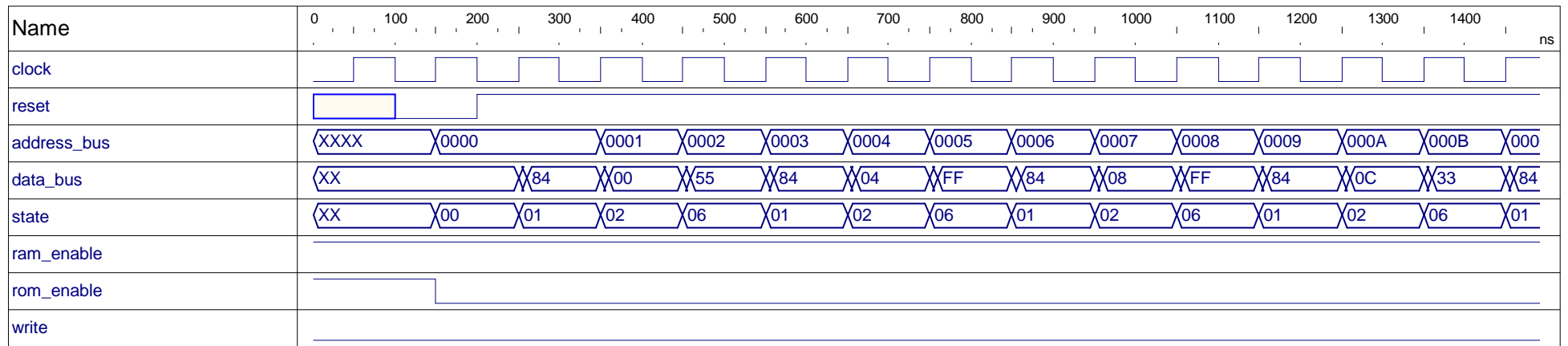

# CPU test program B

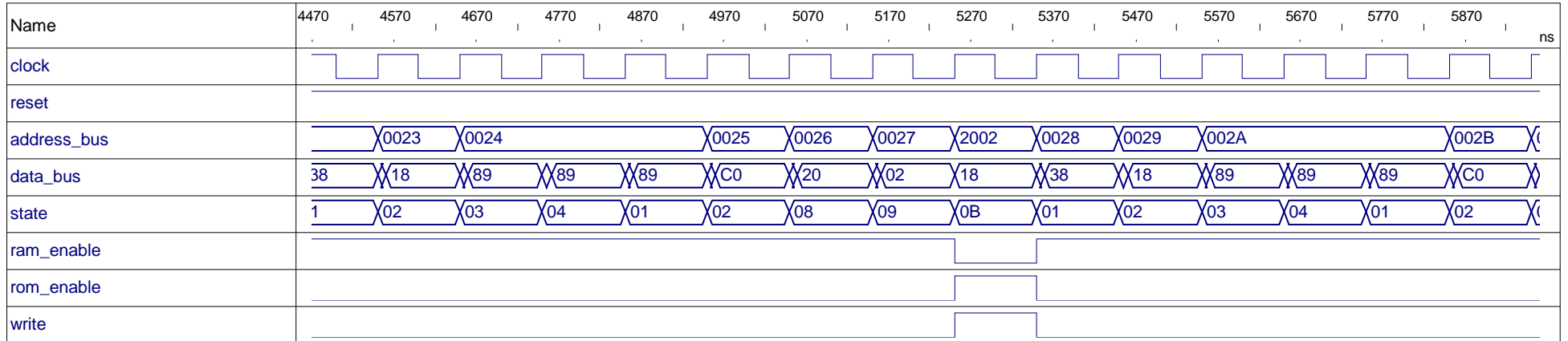
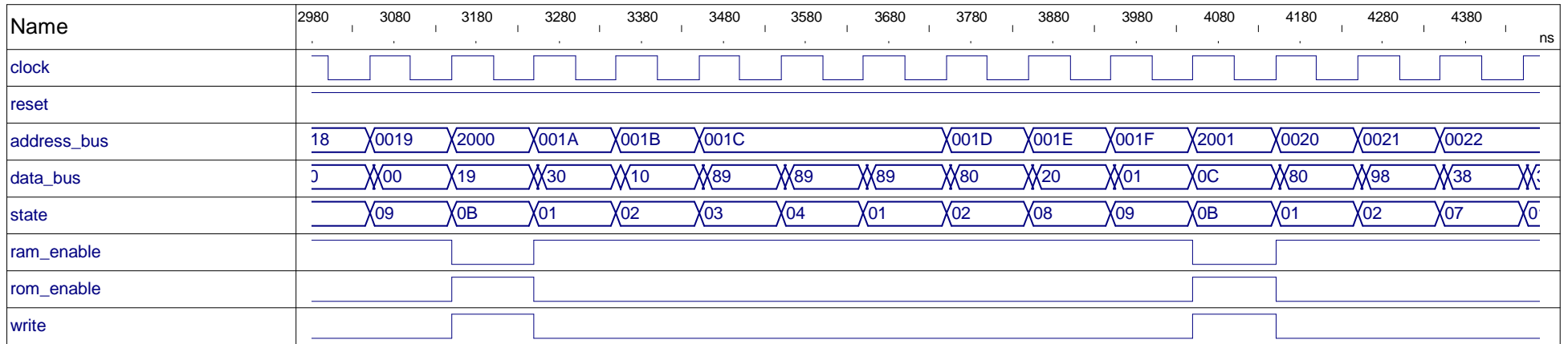


# CPU test program B

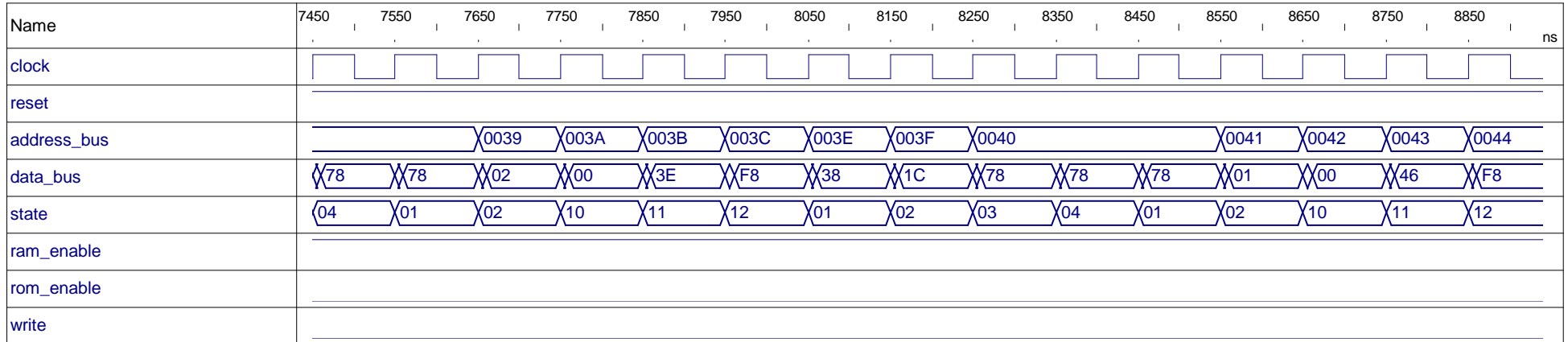
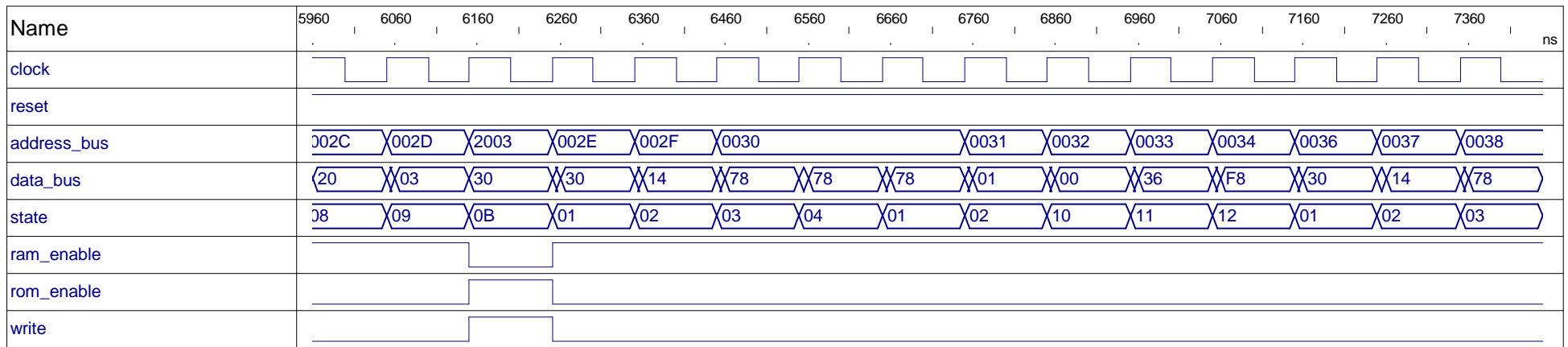






# CPU test program B

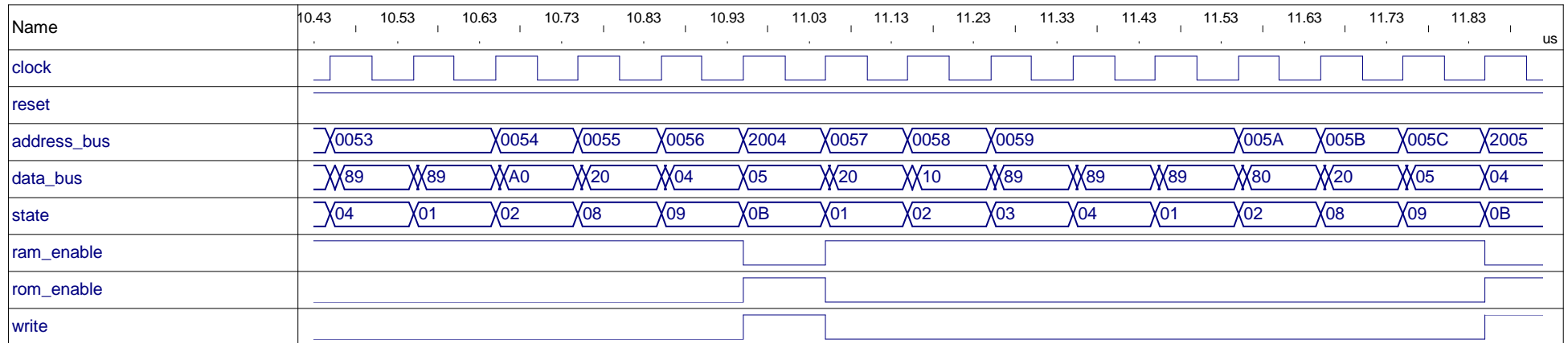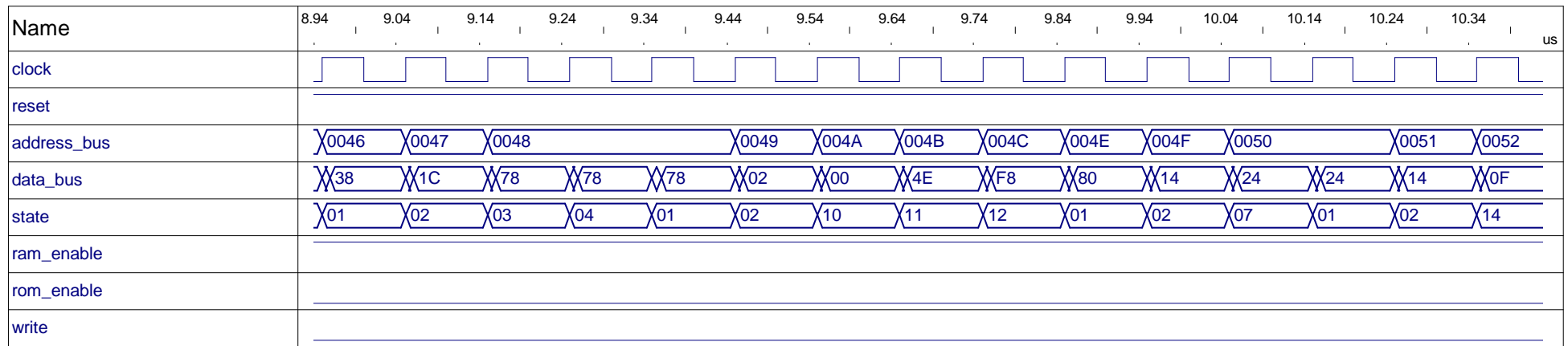



# CPU test program B

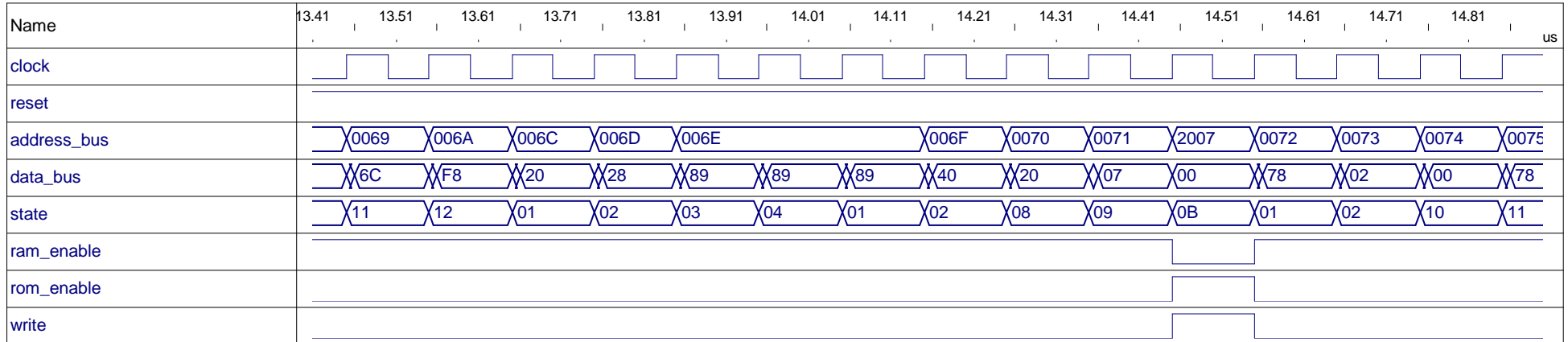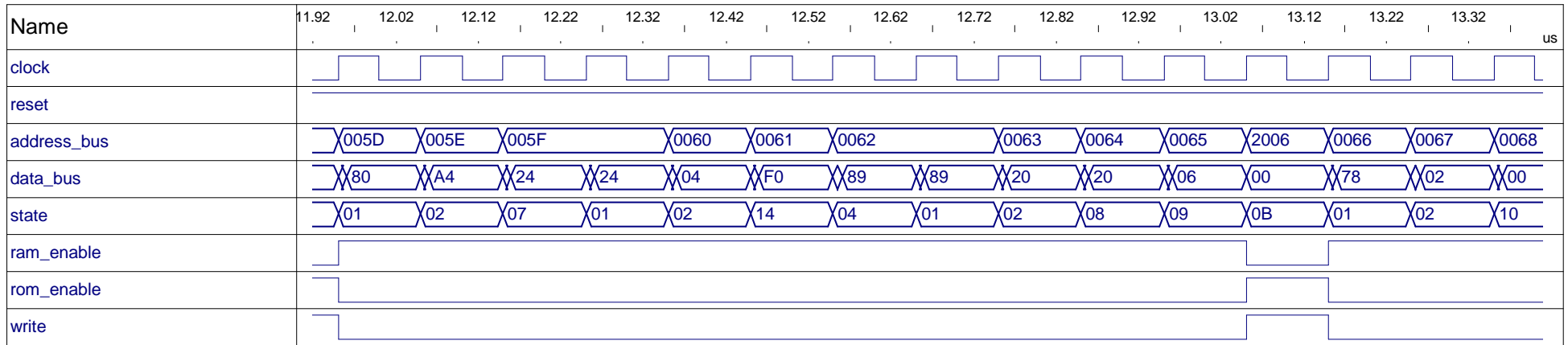


# CPU test program B

 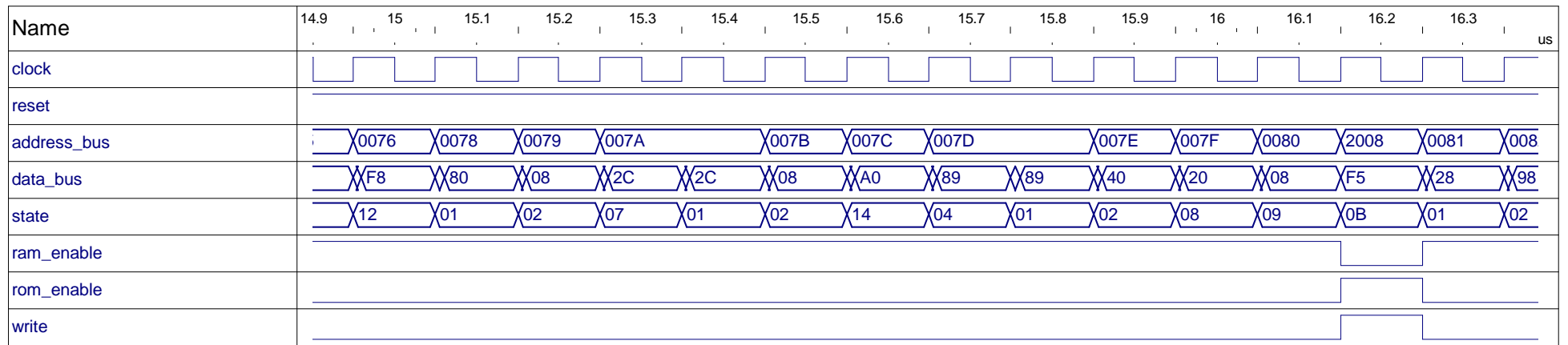

# CPU test program B

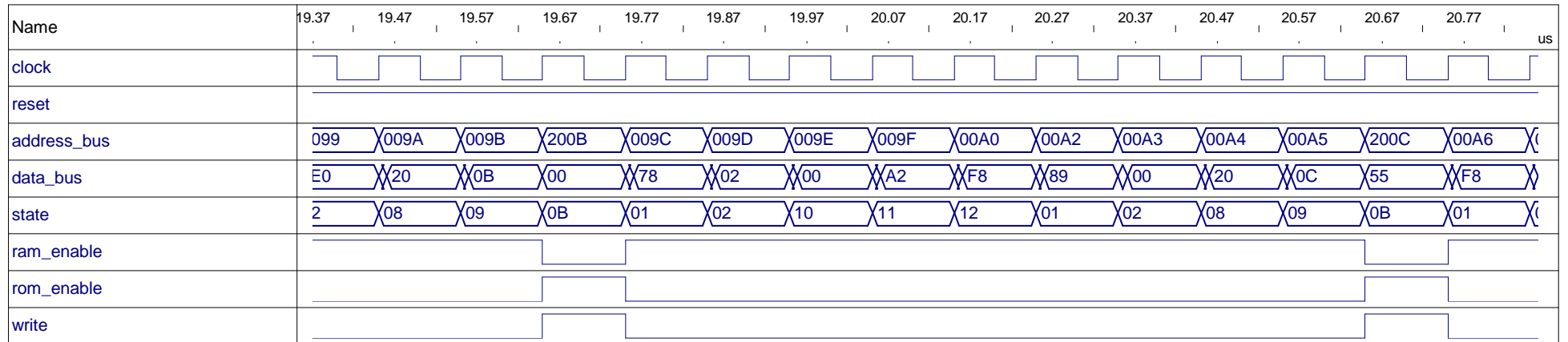 


CPU test program B

 

## D PCB diagrams

### D.1 Eagle schematic

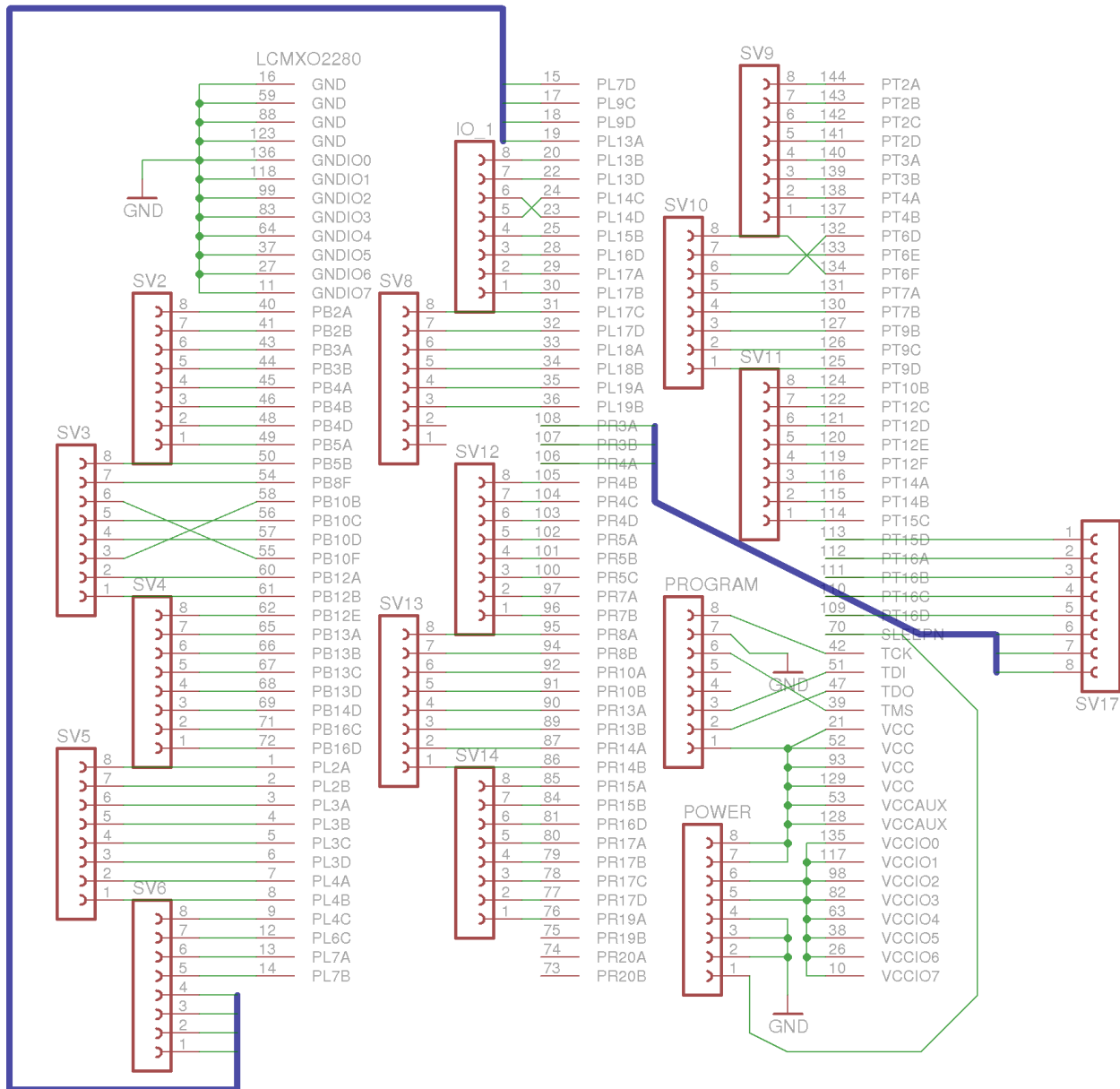



## E Assembler code

```
1  /**
2   * \file main.cpp
3   * Main code file for Steven's (purposeful|powerful|pimpin'|pernicious)
4     assembler (SPASM)
5   * \author Steven Bell <steven.bell@student.oc.edu>
6   * \date 4 November 2010
7   * $LastChangedDate: 2010-12-14 23:24:10 -0600 (Tue, 14 Dec 2010) $
8   */
9
10 /*
11  * Command-line arguments
12  * Usage:
13  *   spasm [args] inputfile
14  *
15  * -o           Output file
16  * -v, --verbose Verbose mode, print out lots of information about what's
17  *               going on
18  * -d, --dump   Do a hex dump of the program after it is assembled
19  * -h, --help   Print this help message
20  */
21
22 #include <QCoreApplication>
23 #include <QStringList>
24 #include <QFile>
25 #include "cstdio"
26 #include "console.h"
27 #include "parser.h"
28
29 int main(int argc, char* argv[])
30 {
31     // Read the input arguments
32     // We don't really need QCoreApplication for anything except the arguments,
33     // so maybe there's
34     // a better way to do this?
35     QCoreApplication app(argc, argv);
36     QStringList argList = app.arguments();
37
38     // If the help flag was specified, then just print the help message and quit
39     if(argList.contains("-h") || argList.contains("--help")){
40         printf("SPASM - Steven's special-purpose assembler\n");
41         printf("Copyright (c) 2010 Steven Bell <steven.bell@student.oc.edu>\n\n");
42         printf("Usage:\n");
43         printf("  spasm [args] inputfile\n\n");
44         printf("  -o, --output      Output file\n");
45         printf("  -v, --verbose     Verbose mode, print out lots of information\n");
46         printf("                    about what's going on\n");
47         printf("  -s, --simulator   Do a hex dump of the program for the Verilog\n");
48         printf("                    testbench\n");
49         printf("  -l, --listing     Print a command listing useful for debugging\n");
50         printf("  -h, --help        Print this help message\n");
51     }
```



```

46     printf(" Note that the -s, -l, and -v arguments are mutually exclusive.\n\
         n");
47     return(0);
48 }
49
50 // Get the input file name
51 QString inputFilePath(argList.last()); // Assume input file name is the last
        argument
52
53 // Determine the output file name
54 // If the -o flag was specified, use that name regardless of extension
55 QString outputFilePath;
56 if(argList.contains("-o")){
57     outputFilePath = argList.at(argList.indexOf("-o") + 1);
58 }
59 else if(argList.contains("--output")){
60     outputFilePath = argList.at(argList.indexOf("--output") + 1);
61 }
62 else{
63     // If no output file was specified, then use the input file name with the
        .S19 file extension
64     outputFilePath = inputFilePath + ".s19"; // Do something to strip off the
        extension
65 }
66
67 // Determine what kind of output to send to the terminal
68 bool verbose = false;
69 bool simDump = false;
70 bool listing = false;
71
72 if(argList.contains("-v") || argList.contains("--verbose")){
73     verbose = true;
74 }
75 else if(argList.contains("-s") || argList.contains("--simulator")){
76     simDump = true;
77 }
78 else if(argList.contains("-l") || argList.contains("--listing")){
79     listing = true;
80 }
81 Console::instance().setVerbose(verbose);
82
83 // Open the input file
84 QFile inputFile(inputFilePath);
85 if(!inputFile.open(QIODevice::ReadOnly | QIODevice::Text)){
86     printf("Failed to open file %s\n", inputFilePath.toAscii().constData());
87     return(1);
88 }
89
90 Parser p;
91 QByteArray programBytes;
92
93 // Run the first pass of the parser
94 // When undefined labels are encountered, the parser inserts 0x0000
95 // If undefined aliases are encountered, the parser throws an error

```

```

96 while(!inputFile.atEnd())
97 {
98     QString command(inputFile.readLine()); // Get the command string to parse
99     VERBOSE(p.linesRead(), command.trimmed().toAscii().constData()); // Print
        the command
100
101     // TODO: for each line, store the starting address so we can create a
        listing-style output
102     QByteArray commandBytes = p.parseLine(command);
103     programBytes.append(commandBytes);
104 }
105
106 // Fill in the labels which were undefined in the first pass
107 p.assignUnknownLabels(programBytes);
108
109 if(simDump) {
110     for(int i = 0; i < programBytes.length(); i++){
111         printf("%02x\n", (unsigned char) (programBytes[i]));
112     }
113 }
114
115 /* Create the output file (Motorola SREC format)
116    All values are hexadecimal, but are written in pairs of ASCII
        characters.
117    The format follows this pattern:
118    | "S1" | Byte Count | Start address | Data Data Data Data | Checksum |
119    |      | 1 byte    | 2 bytes    | Up to 32 bytes    | 1 byte    |
120 */
121
122 // Open the file
123 QFile outputFile(outputFilePath);
124 outputFile.open(QIODevice::WriteOnly | QIODevice::Text);
125
126 int i = 0;
127 while(i < programBytes.length())
128 {
129     unsigned char checksum; // The checksum is the ones' complement of the sum
        of the byte count, address, and data
130
131     // Create the line header
132     int lineByteCount = programBytes.length() - i; // Number of bytes
        remaining
133     lineByteCount = (lineByteCount < 32) ? lineByteCount : 32; // If there are
        more than 32 bytes remaining, only print 32 of them
134     QString lineString = QString("S1%1%2").arg(lineByteCount + 3, 2, 16, QChar
        ('0')).arg(i, 4, 16, QChar('0'));
135     checksum += lineByteCount; // Add the data byte count to the checksum
136     checksum += i; // Add the starting address to the checksum
137
138     for(int j = 0; j < lineByteCount; j++)
139     {
140         // Add the bytes

```

```

142     lineString.append(QString("%1").arg((unsigned char) (programBytes[i]), 2,
143         16, QChar('0')));
143     checksum += programBytes[i];
144     i++;
145 }
146 // Write the checksum
147 checksum = ~checksum;
148 lineString.append(QString("%1").arg(checksum, 2, 16, QChar('0')));
149 outputFile.write(lineString.toAscii().constData());
150 outputFile.write("\n"); // Write a newline
151 }
152
153
154 return(0);
155 }

```

```

1  /** parser.cpp
2   * Class declaration for the parser class, which parses sets of instructions
3   *   passed to it.
4   * Author: Steven Bell <steven.bell@student.oc.edu>
5   * Date: 24 November 2010
6   * $LastChangedDate: 2010-12-14 23:24:10 -0600 (Tue, 14 Dec 2010) $
7   */
8
9  #ifndef PARSER_H
10 #define PARSER_H
11
12 #include <QString>
13 #include <QHash>
14 #include <QByteArray>
15
16 class Parser
17 {
18 public:
19     typedef enum
20     {
21         NOP = 0x00,
22         ADD = 0x01,
23         SUB = 0x02,
24         MUL = 0x03,
25         AND = 0x04,
26         OR = 0x05,
27         LSR = 0x06,
28         LSL = 0x07,
29         COMP = 0x08,
30         ASR = 0x09,
31         ASL = 0x0a,
32         NEG = 0x0b, // Two's complement
33         // PASSTHROUGH (0x0c) is for internal use only
34         JUMP = 0x0f,
35         LOAD = 0x10,
36         STORE = 0x11,
37         MOVE = 0x12,

```

```

38     LSTACK = 0x13,
39     JSR = 0x14,
40     RSUB = 0x15,
41     RINT = 0x16,
42     HALT = 0x1F,
43     INVALID = 0xFF
44 } Opcode;
45
46 typedef enum
47 {
48     A = 0,
49     B = 1,
50     C = 2,
51     D = 3,
52     E = 4,
53     F = 5,
54     G = 6,
55     H = 7
56 } RegisterCode;
57
58 typedef enum
59 {
60     NONE = 0,
61     REGISTER = 2,
62     IMMEDIATE = 4,
63     ADDRESS = 8
64 } TokenType;
65
66 Parser();
67 QByteArray parseLine(QString line);
68 void assignUnknownLabels(QByteArray& code);
69 int linesRead(void) {return(mLineCount);}
70
71 private:
72     bool parseRegisterDest(QStringList* tokens, unsigned short* opcodeBytes);
73     Opcode stringToOpcode(QString str);
74     TokenType parseParameterToken(QString token, int allowable, unsigned short &
        value);
75
76     int mLineCount; ///< Counts how many lines have been parsed
77
78     ///< Address where the next instruction will be stored in memory, used for
        labels
79     unsigned int mByteLocation;
80
81     ///< Map of addresses to unknown labels
82     QHash<unsigned short, QString> mUnknownLabels;
83
84     ///< Map of defines and labels to addresses
85     QHash<QString, QString> mDefineTable;
86
87 };
88
89 #endif // PARSER_H

```

```

1  /** parser.cpp
2   * Code to parse instructions given one at a time. Labels are held
   * persistently and handled appropriately.
3   * Author: Steven Bell <steven.bell@student.oc.edu>
4   * Date: 24 November 2010
5   * $LastChangedDate: 2010-12-14 23:24:10 -0600 (Tue, 14 Dec 2010) $
6   */
7
8  #include <cstdio>
9  #include <QStringList>
10 #include "console.h"
11 #include "parser.h"
12
13
14 /** Constructor
15  */
16 Parser::Parser()
17 {
18     mByteLocation = 0;
19     mLineCount = 1; // Line numbers start at 1, not 0!
20 }
21
22 /** Parses a single line of code, which is assumed to contain a single
   * instruction at most.
23  * \param line Text string to parse.
24  */
25 QByteArray Parser::parseLine(QString command)
26 {
27     // Strip off any comment
28     int commentPos = command.indexOf('*');
29     if(commentPos != -1){ // If a comment delimiter was found,
30         command = command.left(commentPos);
31     }
32
33     QStringList tokens = command.split(QRegExp(",|\\s"), QString::SkipEmptyParts
   );
34
35     // TODO: should use a regex here to make sure that we don't end up with
36     // funky characters in the labels.
37     while(!tokens.isEmpty() && tokens.first().contains(QRegExp("[a-zA-Z]\\w+:$"
   )))
38     {
39         // Parse the label(s) from the front, if there are any
40         QString label = tokens.first();
41         label = label.remove(QChar(':')); // Take the colon off the end
42         VERBOSE(mLineCount, "Label_found_at_0x%04x:_%s\\n", mByteLocation, label.
   toAscii().constData());
43
44         // Create a string with the memory address so we can use it like any other
         define
45         mDefineTable[label] = QString("0x%1").arg(mByteLocation, 4, 16, QChar('0')
   );
46         tokens.removeFirst();
47     }

```

```

48
49 if(tokens.isEmpty()){ // If there's nothing, or only labels,
50     VERBOSE(mLineCount, "Empty_line!"); // Then move on
51     mLineCount++;
52     return(QByteArray());
53 }
54
55 QByteArray commandBytes; // Complete set of bytes, including immediates and
    addresses
56 unsigned short opcodeBytes = 0; // Pair of bytes used to assemble the opcode
57 unsigned short parsedBytes; // Values returned from each token parsing
58 Parser::TokenType parseResult; // Return type of token that was parsed
59
60 QString codeString = tokens.first(); // Save this in a separate variable so
    we can use it to differentiate the jumps
61 Parser::Opcode code = stringToOpcode(codeString);
62 tokens.removeFirst();
63 opcodeBytes = code << 11; // Move the code into the 5 highest bytes
64 mByteLocation += 2;
65
66 switch(code) {
67     case Parser::NOP:
68     case Parser::HALT:
69     case Parser::RSUB:
70     case Parser::RINT:
71         VERBOSE(mLineCount, "No_args_required");
72         break;
73     case Parser::ADD:
74     case Parser::SUB:
75     case Parser::MUL:
76     case Parser::AND:
77     case Parser::OR:
78         VERBOSE(mLineCount, "Two_args_required,_register_and_register/immediate"
79             );
80         parseRegisterDest(&tokens, &opcodeBytes);
81
82         parseResult = parseParameterToken(tokens.first(), Parser::REGISTER |
            Parser::IMMEDIATE, parsedBytes);
83         tokens.removeFirst();
84         if(parseResult == REGISTER){
85             opcodeBytes = opcodeBytes | (parsedBytes << 5); // Put the source
                register into bytes 7-5
86             // Don't have to set the source type, since it's already 00
87         }
88         else if(parseResult == IMMEDIATE){
89             // Append the immediate to the extra bytes
90             commandBytes.append((char)parsedBytes);
91             mByteLocation += 1;
92             opcodeBytes = opcodeBytes | (0x0400); // Set the source type bits to
                immediate
93         }
94         else{

```

```

95         ERROR(mLineCount, "Expected_register_or_immediate_as_second_argument")
96     };
97     break;
98     case Parser::LSR:
99     case Parser::LSL:
100    case Parser::ASR:
101    case Parser::ASL:
102    case Parser::COMP:
103    case Parser::NEG:
104        VERBOSE(mLineCount, "One_register_argument_required");
105        parseRegisterDest(&tokens, &opcodeBytes); // The first argument must
            always be a the destination register
106    break;
107    case Parser::JUMP:
108        if(codeString.toUpper() == "JCAR"){
109            opcodeBytes = opcodeBytes | (0x0001); // Carry code is binary 01
110        }
111        else if(codeString.toUpper() == "JZERO"){
112            opcodeBytes = opcodeBytes | (0x0002); // Zero code is binary 10
113        }
114        else if(codeString.toUpper() == "JNEG"){
115            opcodeBytes = opcodeBytes | (0x0003); // Negative code is binary 11
116        }
117        // Jump always code is binary 00, so we don't have to do anything
118        // Fall through the case so that we can get the memory argument
119    case Parser::LSTACK:
120    case Parser::JSR:
121        VERBOSE(mLineCount, "One_memory_argument_required");
122        parseResult = parseParameterToken(tokens.first(), Parser::ADDRESS,
            parsedBytes);
123        tokens.removeFirst();
124        if(parseResult == ADDRESS){
125            commandBytes.append((char)(parsedBytes >> 8));
126            commandBytes.append((char)parsedBytes);
127            mByteLocation += 2;
128        }
129        else{
130            ERROR(mLineCount, "Expected_address_or_label_as_first_argument");
131        }
132
133    break;
134    case Parser::LOAD:
135        VERBOSE(mLineCount, "Two_args_required,_register_and_register/immediate/
            memory");
136        parseRegisterDest(&tokens, &opcodeBytes); // The first argument must
            always be a the destination register
137        parseResult = parseParameterToken(tokens.first(), Parser::REGISTER |
            Parser::IMMEDIATE | Parser::ADDRESS, parsedBytes);
138        tokens.removeFirst();
139        if(parseResult == REGISTER){ // COPY
140            opcodeBytes = opcodeBytes | (parsedBytes << 5); // Put the source
                register as
141            // Don't have to set the source type, since it's already 00

```

```

142     }
143     else if (parseResult == IMMEDIATE) {
144         commandBytes.append((char)parsedBytes);
145         mByteLocation += 1;
146         opcodeBytes = opcodeBytes | (0x0400); // Set the source type bits to
            immediate
147     }
148     else if (parseResult == ADDRESS) {
149         commandBytes.append((char) (parsedBytes >> 8));
150         commandBytes.append((char)parsedBytes);
151         mByteLocation += 2;
152         opcodeBytes = opcodeBytes | (0x0200); // Set the source type bits to
            memory
153     }
154
155     break;
156 case Parser::STORE:
157     VERBOSE(mLineCount, "Two_args_required,_register_and_memory");
158
159     parseResult = parseParameterToken(tokens.first(), Parser::REGISTER,
        parsedBytes);
160     tokens.removeFirst();
161     if (parseResult == REGISTER) {
162         opcodeBytes = opcodeBytes | (parsedBytes << 5);
163     }
164     else {
165         ERROR(mLineCount, "Expected_register_as_first_argument");
166     }
167
168     parseResult = parseParameterToken(tokens.first(), Parser::ADDRESS,
        parsedBytes);
169     tokens.removeFirst();
170     if (parseResult == ADDRESS) {
171         commandBytes.append((char) (parsedBytes >> 8));
172         commandBytes.append((char)parsedBytes);
173         mByteLocation += 2;
174         opcodeBytes = opcodeBytes | (0x0100); // Set the destination type bits
            to memory
175     }
176     else {
177         ERROR(mLineCount, "Expected_address_as_second_argument");
178     }
179
180     break;
181 case Parser::MOVE:
182     // This code is repeated several times essentially verbatim. Time for a
        function?
183     VERBOSE(mLineCount, "Two_addresses_required\n");
184     parseResult = parseParameterToken(tokens.first(), Parser::ADDRESS,
        parsedBytes);
185     tokens.removeFirst();
186     if (parseResult == ADDRESS) {
187         commandBytes.append((char) (parsedBytes >> 8));
188         commandBytes.append((char)parsedBytes);

```



```

189         mByteLocation += 2;
190     }
191     else{
192         ERROR(mLineCount, "Expected_address_as_first_argument");
193     }
194     parseResult = parseParameterToken(tokens.first(), Parser::ADDRESS,
195         parsedBytes);
196     tokens.removeFirst();
197     if(parseResult == ADDRESS){
198         commandBytes.append((char) (parsedBytes >> 8));
199         commandBytes.append((char) parsedBytes);
200         mByteLocation += 2;
201     }
202     else{
203         ERROR(mLineCount, "Expected_address_as_second_argument");
204     }
205
206     break;
207 default:
208     ERROR(mLineCount, "Unrecognized_opcode");
209     break;
210 }
211
212 // Make sure that we've used up all of the arguments. If not, print a
213 // warning
214 if(!tokens.isEmpty()){
215     WARNING(mLineCount, "Unused_arguments");
216 }
217
218 commandBytes.push_front((char) (opcodeBytes & 0x00ff));
219 commandBytes.push_front((char) (opcodeBytes >> 8));
220
221 mLineCount++;
222 // Byte location was already handled in-line
223
224 return(commandBytes);
225 }
226
227 /** This function goes through all of the locations in the unknown labels list
228     and
229     * replaces the placeholder address with the correct value. If the label is
230     not
231     * found, then it prints an error.
232     */
233 void Parser::assignUnknownLabels(QByteArray& code)
234 {
235     QHash<unsigned short, QString>::iterator i;
236     for(i = mUnknownLabels.begin(); i != mUnknownLabels.end(); i++)
237     {
238         if(mDefineTable.contains(i.value())){
239             QString replacementString = mDefineTable[i.value()];
240             bool conversionOk; // Assume that it works; since we created the value!

```

```

238     unsigned int replacementValue = replacementString.mid(3).toUShort(&
        conversionOk, 16);
239
240     // TODO: This will fail badly if the code has multiple segments or doesn
        't start at 0.
241     code[i.key()] = (replacementValue >> 8);
242     code[i.key() + 1] = (replacementValue & 0x00FF);
243
244
245     VERBOSE(mLineCount, "Replacing_label_\\"%s\\""_with_0x%04x", i.value().
        toAscii().constData(), replacementValue);
246 }
247 else{
248     ERROR(mLineCount, "Unknown_label_\\"%s\\"", i.value().toAscii().constData
        ());
249 }
250 }
251 }
252
253
254 /* This function removes one of the tokens from the list
255 */
256 bool Parser::parseRegisterDest(QStringList* tokens, unsigned short*
    opcodeBytes)
257 {
258     unsigned short parsedBytes;
259     Parser::TokenType parseResult = parseParameterToken(tokens->first(), Parser
        ::REGISTER, parsedBytes);
260     tokens->removeFirst();
261     if(parseResult == REGISTER){
262         *opcodeBytes = *opcodeBytes | (parsedBytes << 2); // Put the destination
            register into bytes 4-2
263         return(true);
264     }
265     else{
266         ERROR(mLineCount, "Expected_register_as_first_argument");
267         return(false);
268     }
269 }
270
271
272 /** Converts a string token (e.g, ADD or HALT) into an enum constant
    representing
273 * the opcode.
274 */
275 Parser::Opcode Parser::stringToOpcode(QString str)
276 {
277     str = str.toUpper(); // Force everything to uppercase
278
279     if(str == "NOP"){
280         return(NOP);
281     }
282     else if(str == "ADD"){
283         return(ADD);

```

```

284     }
285     else if(str == "SUB") {
286         return(SUB);
287     }
288     else if(str == "MUL") {
289         return(MUL);
290     }
291     else if(str == "AND") {
292         return(AND);
293     }
294     else if(str == "OR") {
295         return(OR);
296     }
297     else if(str == "LSR") {
298         return(LSR);
299     }
300     else if(str == "LSL") {
301         return(LSL);
302     }
303     else if(str == "COMP") {
304         return(COMP);
305     }
306     else if(str == "ASR") {
307         return(ASR);
308     }
309     else if(str == "ASL") {
310         return(ASL);
311     }
312     else if(str == "NEG") {
313         return(NEG);
314     }
315     else if(str == "JMP" || str == "JCAR" || str == "JZERO" || str == "JNEG") {
316         return(JUMP);
317     }
318     else if(str == "LOAD" || str == "COPY") {
319         return(LOAD);
320     }
321     else if(str == "STORE") {
322         return(STORE);
323     }
324     else if(str == "MOVE") {
325         return(MOVE);
326     }
327     else if(str == "LSTACK") {
328         return(LSTACK);
329     }
330     else if(str == "JSR") {
331         return(JSR);
332     }
333     else if(str == "RSUB") {
334         return(RSUB);
335     }
336     else if(str == "RINT") {
337         return(RINT);

```

```

338     }
339     else if(str == "HALT"){
340         return(HALT);
341     }
342     else{
343         return(INVALID);
344     }
345 }
346
347
348 /** Takes a single token, determines what type of token it is, and parses its
349     value.
350     * If the token is a label or macro, it looks it up in the appropriate table
351     and
352     * substitutes that value.
353     * \param token The token to parse.
354     * \param allowable Acceptable types of tokens. Multiple types can be
355     selected using bitwise OR. If
356     * a token of the selected type is not found, this function will return
357     failure.
358     * \param value 2-byte variable which will hold the parsed value.
359     * \return The type of token that was parsed. This could be a 3-bit register
360     (registerCode),
361     * a one byte immediate value, a two byte immediate address, or a failure.
362     */
363 Parser::TokenType Parser::parseParameterToken(QString token, int allowable,
364     unsigned short &value)
365 {
366     bool conversionOk;
367
368     // Use a set of regular expressions to sort the tokens
369     // If the token is a single letter, A-H (a-h) then it is a register
370     if(((allowable & REGISTER) != 0) && token.contains(QRegExp("^a-zA-H]$"))){
371         VERBOSE(mLineCount, "Token_is_register");
372         char regChar = token.at(0).toLower().toAscii();
373         value = regChar - 97; // 97 is ascii for 'a'
374         return(REGISTER);
375     }
376
377     // If the token begins with 0x, then it is a hexadecimal address
378     else if(((allowable & ADDRESS) != 0) && token.contains(QRegExp("^0x[0-9a-fA-
379 F_]+$"))){
380         VERBOSE(mLineCount, "Token_is_hex_address");
381         value = token.toUShort(&conversionOk, 16); // Qt doesn't mind the leading
382         0x
383         if(conversionOk){
384             return(ADDRESS);
385         }
386         else{
387             return(NONE);
388         }
389     }
390
391     // If the token begins with 0b, then it is a binary address

```

```

383     else if(((allowable & ADDRESS) != 0) && token.contains(QRegExp("^0b[01_]+$")
384         )){
385         VERBOSE(mLineCount, "Token_is_binary_address");
386         value = token.mid(2).toUShort(&conversionOk, 2); // Drop the "0b" and
387             convert
388         if(conversionOk){
389             return(ADDRESS);
390         }
391         else{
392             return(NONE);
393         }
394     }
395     // If the token begins with any digit, then it is a decimal address
396     else if(((allowable & ADDRESS) != 0) && token.contains(QRegExp("[+-]?\\d+$")
397         ))){
398         VERBOSE(mLineCount, "Token_is_decimal_address");
399         value = token.toUShort(&conversionOk, 10); // Qt automatically handles
400             negative values
401         if(conversionOk){
402             return(ADDRESS);
403         }
404         else{
405             return(NONE);
406         }
407     }
408     // If the token begins with #0x, then it is a hexadecimal immediate
409     else if(((allowable & IMMEDIATE) != 0) && token.contains(QRegExp("#0x[0-9a-
410         fA-F_]+$"))){
411         VERBOSE(mLineCount, "Token_is_hex_immediate");
412         value = token.mid(3).toUShort(&conversionOk, 16); // Drop the #0x
413         if(conversionOk){
414             return(IMMEDIATE);
415         }
416         else{
417             return(NONE);
418         }
419     }
420     // If the token begins with #0b, then it is a binary address
421     else if(((allowable & IMMEDIATE) != 0) && token.contains(QRegExp("#0b[01_]+
422         $"))){
423         VERBOSE(mLineCount, "Token_is_binary_immediate");
424         value = token.mid(3).toUShort(&conversionOk, 2); // Drop the "#0b" and
425             convert
426         if(conversionOk){
427             return(IMMEDIATE);
428         }
429         else{
430             return(NONE);
431         }
432     }
433     // If the token begins with '#' and then any digit, then it is a decimal
434     address

```

```

428     else if(((allowable & IMMEDIATE) != 0) && token.contains(QRegExp("^#[+-]?\\d
        +$"))){
429         VERBOSE(mLineCount, "Token_is_decimal_immediate");
430         value = token.mid(1).toUShort(&conversionOk, 10); // Drop the "#"
431         if(conversionOk){
432             return(IMMEDIATE);
433         }
434         else{
435             return(NONE);
436         }
437     }
438     else if(token.contains(QRegExp("^([a-zA-Z]\\w+$"))){
439         // If the token starts with a letter, contains only alphanumeric
            characters and
440         // underscores, and is at least 2 characters long, then see if it's a
            label or macro
441
442         if(mDefineTable.contains(token)){
443             // Replace the macro or label with the appropriate token
444             // Call this function recursively on the replaced token
445             return(parseParameterToken(mDefineTable[token], allowable, value));
446         }
447         else{
448             // If the table doesn't contain what we're looking for, just substitute
                a placeholder
449             // address and put this location into the unknown labels table.
450             if(allowable & ADDRESS){
451                 VERBOSE(mLineCount, "Encountered_unknown_label_s_at_0x04x", token.
                    toAscii().constData(), mByteLocation);
452                 mUnknownLabels[mByteLocation] = token;
453                 value = 0;
454                 return(ADDRESS);
455             }
456             else{
457                 // If an address isn't allowed here, then it's an error
458                 ERROR(mLineCount, "Unexpected_token_\"%s\"", token.toAscii().constData
                    ());
459                 return(NONE);
460             }
461         }
462     }
463     else{
464         ERROR(mLineCount, "Unexpected_token_\"%s\"", token.toAscii().constData());
465         return(NONE);
466     }
467 }

```

```

1  /** \file console.h
2   * Singleton class which handles printing of messages, errors and warnings
3   * to the console. It contains flags which can be used to turn messages on
4   * and off, and keeps track of the total number of errors/warnings.
5   * \author Steven Bell <steven.bell@student.oc.edu>
6   * \date 12 December 2010
7   */

```

```

8
9 class Console
10 {
11 public:
12     static Console& instance();
13     void setVerbose(bool verbose);
14     void printError(int lineNum, const char* format, ...);
15     void printWarning(int lineNum, const char* format, ...);
16     void printMessage(int lineNum, const char* format, ...);
17     void printVerbose(int lineNum, const char* format, ...);
18     void printSummary(void);
19     bool errorOccured(void) {return(mErrorCount > 0);}
20
21 private:
22     Console(); ///< Private singleton constructor
23     static Console mInstance;
24     int mErrorCount; ///< Number of times the error message function has been
        called
25     int mWarningCount; ///< Number of times the warning function has been called
26     bool mVerbose; ///< Whether or not to print verbose stuff.
27
28 };
29
30 // Convenience macros
31 #define ERROR(line, ...) Console::instance().printError(line, __VA_ARGS__)
32 #define WARNING(line, ...) Console::instance().printWarning(line, __VA_ARGS__)
33 #define MESSAGE(line, ...) Console::instance().printMessage(line, __VA_ARGS__)
34 #define VERBOSE(line, ...) Console::instance().printVerbose(line, __VA_ARGS__)

```

```

1 /** \file console.cpp
2  * \author Steven Bell <steven.bell@student.oc.edu>
3  * \date 12 December 2010
4  */
5
6 #include <cstdio>
7 #include <stdarg.h>
8 #include "console.h"
9
10 // Single instance instantiation
11 Console Console::mInstance;
12
13 Console::Console()
14 {
15     mErrorCount = 0;
16     mWarningCount = 0;
17 }
18
19 Console& Console::instance(void)
20 {
21     return(mInstance);
22 }
23
24 void Console::printError(int lineNum, const char*format, ...)
25 {

```

```

26     mErrorCount++;
27
28     va_list argptr;
29     va_start(argptr, format);
30     printf("%d_Error:_", lineNum);
31     vprintf(format, argptr);
32     printf("\n");
33     va_end(argptr);
34 }
35
36 void Console::printWarning(int lineNum, const char*format, ...)
37 {
38     mWarningCount++;
39
40     va_list argptr;
41     va_start(argptr, format);
42     printf("%d_Warning:_", lineNum);
43     vprintf(format, argptr);
44     printf("\n");
45     va_end(argptr);
46 }
47
48 void Console::printMessage(int lineNum, const char*format, ...)
49 {
50     va_list argptr;
51     va_start(argptr, format);
52     printf("%d:_", lineNum);
53     vprintf(format, argptr);
54     printf("\n");
55     va_end(argptr);
56 }
57
58 void Console::printVerbose(int lineNum, const char*format, ...)
59 {
60     if(mVerbose) {
61         va_list argptr;
62         va_start(argptr, format);
63         printf("%d:_", lineNum);
64         vprintf(format, argptr);
65         printf("\n");
66         va_end(argptr);
67     }
68 }
69
70 void Console::printSummary(void)
71 {
72     printf("\n");
73     printf("%d_errors,_%d_warnings\n", mErrorCount, mWarningCount);
74 }
75
76
77 void Console::setVerbose(bool verbose)
78 {
79     mVerbose = verbose;

```





## **F Final test program**

The code on the following pages is based on the test code provided on Blackboard and modified for my assembler. The code was syntax-highlighted with Vim.

```

* Final test program for IC design, Part A
* Steven Bell
* 13 December 2010
*
* Several changes were made from the code given on Blackboard to this code:
* - The assembler takes two opcodes at most, so adding an immediate to a register
*   puts the value back into that same register. A COPY is done first to achieve
*   the effect of adding an immediate and putting the result in another register.
* - The registers are labeled a through h.
* - RAM is located at 0x2000 through 0x3999.

* Test NOP
NOP

* Test LOAD and STORE with RAM
LOAD a, #0x55 * Load immediate
STORE a, 0x2000 * Store to RAM, 0x55 expected
LOAD b, 0x2000 * Load back from RAM into another register
STORE b, 0x2001 * Store back to RAM, 0x55 expected

* Test ADD
COPY c, b * Copy from b into c
ADD c, #0x22 * Add an immediate to c
STORE c, 0x2002 * Expect 0x77

* Test flags from ADD
LOAD e, #0x5A
ADD b, a * Should give 0xAA in b
ADD e, #0xA5 * Should give 0xFF in e
JCAR end * Should not jump
STORE b, 0x2003 * Should be 0xAA
STORE e, 0x2004 * Should be 0xFF
JZERO end * Should not jump

* Test SUBtract and flags
LOAD d, #0xA9
COPY f, b * Copy b to f (should be 0xAA)
SUB f, #0x33 * Subtract 0x33, f should be 0x77
SUB d, c * Subtract c from d, d should be 0x32
JCAR end * Should not jump
JZERO end * Should not jump
STORE d, 0x2005 * Should be 0x32
STORE f, 0x2006 * Should be 0x77
JMP pass1
HALT

pass1:
COPY a, e * Copy 0xFF into a
ADD a, #0xFF * Add 0xFF, should give 0xFE with carry
STORE a, 0x2007 * Should be 0xFE
JZERO end * Should not jump
JCAR pass2 * Should jump
HALT

pass2:
ADD a, #0x01 * Should give 0xFF, no carry
JZERO end * Should not jump
JCAR end * Should not jump
STORE a, 0x2008 * Should give 0xFF
ADD a, #0x01 * Should give 0x00 with a carry
JZERO pass3 * Should jump
HALT

pass3:
STORE a, 0x2009 * Should give 0x00
SUB d, #0x21 * Should give 0x11 in d
JZERO end * Should not jump
JCAR end * Should not jump
STORE d, 0x200A * Should give 0x11
SUB d, #0x11 * Should give 0x00 in d
JCAR end * Should not jump
JZERO pass4 * Should jump
HALT

pass4:

```

```

STORE d, 0x200B * Should give 0x00
SUB d, #0x33 * Should give -0x33 = 0xCD in d
JZERO end * Should not jump
JNEG pass5 * Should jump
HALT

pass5:
STORE d, 0x200C * Should give -0x33 = 0xCD
ADD f, #0x00 * f should contain 0x77, and it shouldn't change!
JCAR end * Should not branch
SUB f, e * e should contain 0xFF, giving 0x78 with a borrow
JZERO end * Should not jump
JNEG end * Should not jump (the resulting value is positive)
JCAR pass6 * Should jump (a borrow occurred)

* Test multiply
pass6:
STORE f, 0x200D * Should give 0x78
COPY g, b * Should give 0xAA in g
MUL g, #0xA5 * Multiply giving 6D92
STORE g, 0x200E * Store the top half of the multiply (0x6D)
STORE h, 0x200F * Store the bottom half of the multiply (0x92)
LOAD h, #0xBB * Load 0xBB into h
MUL h, g * Multiply the top and bottom half of gh together, result should be 0x4F9F
STORE g, 0x2010 * Write the result out (0x4F)
STORE h, 0x2011 * (0x9F)

* Test unary ALU operations
COPY b, a * b should contain 0x00
COMP b * b should be 0xFF
STORE b, 0x2012
COMP b * Complement again, should give 0x00
STORE b, 0x2013
JCAR end * Shouldn't jump
JZERO pass7 * Should jump
HALT

pass7:
COPY e, d * e should now contain 0xCD = 0b 1100 1101
LSR e * Logical shift right
STORE e, 0x2014 * Should be 0b 0110 0110 = 0x66
LSR e * Logical shift right again
STORE e, 0x2015 * Should be 0x 0011 0011 = 0x33
COPY g, e * g should now be 0x33
LSL g * Logical shift left
STORE g, 0x2016 * Should be 0x 0110 0110 = 0x66
LSL g
STORE g, 0x2017 * Should be 0x 1100 1100 = 0xCC

end:
NOP
NOP
HALT

```

```

* Final test program for IC design, Part B
* Steven Bell
* 14 December 2010
*
* Several changes were made from the code given on Blackboard to this code:
* - The assembler takes two opcodes at most, so adding an immediate to a register
*   puts the value back into that same register. A COPY is done first to achieve
*   the effect of adding an immediate and putting the result in another register.
* - The registers are labeled a through h.
* - RAM is located at 0x2000 through 0x3999.

* Begin by loading registers with their nominal values from part A

LOAD a, #0x55
LOAD b, #0xFF
LOAD c, #0xFF
LOAD d, #0x33
* e will be assigned later
LOAD f, #0x03
* g will be assigned later
LOAD h, #0xC0

* Continue testing shifts
COPY e, d * Copy 0x33 = 0b 0011 0011 into e
LSR e * Shift e right (shift in a 0, giving 0b 0001 1001 = 0x19)
STORE e, 0x2000 * Should give 0x19
LSR e * 0b 0000 1100 = 0x0C
STORE e, 0x2001 * Should give 0x0C
COPY g, e
LSL g * 0b 0001 1000 = 0x18
STORE g, 0x2002 * Should give 0x18
LSL g * 0b 0011 0000 = 0x30
STORE g, 0x2003 * Should give 0x30

* Test shifts with jumps
LSR f * Shift 0b 0000 0011 to get 0b 0000 0001 with a carry
JCAR shift1 * Should jump
HALT

shift1:
LSR f * f should now be 0x00
JZERO shift2 * Should jump
HALT

shift2:
LSL h * h was 0xC0 = 0b 1100 0000, should now be 0b 1000 0000 with a carry
JCAR shift3 * Should jump
HALT

shift3:
LSL h * h will now be 0x00
JZERO pass8 * Should jump
HALT

* Test AND
pass8:
COPY f, a * Copy 0x55 into f
AND f, #0x0F * Mask the top four bits
STORE f, 0x2004 * Should be 0x05
AND e, a * e = 0b 0000 1100, a = 0b 0101 0101
STORE e, 0x2005 * Should be 0x04
COPY b, f * Copy 0x00 into b
AND b, #0xF0
STORE b, 0x2006 * Should be 0x00
JZERO pass9
HALT

* Test AND of 0x00 and 0xFF, and jump on zero
pass9:
AND c, b * c = 0xFF, b = 0x00
STORE c, 0x2007 * Should be 0x00
JZERO pass10 * Should jump
HALT

* Test OR

```

```


pass10:
COPY c, a * Copy 0x55 into c
OR c, #0xA0 * 0b 0101 0101 OR 0b 1010 0000 gives 0xF5
STORE c, 0x2008 * Should be 0xF5
OR g, e * g = 0x30 OR e = 0x04
STORE g, 0x2009 * Should be 0x34
COPY c, h * Copy 0x00 into c
OR c, #0x00
STORE c, 0x200A * Should be 0x00
JZERO pass11 * Should jump
HALT

pass11:
OR h, b * 0x00 OR 0x00
STORE h, 0x200B * Should be 0x00
JZERO end * Should jump
HALT

end:
STORE a, 0x200C * Should be 0x55
MOVE 0x200C, 0x200D * Put 0x55 into 0x200C
LOAD b, 0x200D
HALT


```

## G Logic analyzer captures

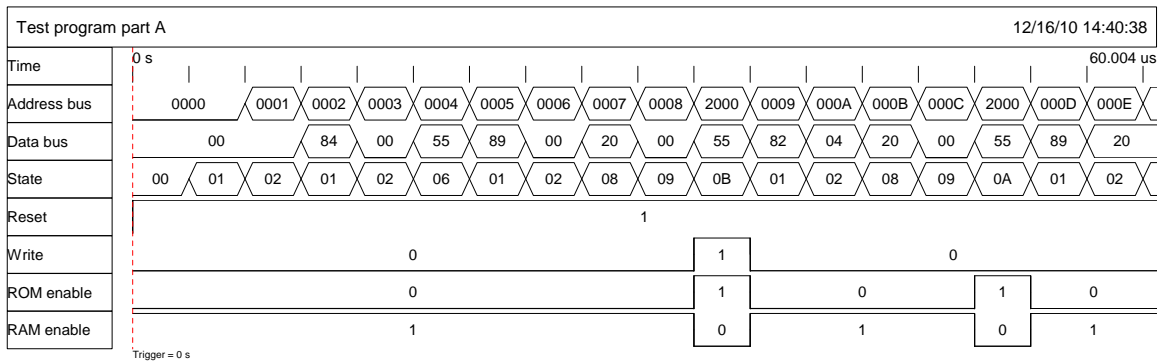

Time -23.957549 ns to 60.804259431 us

Page 1

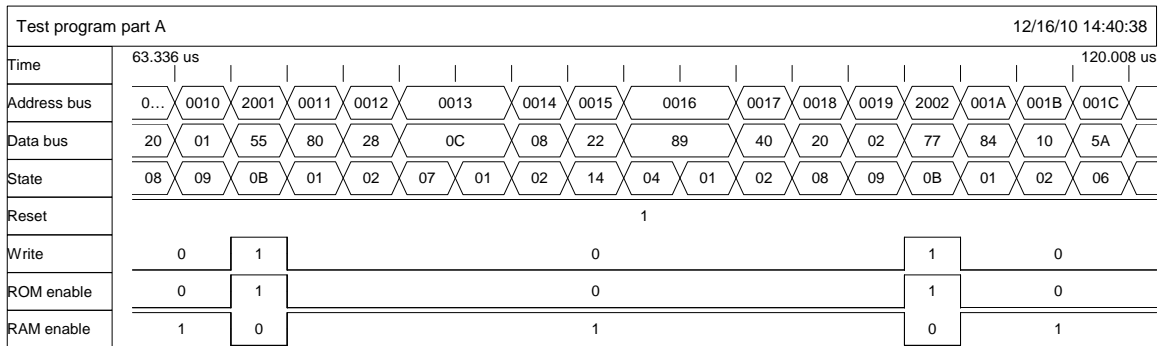

Time 60.816238206 us to 121.644455186 us

Page 2



Test program part A															12/16/10 14:40:38																					
Time	123.34 us																		180.012 us																	
Address bus	001E		001F			0020		0021		0022		0023		0024		0025		0026		0027		0028		0029		2003		0...								
Data bus	04		0C			10		A5		78		01		19		89		20			03		AA		89											
State	02		03		04		01		02		14		04		01		02		10		11		12		01		02		08		09		0B		01	
Reset	1																																			
Write	0																		1		0															
ROM enable	0																		1		0															
RAM enable	1																		0		1															

Time 121.656433961 us to 182.484650941 us

Page 3

Test program part A																	12/16/10 14:40:38		
Time	183.348 us																	240.016 us	
Address bus	002B	002C	002D	2004	002E	002F	0030	0031	0032		0033	0034	0035	0036	0037		0038	0039	
Data bus	80	20	04	FF	78	02	01	19	84		0C	A9	80	34	14		33		
State	02	08	09	0B	01	02	10	11	12	01	02	06	01	02	07	01	02	14	
Reset	1																		
Write	0			1		0													
ROM enable	0			1		0													
RAM enable	1			0		1													

Time 182.496629716 us to 243.324846696 us

Page 4

Test program part A																12/16/10 14:40:38																				
Time	243.352 us																303.356 us																			
Address bus	003A		003B		003C			003D		003E		003F		0040		0041		0042		0043		0044		0045		0046										
Data bus	10		4C		78			01		19		78		02		01		19		89		60		20												
State	04		01		02		03		04		01		02		10		11		12		01		02		10		11		12		01		02		08	
Reset																	1																			
Write																	0																			
ROM enable																	0																			
RAM enable																	1																			

Time 243.336825471 us to 304.165042451 us

Page 5

Test program part A																	12/16/10 14:40:38		
Time	306.688 us																	363.36 us	
Address bus	0...	2005	0048	0049	004A	004B	2006	004C	004D	004E	004F	0050	0052	0053	0054	0055	0056		
Data bus	05	32	89	A0	20	06	77	78	00		52	F8	80		0C	00	FF		
State	09	0B	01	02	08	09	0B	01	02	10	11	12	01	02	07	01	02	14	
Reset	1																		
Write	0	1	0				1	0											
ROM enable	0	1	0				1	0											
RAM enable	1	0	1				0	1											

Time 304.177021225 us to 365.005238206 us

Page 6

Test program part A																	12/16/10 14:40:38		
Time	366.692 us																	423.364 us	
Address bus	0057	0058	0059	005A	2007	005B	005C	005D	005E	005F	0060	0061	0062	0063	0065	0066	0...		
Data bus	89	00	20	07	FE	78	02	01	19	78	01	00	65	F8	0C	00	01		
State	01	02	08	09	0B	01	02	10	11	12	01	02	10	11	12	01	02	14	
Reset	1																		
Write	0				1		0												
ROM enable	0				1		0												
RAM enable	1				0		1												

Time 365.01721698 us to 425.845433961 us

Page 7

Test program part A																12/16/10 14:40:38		
Time	426.696 us															483.368 us		
Address bus	0068	0069	006A	006B	006C	006D	006E	006F	0070	0071	0072	0073	2008	0074	0075			
Data bus	78	02	01	19	78	01	19	89	00	20	08	FF	0C	00				
State	04	01	02	10	11	12	01	02	10	11	12	01	02	08	09	0B	01	02
Reset	1																	
Write	0															1	0	
ROM enable	0															1	0	
RAM enable	1															0	1	

Time 425.857412735 us to 486.685629716 us

Page 8

Test program part A																12/16/10 14:40:38
Time	486.704 us															546.708 us
Address bus	0076	0077	0078	0079	007A	007B	007D	007E	007F	0080	2009	0081	0082	0083	0084	0085
Data bus	01	78	02	00	7D	F8	89	00	20	09	00	14	0C	21	78	02
State	14	04	01	02	10	11	12	01	02	08	09	0B	01	02	14	04
Reset	1															
Write	0										1	0				
ROM enable	0										1	0				
RAM enable	1										0	1				

Time 486.69760849 us to 547.525825471 us

Page 9

Test program part A																12/16/10 14:40:38
Time	550.04 us															606.712 us
Address bus	0...	0087	0088	0089	008A	008B	008C	008D	008E	008F	200A	0090	0091	0092	0093	
Data bus	01	19	78	01	19	89	60	20	0A	11	14	0C	11	78		
State	10	11	12	01	02	10	11	12	01	02	08	09	0B	01	02	14
Reset	1															
Write	0										1	0				
ROM enable	0										1	0				
RAM enable	1										0	1				

Time 547.537804245 us to 608.366021225 us

Page 10

Test program part A																12/16/10 14:40:38																				
Time	610.044 us																666.716 us																			
Address bus	0095		0096		0097		0098		0099		009A		009B		009D		009E		009F		00A0		200B		00A1		00A2		00A3		00A4					
Data bus	01		19		78		02		00		9D		F8		89		60		20		0B		00		14		0C		33		78					
State	10		11		12		01		02		10		11		12		01		02		08		09		0B		01		02		14		04		01	
Reset	1																																			
Write	0																						1		0											
ROM enable	0																						1		0											
RAM enable	1																						0		1											

Time 608.378 us to 669.20621698 us

Page 11

Test program part A																12/16/10 14:40:38		
Time	670.048 us																726.72 us	
Address bus	00A5	00A6	00A7	00A8	00A9	00AA	00AB	00AC	00AE	00AF	00B0	00B1	200C	00B2	00B3	00B4	00B5	
Data bus	02	01	19	78	03	00	AE	F8	89	60	20	0C	CD	0C	14	00	78	
State	02	10	11	12	01	02	10	11	12	01	02	08	09	0B	01	02	14	04
Reset	1																	
Write	0												1		0			
ROM enable	0												1		0			
RAM enable	1												0		1			

Time 669.218195755 us to 730.046412735 us

Page 12

Test program part A															12/16/10 14:40:38					
Time	733.388 us															790.056 us				
Address bus	00B5	00B6	00B7	00B8	00B9	00BA	00BB		00BC	00BD	00BE	00BF	00C0	00C1	00C2					
Data bus	78	01		19	10		94	78		02	01	19	78		03	01	19			
State	01	02	10	11	12	01	02	03	04	01	02	10	11	12	01	02	10	11		
Reset	1																			
Write	0																			
ROM enable	0																			
RAM enable	1																			

Time 730.05839151 us to 790.88660849 us

Page 13

Test program part A																12/16/10 14:40:38		
Time	793.392 us																850.064 us	
Address bus	00C3	00C4	00C5	00C6	00C7	00C8	00C9	00CA	200D	00CB	00CC	00CD	00CE	00CF	00D0			
Data bus	78	01	00	C7	89	A0	20	0D	78	80	38	1C	18	A5	89			
State	12	01	02	10	11	12	01	02	08	09	0B	01	02	07	01	02	14	04
Reset	1																	
Write	0								1	0								
ROM enable	0								1	0								
RAM enable	1								0	1								

Time 790.898587265 us to 851.726804245 us

Page 14

Test program part A																12/16/10 14:40:38				
Time	853.396 us																910.068 us			
Address bus	00D0	00D1	00D2	00D3	200E	00D4	00D5	00D6	00D7	200F	00D8	00D9	00DA	00DB	00DC	00DD				
Data bus	89	C0	20	0E	6D	89	E0	20	0F	92	84	1C	BB	18	DC	89				
State	01	02	08	09	0B	01	02	08	09	0B	01	02	06	01	02	03	04	05		
Reset	1																			
Write	0				1		0				1		0							
ROM enable	0				1		0				1		0							
RAM enable	1				0		1				0		1							

Time 851.73878302 us to 912.567 us

Page 15

Test program part A																12/16/10 14:40:38																				
Time	913.4 us																973.404 us																			
Address bus	00DD		00DE		00DF		00E0		2010		00E1		00E2		00E3		00E4		2011		00E5		00E6		00E7		00E8		00E9							
Data bus	89		C0		20		10		4F		89		E0		20		11		9F		80		04		40		04		89							
State	01		02		08		09		0B		01		02		08		09		0B		01		02		07		01		02		03		04		01	
Reset	1																																			
Write	0				1		0				1		0																							
ROM enable	0				1		0				1		0																							
RAM enable	1				0		1				0		1																							

Time 912.578978775 us to 973.407195755 us

Page 16

Test program part A																12/16/10 14:40:38		
Time	976.74 us																1.033408 ms	
Address bus	00EA	00EB	00EC	2012	00ED	00EE	00EF		00F0	00F1	00F2	2013	00F3	00F4	00F5	00F6	00F7	
Data bus	20		12	FF	40	04	89		20		13	00	78	01		19	78	
State	02	08	09	0B	01	02	03	04	01	02	08	09	0B	01	02	10	11	12
Reset	1																	
Write	0		1		0						1		0					
ROM enable	0		1		0						1		0					
RAM enable	1		0		1						0		1					

Time 973.419174529 us to 1.03424739151 ms


Page 17

Test program part A																12/16/10 14:40:38		
Time	1.036744 ms																1.093412 ms	
Address bus	0...	00F8	00F9	00FA	00FB	00FD	00FE	00FF	0100	0101		0102	0103	0104	2014	0105		
Data bus	78	02	00	FD	F8	80	70	30	10	89		80	20	14	66	30		
State	01	02	10	11	12	01	02	07	01	02	03	04	01	02	08	09	0B 01	
Reset	1																	
Write	0														1		0	
ROM enable	0														1		0	
RAM enable	1														0		1	

Time 1.034259370284 ms to 1.095087587265 ms


Page 18



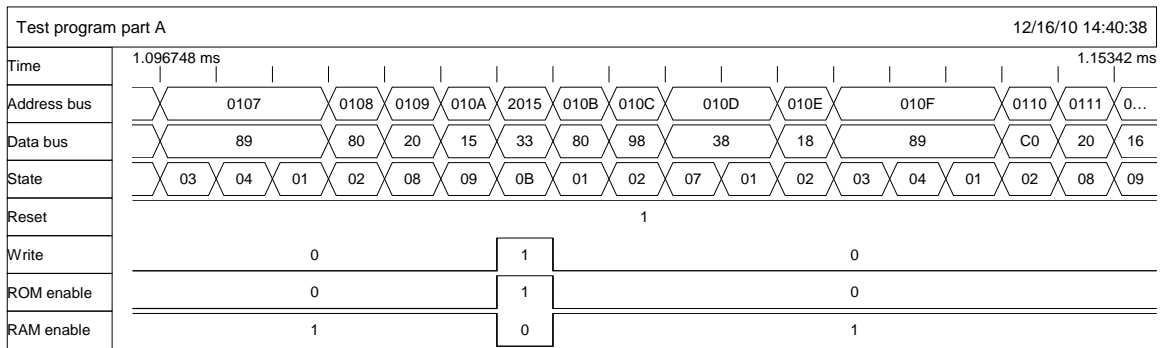

Time 1.095099566039 ms to 1.15592778302 ms

Page 19

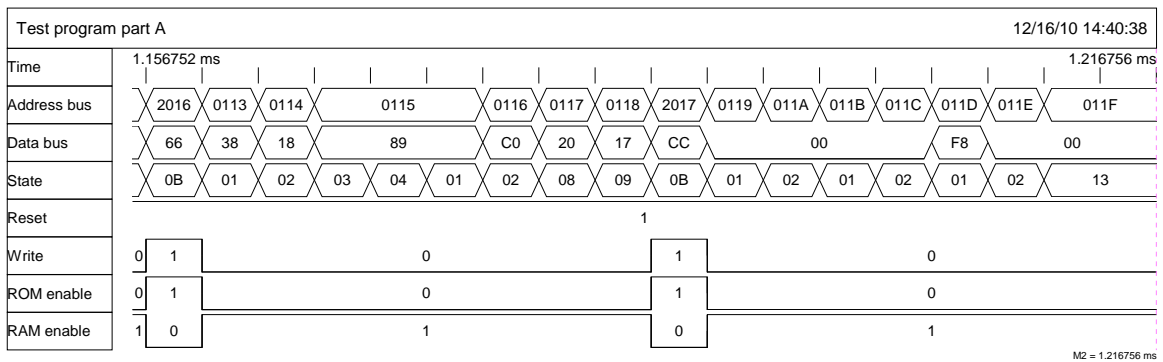

Time 1.155939761794 ms to 1.216767978775 ms

Page 20

Test program part B																12/16/10 14:49:41
Time	0 s															56.672 us
Address bus	0000	0001	0002	0003	0004	0005	0006	0007	0008	0009	000A	000B	000C	000D	000E	000F
Data bus	84	00	55	84	04	FF	84	08	FF	84	0C	33	84	14	03	84
State	00	01	02	06	01	02	06	01	02	06	01	02	06	01	02	06
Reset	1															
Write	0															
ROM enable	0															
RAM enable	1															

Trigger = 0 s

Time -22.973615 ns to 58.30703518 us

Page 1

Test program part B																12/16/10 14:49:41
Time	60.004 us															113.344 us
Address bus	0011	0012	0013	0014	0015	0016		0017	0018	0019	2000	001A	001B	001C		
Data bus	C0	80	70	30	10	89		80	20	00	19	30	10	89		
State	06	01	02	07	01	02	03	04	01	02	08	09	0B	01	02	03
Reset	1															
Write	0										1		0			
ROM enable	0										1		0			
RAM enable	1										0		1			

Time 58.318521987 us to 116.648530782 us

Page 2

Test program part B															12/16/10 14:49:41		
Time	116.676 us															173.348 us	
Address bus	001C	001D	001E	001F	2001	0020	0021	0022	0023	0024		0025	0026	0027	2002		
Data bus	89	80	20	01	0C	80	98	38	18	89		C0	20	02	18		
State	01	02	08	09	0B	01	02	07	01	02	03	04	01	02	08	09	0B
Reset	1																
Write	0				1		0								1		0
ROM enable	0				1		0								1		0
RAM enable	1				0		1								0		1

Time 116.66001759 us to 174.990026385 us

Page 3

Test program part B															12/16/10 14:49:41				
Time	176.68 us															230.016 us			
Address bus	0029		002A			002B	002C	002D	2003	002E	002F	0030			0031	0032	0033	0034	
Data bus	18		89			C0	20	03	30		14	78			01	00	36	F8	
State	02		03	04	01	02	08	09	0B	01	02	03	04	01	02	10	11	12	
Reset	1																		
Write	0								1	0									
ROM enable	0								1	0									
RAM enable	1								0	1									

Time 175.001513192 us to 233.331521987 us

Page 4

Test program part B																12/16/10 14:49:41				
Time	233.352 us																290.024 us			
Address bus	0036	0037	0038		0039	003A	003B	003C	003E	003F	0040		0041	0042	0043					
Data bus	30	14	78		02	00	3E	F8	38	1C	78		01	00	46					
State	01	02	03	04	01	02	10	11	12	01	02	03	04	01	02	10	11			
Reset	1																			
Write	0																			
ROM enable	0																			
RAM enable	1																			

Time 233.343008795 us to 291.67301759 us

Page 5

Test program part B															12/16/10 14:49:41					
Time	293.356 us															346.692 us				
Address bus	0046	0047	0048		0049	004A	004B	004C	004E	004F	0050	0051	0052	0053						
Data bus	38	1C	78		02	00	4E	F8	80	14	24	14	0F	89						
State	01	02	03	04	01	02	10	11	12	01	02	07	01	02	14	04	01			
Reset	1																			
Write	0																			
ROM enable	0																			
RAM enable	1																			

Time 291.684504397 us to 350.014513192 us

Page 6

Test program part B															12/16/10 14:49:41	
Time	350.028 us														406.696 us	
Address bus	0054	0055	0056	2004	0057	0058	0059			005A	005B	005C	2005	005D	005E	005F
Data bus	A0	20	04	05	20	10	89			80	20	05	04	80	A4	24
State	02	08	09	0B	01	02	03	04	01	02	08	09	0B	01	02	07 01
Reset	1															
Write	0		1		0						1		0			
ROM enable	0		1		0						1		0			
RAM enable	1		0		1						0		1			

Time 350.026 us to 408.356008795 us

Page 7

Test program part B															12/16/10 14:49:41	
Time	410.032 us														463.368 us	
Address bus	0061	0062	0063	0064	0065	2006	0066	0067	0068	0069	006A	006C	006D	006E		
Data bus	F0	89	20		06	00	78	02	00	6C	F8	20	28	89		
State	14	04	01	02	08	09	0B	01	02	10	11	12	01	02	03	04 01
Reset	1															
Write	0				1		0									
ROM enable	0				1		0									
RAM enable	1				0		1									

Time 408.367495603 us to 466.697504397 us

Page 8

Test program part B															12/16/10 14:49:41	
Time	470.036 us														523.372 us	
Address bus	006F	0070	0071	2007	0072	0073	0074	0075	0076	0078	0079	007A	007B	007C	007D	
Data bus	40	20	07	00	78	02	00	78	F8	80	08	2C	08	A0	89	
State	02	08	09	0B	01	02	10	11	12	01	02	07	01	02	14	04 01
Reset	1															
Write	0		1										0			
ROM enable	0		1										0			
RAM enable	1		0										1			

Time 466.708991205 us to 525.039 us

Page 9

Test program part B															12/16/10 14:49:41	
Time	526.704 us														583.376 us	
Address bus	007F	0080	2008	0081	0082	0083			0084	0085	0086	2009	0087	0088	0089	008A
Data bus	20	08	F5	28	98	89			C0	20	09	34	80	E8	2C	08
State	08	09	0B	01	02	03	04	01	02	08	09	0B	01	02	07	01 02
Reset	1															
Write	0		1								1		0			
ROM enable	0		1								1		0			
RAM enable	1		0								0		1			

Time 525.050486808 us to 583.380495603 us

Page 10

Test program part B															12/16/10 14:49:41		
Time	586.712 us															640.048 us	
Address bus	008B	008C	008D	008E	008F	200A	0090	0091	0092	0093	0094	0096	0097	0098			
Data bus	00	89	40	20	0A	00	78	02	00	96	F8	28	3C	89			
State	14	04	01	02	08	09	0B	01	02	10	11	12	01	02	03	04	
Reset	1																
Write	0					1							0				
ROM enable	0					1							0				
RAM enable	1					0							1				

Time 583.39198241 us to 641.721991205 us

Page 11

Test program part B															12/16/10 14:49:41		
Time	643.38 us															700.052 us	
Address bus	009A	009B	200B	009C	009D	009E	009F	00A0	00A2	00A3	00A4	00A5	200C	00A6	00A7	00A8	
Data bus	20	0B	00	78	02	00	A2	F8	89	00	20	0C	55	F8	00		
State	08	09	0B	01	02	10	11	12	01	02	08	09	0B	01	02	13	
Reset	1																
Write	0	1	0										1	0			
ROM enable	0	1	0										1	0			
RAM enable	1	0	1										0	1			

M2 = 700.052 us

M2 = 700.052 us

Time 641.733478013 us to 700.063486808 us

Page 12

151